

# **DIGITAL LOGIC CIRCUITS**

**Digital logic circuits**  electronic circuits that handle information encoded in binary form (deal with signals that have only two values, **0** and **1**)

◆ *Digital* .... computers, watches, controllers, telephones, cameras, ...

## **★ BINARY NUMBER SYSTEM**

---

*Number ....in  
whatever base*

*Decimal value of the given number*

---

Decimal:    **1,998**    =  $1 \times 10^3 + 9 \times 10^2 + 9 \times 10^1 + 8 \times 10^0 = 1,000 + 900 + 90 + 8 = 1,998$

Binary:

$$\begin{aligned} \textbf{11111001110} &= 1 \times 2^{10} + 1 \times 2^9 + 1 \times 2^8 + 1 \times 2^7 + 1 \times 2^6 + 1 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 = \\ &1,024 + 512 + 256 + 128 + 64 + 8 + 4 + 2 = \textbf{1,998} \end{aligned}$$


---

## Powers of 2

$N$	$2^N$	<i>Comments</i>
0	1	
1	2	
2	4	
3	8	
4	16	
5	32	
6	64	
7	128	
8	256	
9	512	
10	1,024	“Kilo” as $2^{10}$ is the closest power of 2 to 1,000 (decimal)
11	2,048	
15	32,768	$2^{15}$ Hz often used as clock crystal frequency in digital watches
20	1,048,576	“Mega” as $2^{20}$ is the closest power of 2 to 1,000,000 (decimal)
30	1,073,741,824	“Giga” as $2^{30}$ is the closest power of 2 to 1,000,000,000(decimal)

## Negative Powers of 2

$N < 0$	$2^N$
-1	$2^{-1} = 0.5$
-2	$2^{-2} = 0.25$
-3	$2^{-3} = 0.125$
-4	$2^{-4} = 0.0625$
-5	$2^{-5} = 0.03125$
-6	$2^{-6} = 0.015625$
-7	$2^{-7} = 0.0078125$
-8	$2^{-8} = 0.00390625$
-9	$2^{-9} = 0.001953125$
-10	$2^{-10} = 0.0009765625$
...	

 


### Binary numbers less than 1

<i>Binary</i>	<i>Decimal value</i>
<b>0.101101</b>	$= 1 \times 2^{-1} + 1 \times 2^{-3} + 1 \times 2^{-4} + 1 \times 2^{-6} = \mathbf{0.703125}$

## ◆ HEXADECIMAL

*Binary:*

**11111001110**

 

**111    1100    1110**

7

12

14

<== *Decimal*

Hexadecimal: 7CE

$$= 7 \times 16^2 + 12 \times 16^1 + 14 \times 16^0 = 1998$$

Binary	Decimal	Hexadecimal
0000	0	0
0001	1	1
0010	2	2
0011	3	3
0100	4	4
0101	5	5
0110	6	6
0111	7	7
1000	8	8
1001	9	9
1010	10	A
1011	11	B
1100	12	C
1101	13	D
1110	14	E
1111	15	F



## LOGIC OPERATIONS AND TRUTH TABLES


Digital logic circuits handle data encoded in binary form, i.e. signals that have only two values, **0** and **1**.

- ▶ Binary logic dealing with “true” and “false” comes in handy to describe the behaviour of these circuits: **0** is usually associated with “**false**” and **1** with “**true**.”
- ◆ Quite complex digital logic circuits (e.g. entire computers) can be built using a few *types of basic circuits* called **gates**, each performing a single elementary logic operation : *NOT*, *AND*, *OR*, **NAND**, **NOR**, etc..
- ▶ Boole’s binary algebra is used as a formal / mathematical tool to describe and design complex binary logic circuits.

## ◆ GATES


A	$\bar{A}$
0	1
1	0

*NOT*

 


A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

*AND*

 

A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

*OR*

 




... more GATES


A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

*NAND*

 

A	B	$\overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

*NOR*

 




... and more GATES


A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

*XOR*

 

A	B	$\overline{A \oplus B}$
0	0	1
0	1	0
1	0	0
1	1	1





*EQU or XNOR*

 

## ◆ GATES ... with more inputs


**EXAMPLES OF  
GATES WITH  
THREE INPUTS**

A	B	C	$A \cdot B \cdot C$	$A+B+C$	$\overline{A \cdot B \cdot C}$	$\overline{A+B+C}$
0	0	0	0	0	1	1
0	0	1	0	1	1	0
0	1	0	0	1	1	0
0	1	1	0	1	1	0
1	0	0	0	1	1	0
1	0	1	0	1	1	0
1	1	0	0	1	1	0
1	1	1	1	1	0	0

    

# ★ Logic Gate Array that Produces an Arbitrarily Chosen Output

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 



# BOOLEAN ALGEBRA

## AND rules

$$A \cdot A = A$$

$$A \cdot \overline{A} = 0$$

$$0 \cdot A = 0$$

$$1 \cdot A = A$$

$$A \cdot B = B \cdot A$$

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

$$A \cdot (B + C) = A \cdot B + A \cdot C$$

$$\overline{\overline{A} \cdot \overline{B}} = \overline{A} + \overline{B}$$

“ Proof ”:

A	B	C	$A \cdot (B+C)$	$A \cdot B + A \cdot C$
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

## BOOLEAN ALGEBRA ... continued

### ***OR* rules**

$$A + A = A$$

$$A + \overline{A} = 1$$

$$0 + A = A$$

$$1 + A = 1$$

$$A + B = B + A$$

$$A + (B + C) = (A + B) + C$$

$$A + B \cdot C = (A + B) \cdot (A + C)$$

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

A	B	C	$A + B \cdot C$	$(A+B) \cdot (A+C)$
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

# DeMorgan's Theorem


A	B	$\overline{A \cdot B}$	$\overline{A + B}$	$\overline{\overline{A} + \overline{B}}$	$\overline{\overline{A} \cdot \overline{B}}$
0	0	1	1	1	1
0	1	0	0	1	1
1	0	0	0	1	1
1	1	0	0	0	0

$\overline{A \cdot B} = A + B$

$\overline{A + B} = A \cdot B$


 
## Simplifying logic functions using Boolean algebra rules



Sum-of-products form of the logic function:

$$F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC$$


## Simplifying logic functions using Boolean algebra rules ... continued

$$F = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + A\overline{B}C + ABC$$

$$F = (\overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C) + (A\overline{B}C + ABC)$$

$$F = \overline{A}(\overline{B}\overline{C} + BC) + A(\overline{B}C + BC)$$
 
$$F = \overline{A}B(\underbrace{\overline{C} + C}_1) + AC(\underbrace{\overline{B} + B}_1)$$



$$F = \overline{A}B + AC$$




## Simplifying logic functions using Karnaugh maps

- ★ **Karnaugh map** => graphical representation of a truth table for a logic function.
- ★ Each line in the truth table corresponds to a square in the Karnaugh map.
- ★ The Karnaugh map squares are labeled so that horizontally or vertically adjacent squares differ only in one variable. (*Each square in the top row is considered to be adjacent to a corresponding square in the bottom row. Each square in the left most column is considered to be adjacent to a corresponding square in the right most column.*)


Karnaugh map

	A	B	C	F
(0)	0	0	0	...
(1)	0	0	1	...
(2)	0	1	0	...
(3)	0	1	1	...
(4)	1	0	0	...
(5)	1	0	1	...
(6)	1	1	0	...
(7)	1	1	1	...

 

## Simplifying logic functions of 4 variables using Karnaugh maps

	A	B	C	D	F
(0)	0	0	0	0	...
(1)	0	0	0	1	...
(2)	0	0	1	0	...
(3)	0	0	1	1	...
(4)	0	1	0	0	...
(5)	0	1	0	1	...
(6)	0	1	1	0	...
(7)	0	1	1	1	...
(8)	1	0	0	0	...
(9)	1	0	0	1	...
(10)	1	0	1	0	...
(11)	1	0	1	1	...
(12)	1	1	0	0	...
(13)	1	1	0	1	...
(14)	1	1	1	0	...
(15)	1	1	1	1	...

 


	A	B				
	C	D	00	01	11	10
00			0	4	12	8
01			1	5	13	9
11			3	7	15	11
10			2	6	14	10

## Simplifying logic functions using Karnaugh maps ... looping

- ★ The logic expressions for an output can be simplified by properly combining squares (**looping**) in the Karnaugh maps which contain 1s.
- ★ Looping a pair of adjacent 1s eliminates the variable that appears in both direct and complemented form.

	A	B	C	F
(0)	0	0	0	0
(1)	0	0	1	0
(2)	0	1	0	1
(3)	0	1	1	1
(4)	1	0	0	0
(5)	1	0	1	1
(6)	1	1	0	0
(7)	1	1	1	1

 


$$\rightarrow F = \bar{A}B + AC$$

## Simplifying logic functions using Karnaugh maps ... more looping

	A	B	C	D	F
(0)	0	0	0	0	1
(1)	0	0	0	1	0
(2)	0	0	1	0	1
(3)	0	0	1	1	0
(4)	0	1	0	0	0
(5)	0	1	0	1	1
(6)	0	1	1	0	0
(7)	0	1	1	1	1
(8)	1	0	0	0	0
(9)	1	0	0	1	0
(10)	1	0	1	0	0
(11)	1	0	1	1	0
(12)	1	1	0	0	1
(13)	1	1	0	1	1
(14)	1	1	1	0	1
(15)	1	1	1	1	1



 Looping a *quad* of adjacent 1s eliminates the two variables that appears in both direct and complemented form.





$$F = \overline{A} \overline{B} \overline{D} + AB + BD$$

## DeMorgan's Theorem

$$\begin{aligned} \overline{\overline{A} \cdot \overline{B}} &= \overline{A + B} \\ \overline{\overline{A} + \overline{B}} &= \overline{A \cdot B} \end{aligned}$$



## Equivalent Gate Symbols

  
  
## NAND gate implementation of the “sum-of-product” logic functions

$$F = \bar{A}B + AC$$

► NAND gates are faster than ANDs and ORs in most technologies





## ADDING BINARY NUMBERS



Adding two bits:


$$\begin{array}{r} 0+ \\ 0 \\ \hline 0 \end{array} \quad \begin{array}{r} 0+ \\ 1 \\ \hline 1 \end{array} \quad \begin{array}{r} 1+ \\ 0 \\ \hline 1 \end{array} \quad \begin{array}{r} 1+ \\ 1 \\ \hline 10 \end{array}$$

Carry      Sum  
(over)

The binary number 10 is equivalent to the decimal 2

*Truth table*


Inputs		Outputs	
A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

$$\text{Sum} = A + B$$

$$\text{Carry} = A \cdot B$$



*Half-Adder circuit*

 



  
## Adding multi-bit numbers:


$$\begin{array}{r}
 108_D + \\
 90_D \\
 \hline
 198_D
 \end{array}
 \quad
 \begin{array}{r}
 0\ 1\ 1\ 0\ 1\ 1\ 0\ 0 \\
 + \\
 0\ 1\ 0\ 1\ 1\ 0\ 1\ 0 \\
 \hline
 1\ 1\ 0\ 0\ 0\ 1\ 1\ 0
 \end{array}
 \quad
 \begin{array}{l}
 \text{Sum} \\
 \text{Carry}
 \end{array}$$



## ► Full Adder

 

Inputs			Outputs	
A	B	CI	CO	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

$$S = \overline{A} \cdot \overline{B} \cdot \overline{CI} + \overline{A} \cdot B \cdot \overline{CI} + A \cdot \overline{B} \cdot \overline{CI} + A \cdot B \cdot CI$$

$$C = A \cdot B + B \cdot CI + A \cdot CI$$




# HEX-TO-7 SEGMENT DECODER

► This examples illustrates how a practical problem is analyzed in order to generate truth tables, and then how truth table-defined functions are mapped on Karnaugh maps.

	B3	B2	B1	B0
(0)	0	0	0	0
(1)	0	0	0	1
(2)	0	0	1	0
(3)	0	0	1	1
(4)	0	1	0	0
(5)	0	1	0	1
(6)	0	1	1	0
(7)	0	1	1	1
(8)	1	0	0	0
(9)	1	0	0	1
(A)	1	0	1	0
(B)	1	0	1	1
(C)	1	1	0	0
(D)	1	1	0	1
(E)	1	1	1	0
(F)	1	1	1	1

 Four-bit  
“machine”  
representation  
of the hex  
digits




7-segment display to allow the user see the natural representation of the hex digits.

Binary outputs; when such a signal is = 1 then the corresponding segment in the 7-segment display is on (you see it), when the signal is = 0 then the segment is off (you can't see it).

The four-bit representation of the hex digits

“Natural” (i.e. as humans write) representation of the “hex” digits.

	B3	B2	B1	B0
(0)	0	0	0	0
(1)	0	0	0	1
(2)	0	0	1	0
(3)	0	0	1	1
(4)	0	1	0	0
(5)	0	1	0	1
(6)	0	1	1	0
(7)	0	1	1	1
(8)	1	0	0	0
(9)	1	0	0	1
(A)	1	0	1	0
(B)	1	0	1	1
(C)	1	1	0	0
(D)	1	1	0	1
(E)	1	1	1	0
(F)	1	1	1	1

 

We are developing ad-hoc "binary-hex logic" expressions used just for our convenience in the problem analysis process. Each expression will enumerate only those hex digits when the specific display-segment is "on":



$$S1 = 0+2+3+5+6+7+8+9+A+C+E+F$$

$$S2 = 0+1+2+3+4+7+8+9+A+D$$


$$S3 = 0+1+3+4+5+6+7+8+9+A+B+D$$

$$S4 = 0+2+3+5+6+8+9+B+C+D+E$$

$$S5 = 0+2+6+8+A+B+C+D+E+F$$

$$S6 = 0+4+5+6+8+9+A+B+C+E+F$$

$$S7 = 2+3+4+5+6+8+9+A+B+D+E+F$$

 

## ♦ Hex-to-7 segment

	B3	B2	B1	B0
(0)	0	0	0	0
(1)	0	0	0	1
(2)	0	0	1	0
(3)	0	0	1	1
(4)	0	1	0	0
(5)	0	1	0	1
(6)	0	1	1	0
(7)	0	1	1	1
(8)	1	0	0	0
(9)	1	0	0	1
(A)	1	0	1	0
(B)	1	0	1	1
(C)	1	1	0	0
(D)	1	1	0	1
(E)	1	1	1	0
(F)	1	1	1	1

$$S_1 = 0+2+3+5+6+7+8+9+A+C+E+F$$

$$S_2 = 0+1+2+3+4+7+8+9+A+D$$

$$S_3 = 0+1+3+4+5+6+7+8+9+A+B+D$$

$$S_4 = 0+2+3+5+6+8+9+B+C+D+E$$

$$S_5 = 0+2+6+8+A+B+C+D+E+F$$

$$S_6 = 0+4+5+6+8+9+A+B+C+E+F$$

$$S_7 = 2+3+4+5+6+8+9+A+B+D+E+F$$

As we are using ad-hoc “binary-hex logic” equations, (i.e. binary S... outputs as functions of hex variables) it will be useful in this case to have hex-labeled Karnaugh map, instead of the usual 2-D (i.e. two dimensional) binary labeled K-maps. This will allow for a more convenient mapping of the “binary-hex” logic equations onto the K-maps.



B3 B2	00	01	11	10
B1 B0	0	4	C	8
00	1	5	D	9
01	3	7	F	B
11	2	6	E	A
10				

## ♦ Hex-to-7 segment

Mapping the ad-hoc “binary-hex logic” equations onto Karnaugh maps:

B3 B2	B1 B0	00	01	11	10
00	0	4	C	8	
01	1	5	D	9	
11	3	7	F	B	
10	2	6	E	A	

$$\begin{aligned}
 S1 &= 0+2+3+5+6+7+8+9+A+C+E+F \\
 S2 &= 0+1+2+3+4+7+8+9+A+D \\
 S3 &= 0+1+3+4+5+6+7+8+9+A+B+D \\
 S4 &= 0+2+3+5+6+8+9+B+C+D+E
 \end{aligned}$$

B3 B2	B1 B0	00	01	11	10
00	1	0	1	1	
01	0	1	0	1	
11	1	1	1	0	
10	1	1	1	1	

B3 B2	B1 B0	00	01	11	10
00	1	1	0	1	
01	1	1	1	1	
11	1	1	0	1	
10	0	1	0	1	

B3 B2	B1 B0	00	01	11	10
00	1	1	0	1	
01	1	0	1	1	
11	1	1	0	0	
10	1	0	0	1	

B3 B2	B1 B0	00	01	11	10
00	1	0	1	1	
01	0	1	1	1	
11	1	0	0	1	
10	1	1	1	0	

♦ Hex-to-7 segment

B3 B2	00	01	11	10	
B1 B0	00	0	4	C	8
00	01	1	5	D	9
11	3	7	F	B	
10	2	6	E	A	

$$S5 = 0+2+6+8+A+B+C+D+E+F$$

$$S6 = 0+4+5+6+8+9+A+B+C+E+F$$

$$S7 = 2+3+4+5+6+8+9+A+B+D+E+F$$

**S5**

B3 B2	00	01	11	10	
B1 B0	00	1	0	1	1
00	01	0	0	1	0
11	0	0	1	1	
10	1	1	1	1	

**S6**

B3 B2	00	01	11	10	
B1 B0	00	1	1	1	1
00	01	0	1	0	1
11	0	0	1	1	
10	0	1	1	1	

**S7**

B3 B2	00	01	11	10	
B1 B0	00	0	1	0	1
00	01	0	1	1	1
11	1	0	1	1	
10	1	1	1	1	



# SYSTEMS of LOGIC FUNCTIONS

▷ 2-bit Comparator

	A <sub>1</sub>	A <sub>0</sub>	B <sub>1</sub>	B <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>
(0)	0	0	0	0	1	0	0
(1)	0	0	0	1	0	0	1
(2)	0	0	1	0	0	0	1
(3)	0	0	1	1	0	0	1
(4)	0	1	0	0	0	1	0
(5)	0	1	0	1	1	0	0
(6)	0	1	1	0	0	0	1
(7)	0	1	1	1	0	0	1
(8)	1	0	0	0	0	1	0
(9)	1	0	0	1	0	1	0
(10)	1	0	1	0	1	0	0
(11)	1	0	1	1	0	0	1
(12)	1	1	0	0	0	1	0
(13)	1	1	0	1	0	1	0
(14)	1	1	1	0	0	1	0
(15)	1	1	1	1	1	0	0



Compare two 2-bit numbers:

$$A=B \rightarrow F_1 = \Sigma (0,5,10,15)$$

$$A>B \rightarrow F_2 = \Sigma (4,8,9,12,13,14)$$

$$A<B \rightarrow F_3 = \Sigma (1,2,3,6,7,11)$$

## 2-bit Comparator

$$A=B \rightarrow F_1 = \Sigma (0,5,10,15)$$

		$A_1 A_0$			
		$B_1 B_0$			
		00	01	11	10
00		0	4	12	8
01		1	5	13	9
11		3	7	15	11
10		2	6	14	10

$A_1 A_0$	00	01	11	10
$B_1 B_0$	00	1	0	0
00	1	0	0	0
01	0	1	0	0
11	0	0	1	0
10	0	0	0	1


$$F_1 = \overline{(A_0 \oplus B_0)} \cdot \overline{(A_1 \oplus B_1)}$$

$F_1 = 1$  when both numbers, A and B, are equal which happens when all their bits of the same order are identical, i.e.  $A_0 \equiv B_0$  AND  $A_1 \equiv B_1$

## 2-bit Comparator

$$A < B \rightarrow F_3 = \Sigma (1, 2, 3, 6, 7, 11)$$

		$A_1 A_0$			
		$B_1 B_0$			
		00	01	11	10
<b>00</b>		0	4	12	8
<b>01</b>		1	5	13	9
<b>11</b>		3	7	15	11
<b>10</b>		2	6	14	10

 

$A_1 A_0$	00	01	11	10
$B_1 B_0$	00	0	0	0
00	0	0	0	0
01	1	0	0	0
11	1	1	0	1
10	1	1	0	0

$$F_3 = \overline{A_0}B_1B_0 + \overline{A_1}B_1 + \overline{A_1}\overline{A_0}B_0$$

## 2-bit Comparator

$$A > B \rightarrow F_2 = \Sigma (4, 8, 9, 12, 13, 14)$$

		A <sub>1</sub> A <sub>0</sub>	B <sub>1</sub> B <sub>0</sub>	00	01	11	10
		B <sub>1</sub> B <sub>0</sub>	00	0	1	1	1
		00	0	0	1	1	1
		01	0	0	0	0	0
		11	0	0	0	0	0
		10	0	0	1	0	0

		A <sub>1</sub> A <sub>0</sub>	B <sub>1</sub> B <sub>0</sub>	00	01	11	10
		B <sub>1</sub> B <sub>0</sub>	00	0	4	12	8
		01	1	5	13	9	
		11	3	7	15	11	
		10	2	6	14	10	

$$F_2 = \overline{F_1 + F_3}$$

		A <sub>1</sub> A <sub>0</sub>	B <sub>1</sub> B <sub>0</sub>	00	01	11	10
		B <sub>1</sub> B <sub>0</sub>	00	1	0	0	0
		00	1	1	0	0	0
		01	1	1	1	1	1
		11	1	1	0	1	1
		10	1	1	0	1	1

		A <sub>1</sub> A <sub>0</sub>	B <sub>1</sub> B <sub>0</sub>	00	01	11	10
		B <sub>1</sub> B <sub>0</sub>	00	1	0	0	0
		01	0	1	0	0	
		11	0	0	1	0	
		10	0	0	0	1	

		A <sub>1</sub> A <sub>0</sub>	B <sub>1</sub> B <sub>0</sub>	00	01	11	10
		B <sub>1</sub> B <sub>0</sub>	00	0	0	0	0
		01	1	0	0	0	
		11	1	1	0	1	
		10	1	1	0	0	


## 2-bit Comparator

$$F_1 = \overline{(A_0 \oplus B_0)} \cdot \overline{(A_1 \oplus B_1)}$$

$$F_2 = \overline{F_1 + F_3}$$

$$F_3 = \overline{A_0}B_1\overline{B_0} + \overline{A}_1B_1 + \overline{A}_1\overline{A}_0\overline{B}_0$$

 
B<sub>1</sub> B<sub>0</sub> A<sub>1</sub> A<sub>0</sub>





## 3-to-8 Decoder


	A	B	C	F <sub>0</sub>	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>	F <sub>4</sub>	F <sub>5</sub>	F <sub>6</sub>	F <sub>7</sub>
(0)	0	0	0	1	0	0	0	0	0	0	0
(1)	0	0	1	0	1	0	0	0	0	0	0
(2)	0	1	0	0	0	1	0	0	0	0	0
(3)	0	1	1	0	0	0	1	0	0	0	0
(4)	1	0	0	0	0	0	0	1	0	0	0
(5)	1	0	1	0	0	0	0	0	1	0	0
(6)	1	1	0	0	0	0	0	0	0	1	0
(7)	1	1	1	0	0	0	0	0	0	0	1

 




## 3-to-8 Decoder (74 138)

	A	B	C	$\bar{E}$	$\bar{F}_0$	$\bar{F}_1$	$\bar{F}_2$	$\bar{F}_3$	$\bar{F}_4$	$\bar{F}_5$	$\bar{F}_6$	$\bar{F}_7$
(x)	x	x	x	1	1	1	1	1	1	1	1	1
(0)	0	0	0	0	0	1	1	1	1	1	1	1
(1)	0	0	1	0	1	0	1	1	1	1	1	1
(2)	0	1	0	0	1	1	0	1	1	1	1	1
(3)	0	1	1	0	1	1	1	0	1	1	1	1
(4)	1	0	0	0	1	1	1	1	0	1	1	1
(5)	1	0	1	0	1	1	1	1	1	0	1	1
(6)	1	1	0	0	1	1	1	1	1	1	0	1
(7)	1	1	1	0	1	1	1	1	1	1	1	0

 



# BCD-TO-7 SEGMENT DECODER

 



	B3	B2	B1	B0
(0)	0	0	0	0
(1)	0	0	0	1
(2)	0	0	1	0
(3)	0	0	1	1
(4)	0	1	0	0
(5)	0	1	0	1
(6)	0	1	1	0
(7)	0	1	1	1
(8)	1	0	0	0
(9)	1	0	0	1
(x)	1	0	1	0
(x)	1	0	1	1
(x)	1	1	0	0
(x)	1	1	0	1
(x)	1	1	1	0
(x)	1	1	1	1

B3	B2	B1 B0			
		00	01	11	10
00	0	4	x	8	
01	1	5	x	9	
11	3	7	x	x	
10	2	6	x	x	

“Don’t Care” states/situations.  
As it is expected that these states are never going to occur, then we may just as well use them as fill-in “1s” in a Karnaugh map if this helps to make larger loopings

◆ BCD-to-7 segment

	B3	B2	B1	B0
(0)	0	0	0	0
(1)	0	0	0	1
(2)	0	0	1	0
(3)	0	0	1	1
(4)	0	1	0	0
(5)	0	1	0	1
(6)	0	1	1	0
(7)	0	1	1	1
(8)	1	0	0	0
(9)	1	0	0	1
(x)	1	0	1	0
(x)	1	0	1	1
(x)	1	1	0	0
(x)	1	1	0	1
(x)	1	1	1	0
(x)	1	1	1	1

  

$$S4 = 0+2+3+5+6+8+9$$

$$S5 = 0+2+6+8$$

$$S6 = 0+4+5+6+8+9$$

$$S7 = 2+3+4+5+6+8+9$$

$$S3 = 0+1+3+4+5+6+7+8+9$$

$$S4 = 0+2+3+5+6+8+9$$


$$S5 = 0+2+6+8$$

$$S6 = 0+4+5+6+8+9$$

$$S7 = 2+3+4+5+6+8+9$$

◆ BCD-to-7 segment


$$S1 = 0+2+3+5 \\ +6+7+8+9$$

 

$$S1 = \boxed{B3} + \overline{B2}\overline{B0} + \boxed{B1} \\ + \boxed{B2B1} + \boxed{B2B0}$$

B3 B2	00	01	11	10	
B1 B0	00	0	4	x	8
00	1	5	x	9	
01	3	7	x	x	
11	2	6	x	x	
10					

$$S2 = 0+1+2+3 \\ +4+7+8+9$$

 

$$S2 = \boxed{B3} + \overline{B2} + \boxed{B1B0} + \overline{\boxed{B1}\overline{B0}}$$

◆ BCD-to-7 segment

$$S3 = 0+1+3+4+5+6+7+8+9$$

B3	B2	$S3$			
B1	B0	00	01	11	10
	00	1	1	x	1
	01	1	1	x	1
11		1	1	x	x
10		0	1	x	x

$$S3 = \boxed{B3} + \textcircled{B1B0} + \boxed{\bar{B}1} + \boxed{B2}$$

B3	B2	00	01	11	10
B1	B0	00	01	11	10
	00	0	4	x	8
	01	1	5	x	9
11		3	7	x	x
10		2	6	x	x

$$S4 = 0+2+3+5+6+8+9$$

B3	B2	00	01	11	10
B1	B0	00	01	11	10
	00	1	0	x	1
	01	0	1	x	1
11		1	0	x	x
10		1	1	x	x

$$S4 = \boxed{B3} + \textcircled{\bar{B}2\bar{B}0} + \textcircled{\bar{B}2B1} + \textcircled{B2\bar{B}1B0} + \textcircled{B1\bar{B}0}$$

B3 B2				
B1 B0	00	01	11	10
00	0	4	x	8
01	1	5	x	9
11	3	7	x	x
10	2	6	x	x

◆ BCD-to-7 segment

$$S5 = 0+2+6+8$$

B3 B2				
B1 B0	00	01	11	10
00	1	0	x	1
01	0	0	x	0
11	0	0	x	x
10	1	1	x	x

$$S5 = \boxed{\overline{B2}\overline{B0}} + \boxed{B1\overline{B0}}$$

$$S6 = 0+4+5+6+8+9$$

B3 B2				
B1 B0	00	01	11	10
00	1	1	x	1
01	0	1	x	1
11	0	0	x	x
10	0	1	x	x

$$S6 = \boxed{B3} + \boxed{\overline{B1}\overline{B0}} + \boxed{\overline{B1}B2} + \boxed{B2\overline{B0}}$$

$$S7 = 2+3+4+5+6+8+9$$


B3 B2				
B1 B0	00	01	11	10
00	0	1	x	1
01	0	1	x	1
11	1	0	x	x
10	1	1	x	x

$$S7 = \boxed{B3} + \boxed{\overline{B2}B1} \\ + \boxed{\overline{B1}B2} + \boxed{B1\overline{B0}}$$







## MEMORY ELEMENTS: LATCHES AND FLIP-FLOPS

### ★ **R-S Latch** (Reset-Set)

 


$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	Q	$\bar{Q}$

    **Weird state**  
**Set state**  
**Reset state**  
**Hold state**



## ★ **D** (Transparent) Latch

 

Enable	D	S̄	R̄	Q	Q̄
0	0	1	1	Q	Q̄
0	1	1	1	Q	Q̄
1	0	1	0	0	1
1	1	0	1	1	0


S̄	R̄	Q	Q̄
0	0	1	1
0	1	1	0
1	0	0	1
1	1	Q	Q̄

Enable	D	Q	Q̄
0	x	Q	Q̄
1	0	0	1
1	1	1	0





When the **Enable** input is =1 (i.e. TRUE or HIGH) the information present at the **D** input is stored in the latch and will “appear as it is” at the **Q** output ( => it is like that there is a “transparent” path from the **D** input to the **Q** output)

## D Latch


 


<b>Enable</b>	<b>D</b>	<b>S</b>	<b>R</b>	<b>Q</b>	<b><math>\bar{Q}</math></b>
0	0	1	1	Q	$\bar{Q}$
0	1	1	1	Q	$\bar{Q}$
1	0	1	0	0	1
1	1	0	1	1	0

 

 


## Synchronous $D$ Flip-Flop

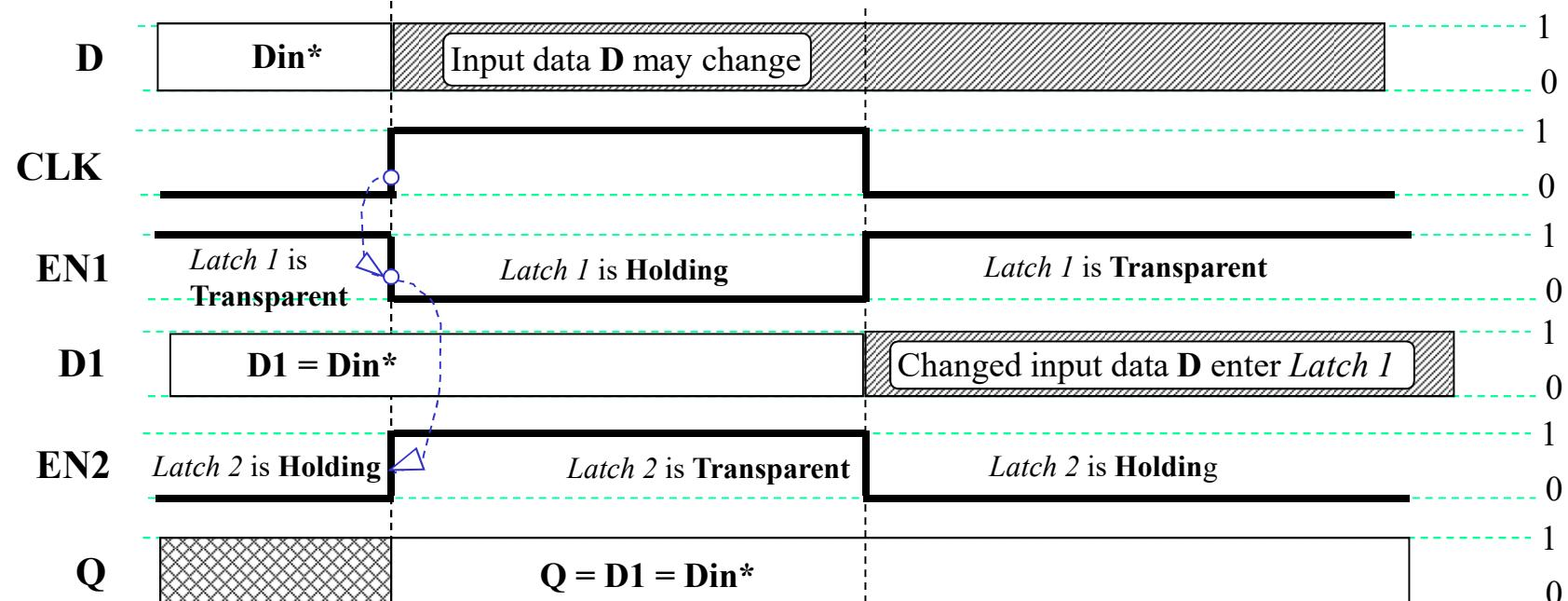 

The state of the flip-flop's output  $Q$  copies input  $D$  when the positive edge of the clock  $CLK$  occurs

Positive-Edge-Triggered  $D$  Flip-Flop

## ♦ Synchronous *D* Flip-Flop

 


Connection diagram  
of the **7474 Dual  
Positive-Edge-Triggered  
D Flip-Flops** with Preset  
and Clear.




 
## COUNTERS

4-Bit Synchronous Counter using  $D$  Flip-Flops



$$Q = \sum_{i=0}^3 Q_i \cdot 2^i$$

  

DECIMAL STATE <i>Q</i>	BINARY STATE OF THE COUNTER				FLIP FLOP INPUTS (for the next state)			
	Q3	Q2	Q1	Q0	D3	D2	D1	D0
0	0	0	0	0	0	0	0	1
1	0	0	0	1	0	0	1	0
2	0	0	1	0	0	0	1	1
3	0	0	1	1	0	1	0	0
4	0	1	0	0	0	1	0	1
5	0	1	0	1	0	1	1	0
6	0	1	1	0	0	1	1	1
7	0	1	1	1	1	0	0	0
8	1	0	0	0	1	0	0	1
9	1	0	0	1	1	0	1	0
10	1	0	1	0	1	0	1	1
11	1	0	1	1	1	1	0	0
12	1	1	0	0	1	1	0	1
13	1	1	0	1	1	1	1	0
14	1	1	1	0	1	1	1	1
15	1	1	1	1	0	0	0	0
0	0	0	0	0				

## ◆ Synchronous 4-bit Counter

Using D flip-flops has the distinct advantage of a straightforward definition of the flip-flop inputs: the current state of these inputs is the next state of the counter. The logic equations for all four flip-flop inputs D3, D2, D1, and D0 are derived from this truth table as functions of the current states of the counter's flip-flops: Q3, Q2, Q1, and Q0.

		Q3 Q2	00	01	11	10
		Q1 Q0	00	01	11	10
00	00	0	4	12	8	
01	01	1	5	13	9	
11	11	3	7	15	11	
10	10	2	6	14	10	

		Q3 Q2	00	01	11	10
		Q1 Q0	00	01	11	10
00	00	0	0	1	1	
01	01	0	0	1	1	
11	11	0	1	0	1	
10	10	0	0	1	1	

		Q3 Q2	00	01	11	10
		Q1 Q0	00	01	11	10
00	00	0	1	1	0	
01	01	0	1	1	0	
11	11	1	0	0	1	
10	10	0	1	1	0	

		Q3 Q2	00	01	11	10
		Q1 Q0	00	01	11	10
00	00	0	0	0	0	
01	01	1	1	1	1	
11	11	0	0	0	0	
10	10	1	1	1	1	

		Q3 Q2	00	01	11	10
		Q1 Q0	00	01	11	10
00	00	1	1	1	1	
01	01	0	0	0	0	
11	11	0	0	0	0	
10	10	1	1	1	1	

## ◆ Synchronous 4-bit Counter

		Q3 Q2		D3			
		Q1	Q0	00	01	11	10
00	00	0	0	1	1	1	1
01	01	0	0	1	1	1	1
11	11	0	1	0	1	1	1
10	10	0	0	1	1	1	1

$$D3 = Q3 \cdot \overline{Q2} + Q3 \cdot \overline{Q1} + Q3 \cdot \overline{Q0} + \overline{Q3} \cdot Q2 \cdot Q1 \cdot Q0$$

		Q3 Q2		D2			
		Q1	Q0	00	01	11	10
00	00	0	0	1	1	1	0
01	01	0	0	1	1	0	0
11	11	1	0	0	0	1	1
10	10	0	1	1	1	0	0

$$D2 = Q2 \cdot \overline{Q0} + Q2 \cdot \overline{Q1} + \overline{Q2} \cdot Q1 \cdot Q0$$

		Q3 Q2		D1			
		Q1	Q0	00	01	11	10
00	00	0	0	0	0	0	0
01	01	1	1	1	1	1	1
11	11	0	0	0	0	0	0
10	10	1	1	1	1	1	1

$$D1 = \overline{Q1} \cdot Q0 + Q1 \cdot \overline{Q0}$$

		Q3 Q2		D0			
		Q1	Q0	00	01	11	10
00	00	1	1	1	1	1	1
01	01	0	0	0	0	0	0
11	11	0	0	0	0	0	0
10	10	1	1	1	1	1	1

$$D0 = \overline{Q0}$$

## ◆ Synchronous 4-bit Counter

$$D_0 = \overline{Q_0}$$

$$D_1 = \overline{Q_1} \cdot Q_0 + Q_1 \cdot \overline{Q_0}$$

$$D_2 = Q_2 \cdot \overline{Q_0} + Q_2 \cdot \overline{Q_1} + \overline{Q_2} \cdot Q_1 \cdot Q_0$$

$$D_3 = Q_3 \cdot \overline{Q_2} + Q_3 \cdot \overline{Q_1} + Q_3 \cdot \overline{Q_0} \\ + \overline{Q_3} \cdot Q_2 \cdot Q_1 \cdot Q_0$$

