

Superconducting Digital Circuits II

Outline

**1. Josephson Switches, Memories
and Characteristic Times (see
Lecture 15 also)**


2. Voltage State Logic

3. Single Flux Quantum (SFQ) Logic

October 27, 2003




Superconducting Parameters

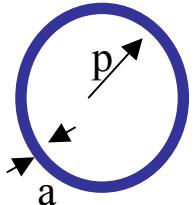

$$L[\text{nH}] = p[\mu\text{m}] \ln \frac{p}{a}$$

$$C_0 = 50 \text{ fF}/\mu\text{m}^2$$

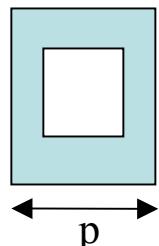

$$L[\text{nH}] = 1.2 p[\mu\text{m}]$$

$$R_n[\Omega] = \frac{190}{A[\mu\text{m}^2] J_c[kA\text{cm}^2]}$$




$$L[\text{nH}] = 1.2 (2\lambda + d)[\mu\text{m}]$$

$$\tau_J[\text{ps}] = 0.15 \left(\frac{R_n}{R_{sh}} \right)$$


$$\tau_{\text{RC}}[\text{ps}] = \frac{7.5}{J_c[kA/cm^2]} \left(\frac{R_{sh}}{R_n} \right)$$
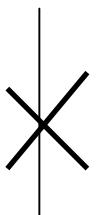
$$\beta_c = \frac{50}{J_c[kA/cm^2]} \left(\frac{R_{sh}}{R_n} \right)^2$$




$$L_J[\text{nH}] = \frac{300 \text{ pH}}{I_c[\mu\text{A}]}$$

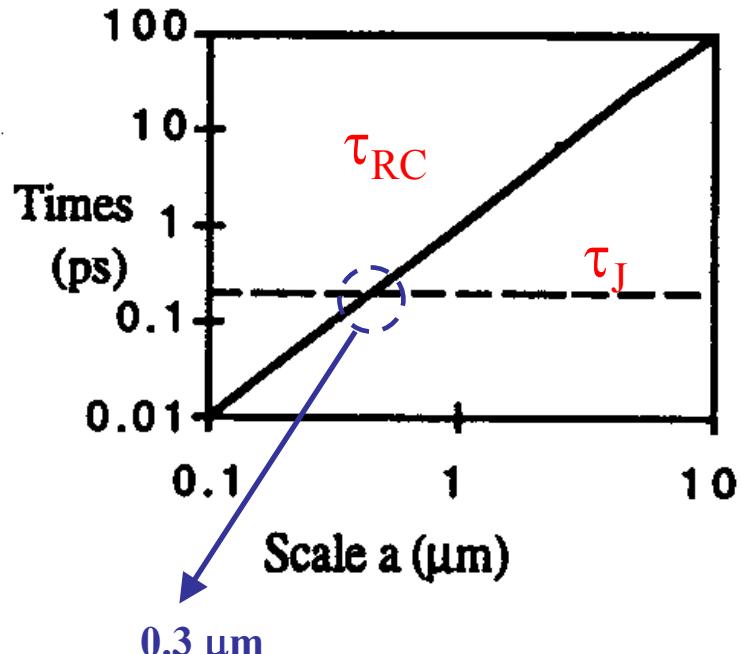Optimal Junction Size and Shunt Resistors







Optimal for self-shunting junctions

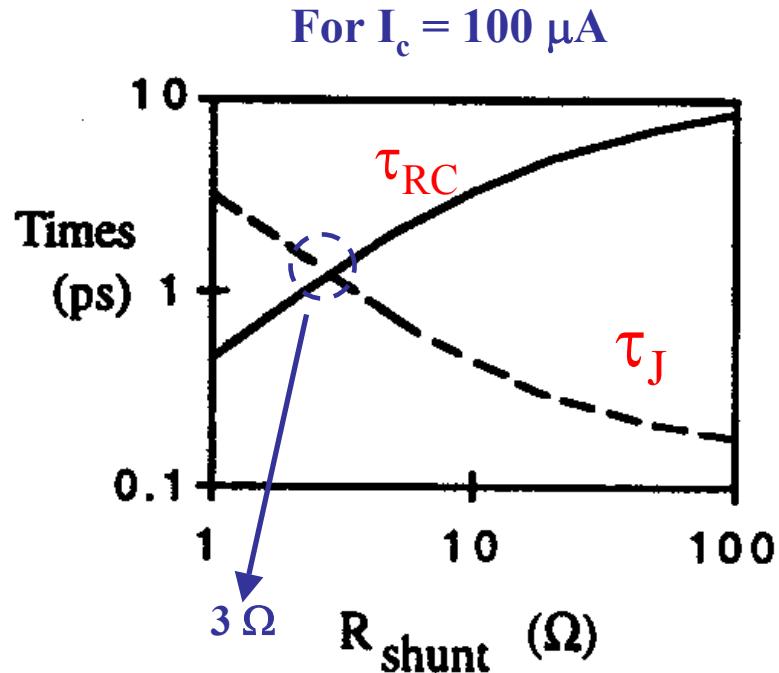

From A. M. Kadin, Introduction to Superconducting Circuits

Transient Response for $\beta_c \gg 1$

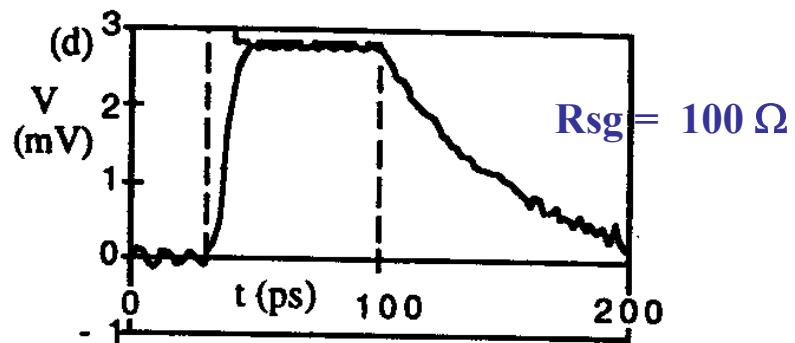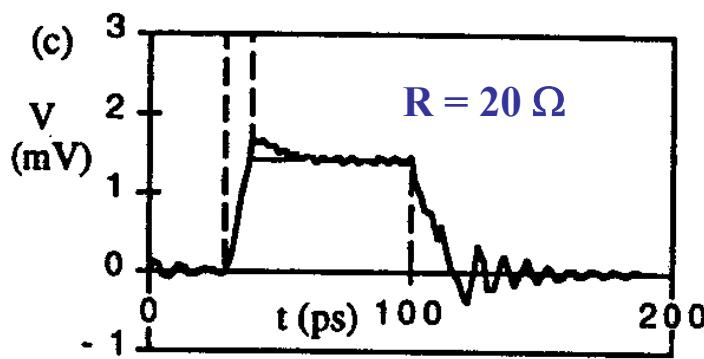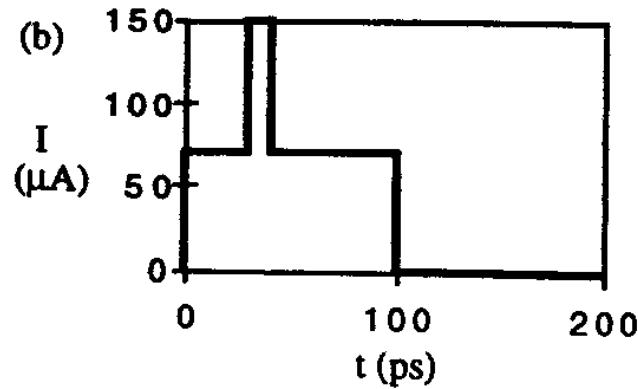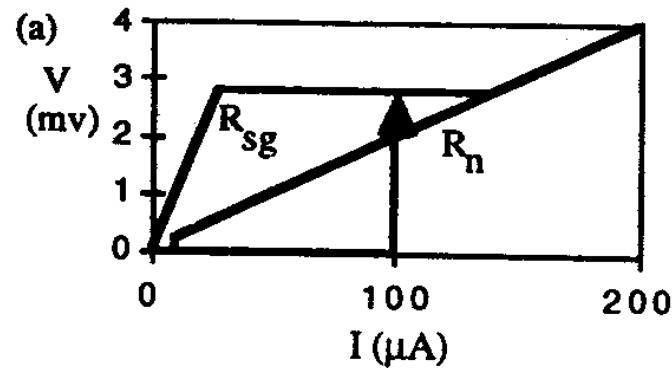

$$I_c = 100 \mu\text{A}, R_n = 20 \Omega, V_g = 2.8 \text{ mV}, \text{ and } C = 0.5 \text{ pF}$$


From A. M. Kadin, Introduction to Superconducting Circuits

Massachusetts Institute of Technology

6.763 2003 Lecture 16



Transient Response for $\beta_c \ll 1$

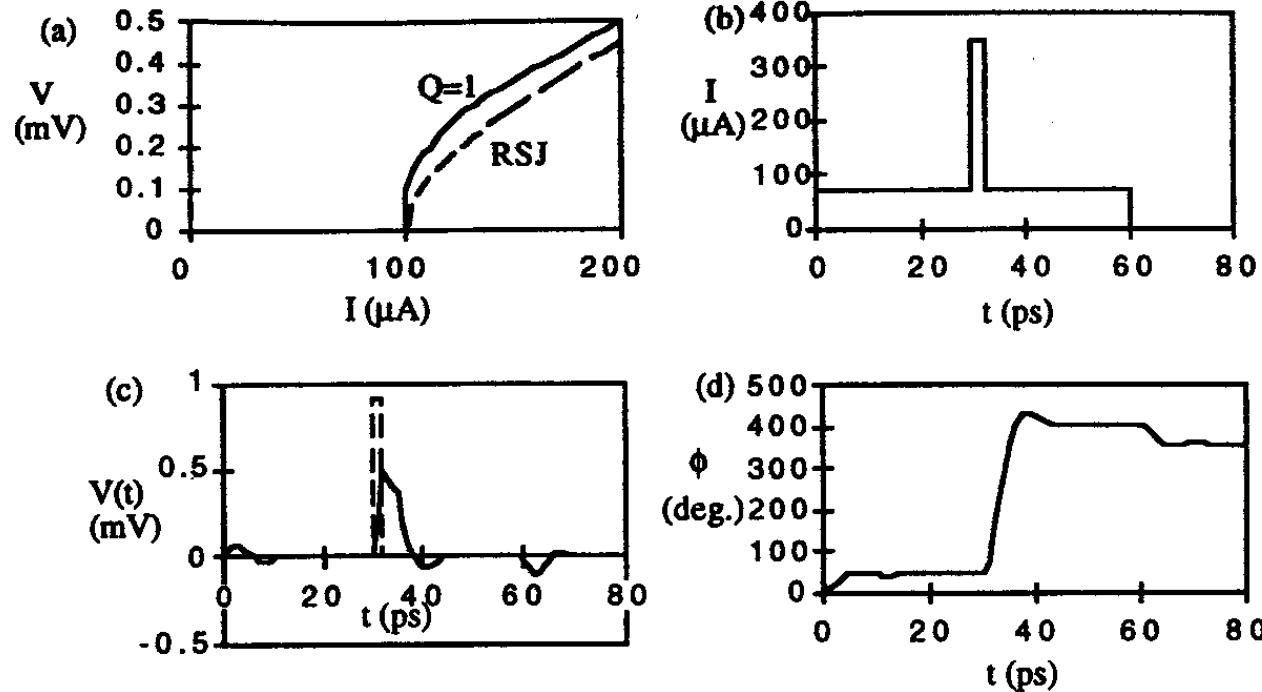

$$I_c = 100 \text{ } \mu\text{A}, R_{sh} = 2.6 \Omega, V_g = 2.8 \text{ mV}, \text{ and } C = 0.5 \text{ pF}$$


From A. M. Kadin, Introduction to Superconducting Circuits

Massachusetts Institute of Technology

6.763 2003 Lecture 16



Delay-Power Graph

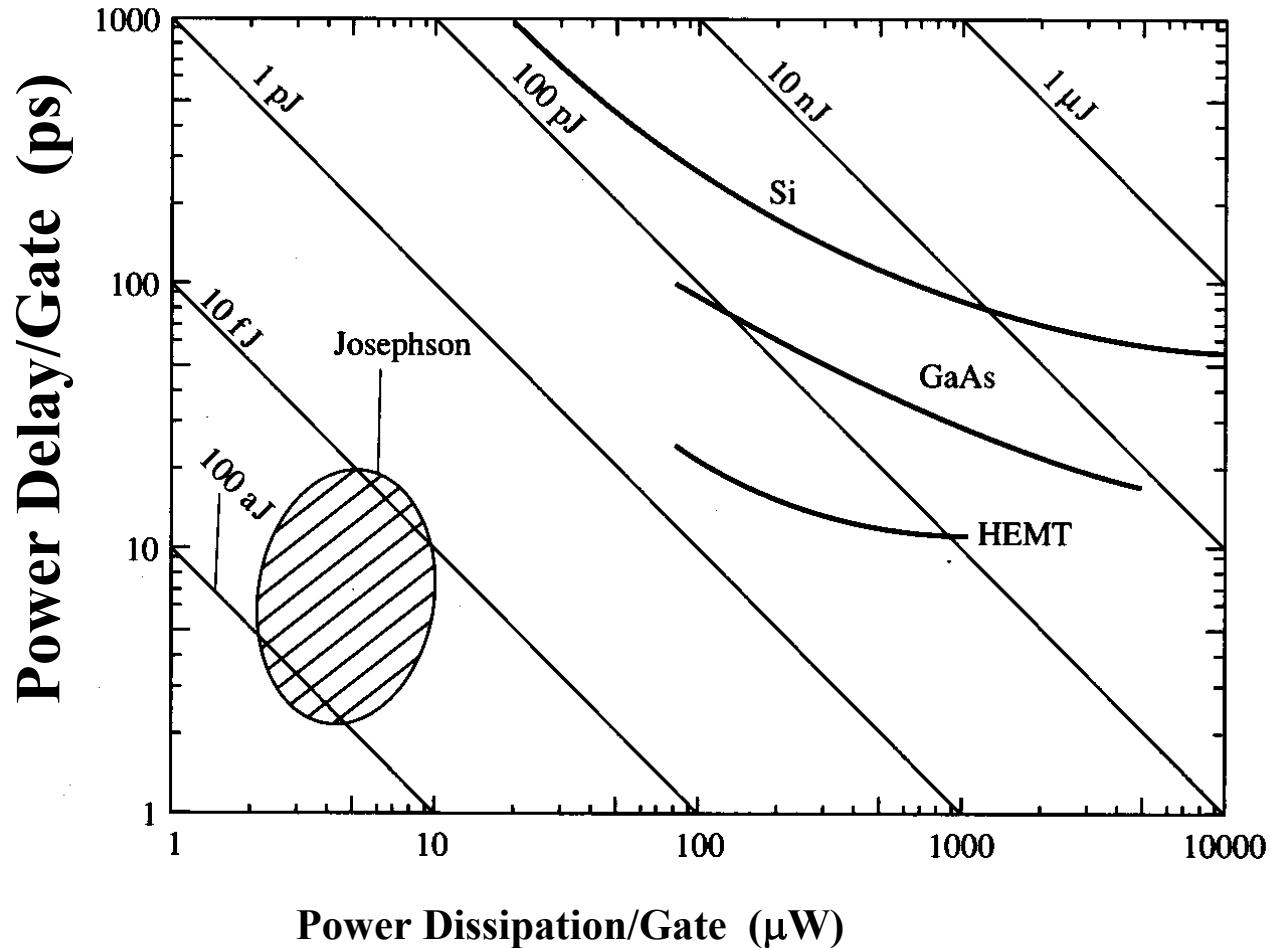


Massachusetts Institute of Technology

6.763 2003 Lecture 16




2. Voltage State Logic

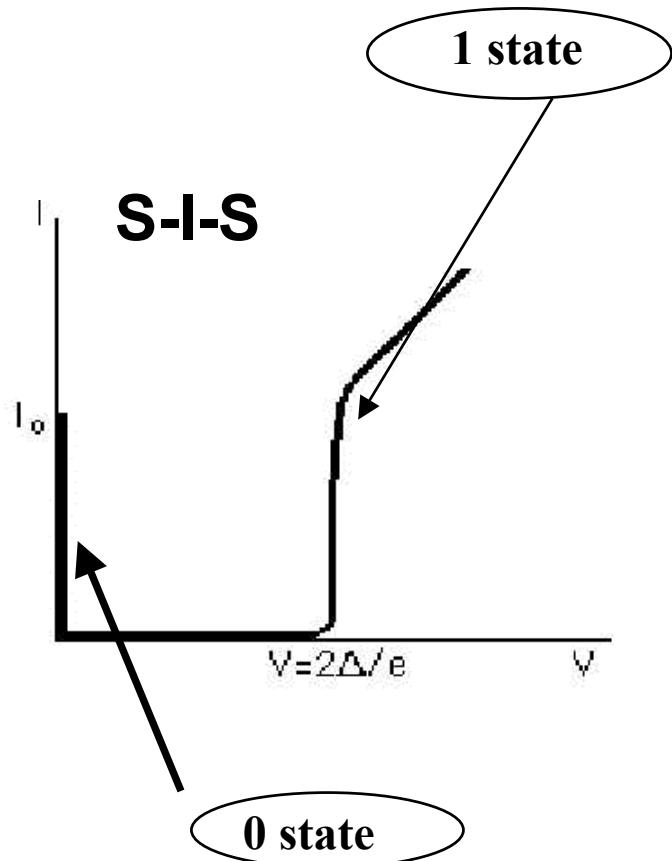

1. Underdamped Junctions $\beta_c \gg 1$
2. Can use unshunted junctions
3. Must induce a “switch” from 0 state to 1 state by changing the critical current
4. Once in the 1 state, must drive critical current to zero to reset

Transient Response for $\beta_c \gg 1$

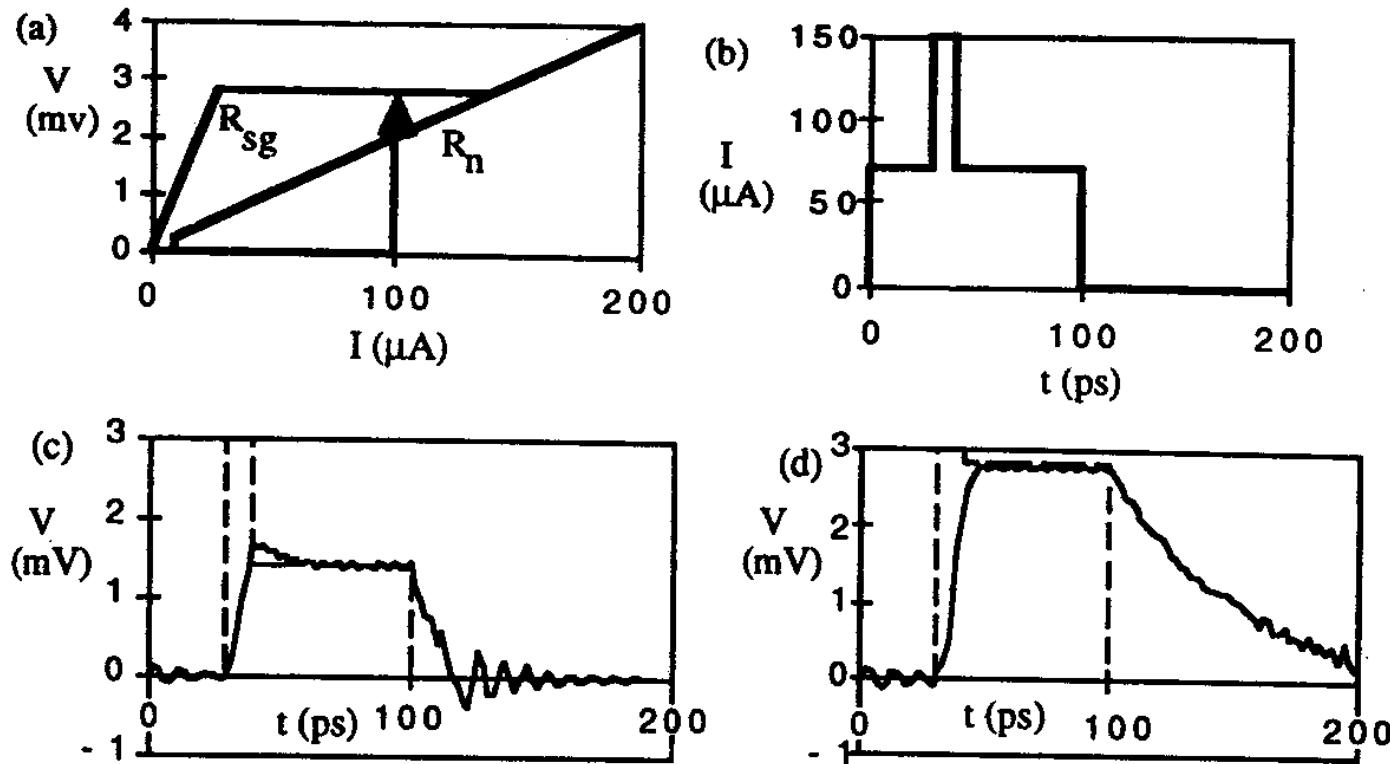

$$I_c = 100 \text{ } \mu\text{A}, R_n = 20 \Omega, R_{sg} = 100 \Omega, V_g = 2.8 \text{ mV}, \text{ and } C = 0.5 \text{ pF}$$


From A. M. Kadin, Introduction to Superconducting Circuits

Massachusetts Institute of Technology

6.763 2003 Lecture 16



Voltage-State Switching

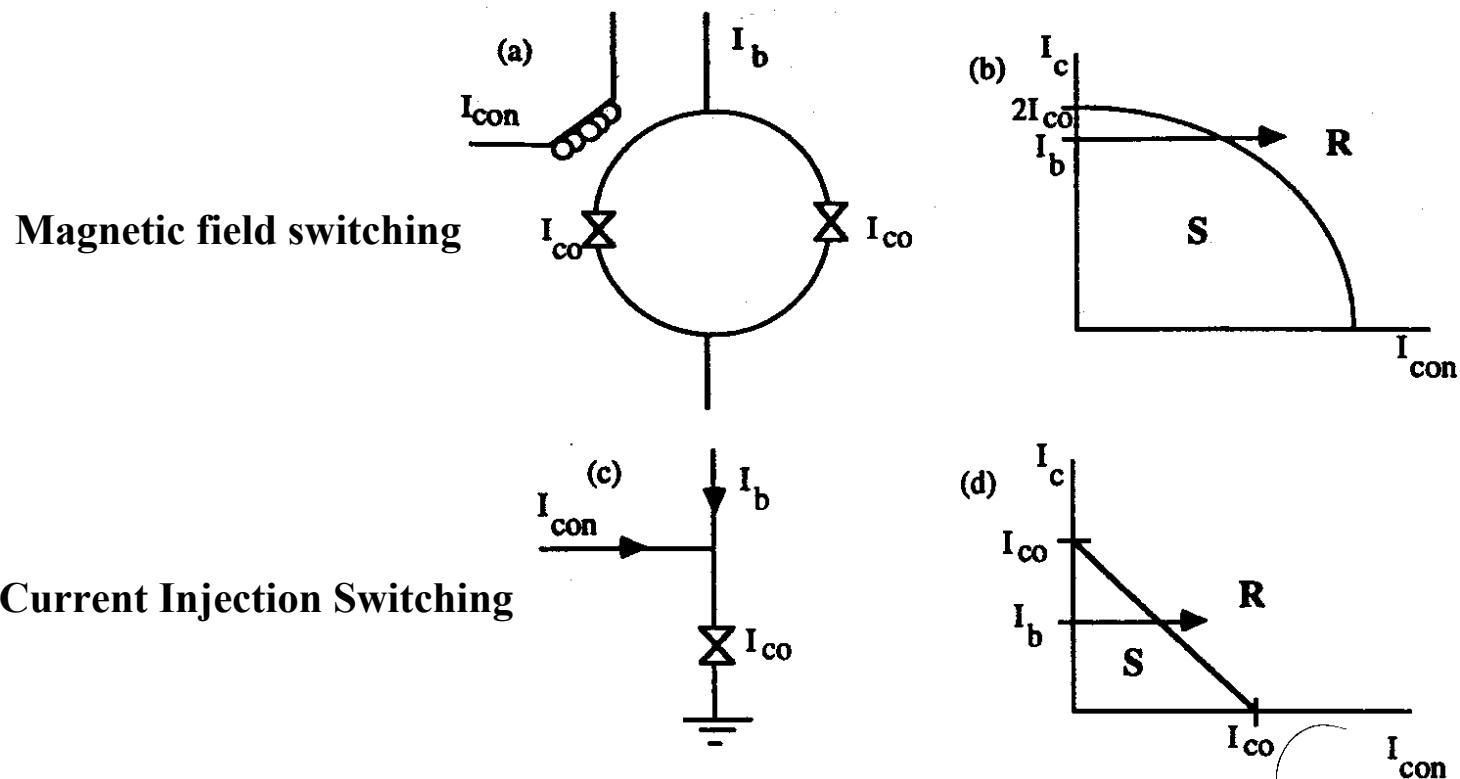


From A. M. Kadin, Introduction to Superconducting Circuits

Massachusetts Institute of Technology
6.763 2003 Lecture 16





Voltage-State Logic Gates

Magnetic Coupling of signals

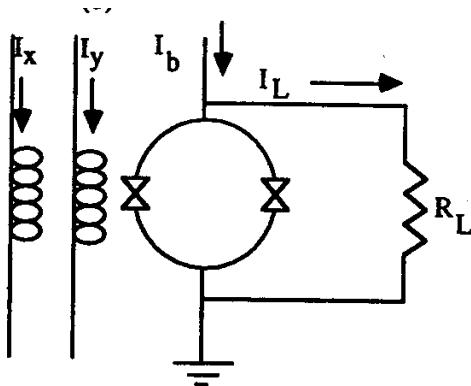

Current coupling of signals

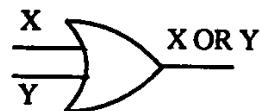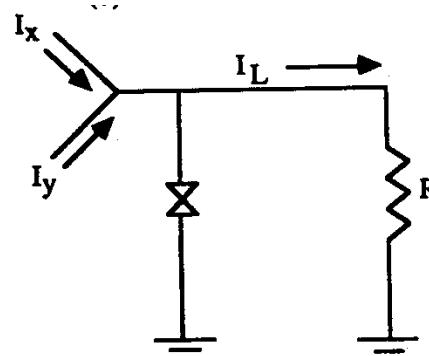


$$I_X + I_b > 2I_c \quad \text{or} \quad I_Y + I_b > 2I_c$$





$$I_X + I_Y + I_b > 2I_c$$

Voltage-State Memory

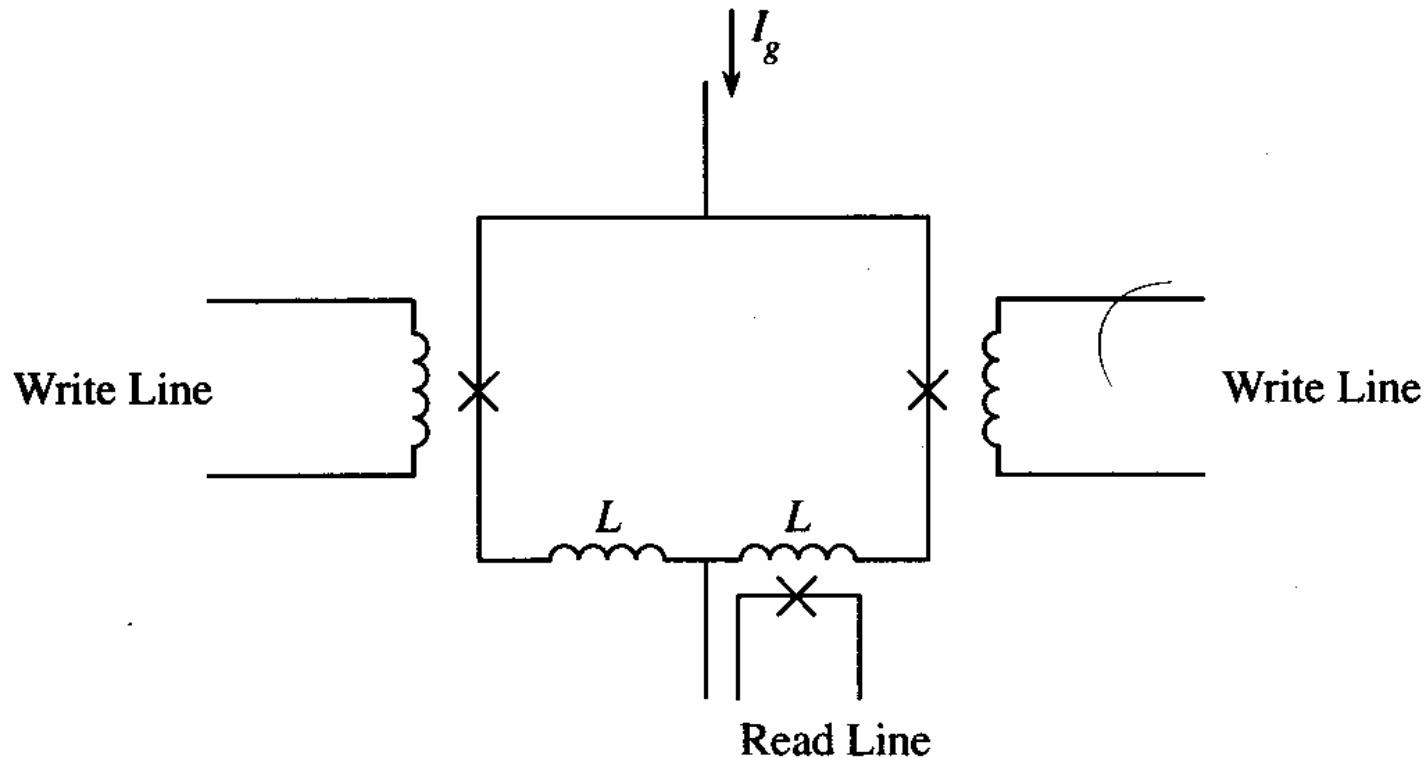

3. Single Flux Quantum (SFQ) Logic

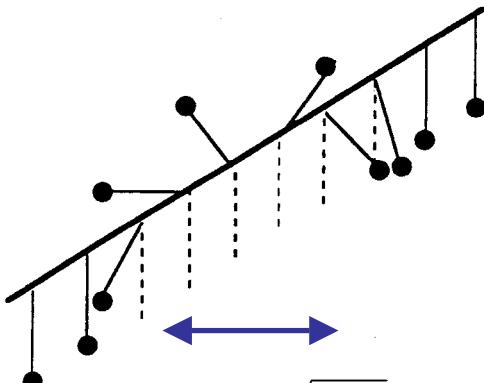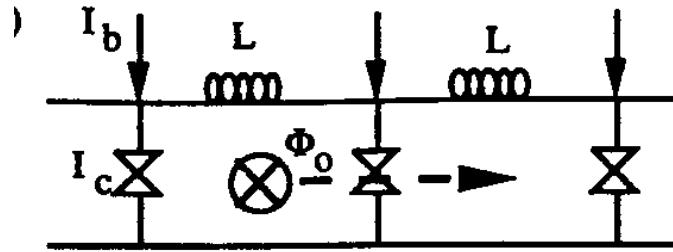


SFQ Pulse (a vortex)

$$\Lambda = \sqrt{\frac{L_J}{L}}$$

Size of a vortex in a parallel array,

SFQ pulse confined to one cell $\Lambda = 1$

Transient Response for $\beta_c \ll 1$

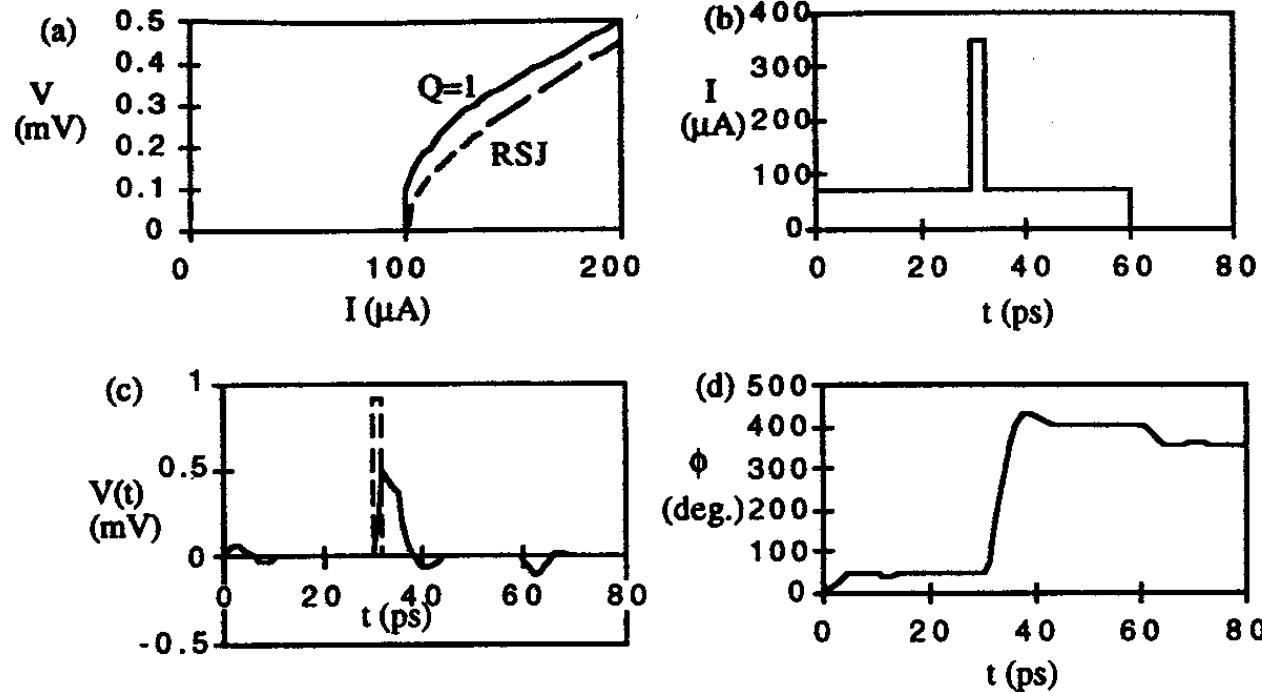

$$I_c = 100 \text{ } \mu\text{A}, R_{sh} = 2.6 \Omega, V_g = 2.8 \text{ mV}, C = 0.5 \text{ pF}, \text{ and } L_J/L = 1$$


From A. M. Kadin, Introduction to Superconducting Circuits

Massachusetts Institute of Technology

6.763 2003 Lecture 16



SFQ: The Josephson Transmission Line

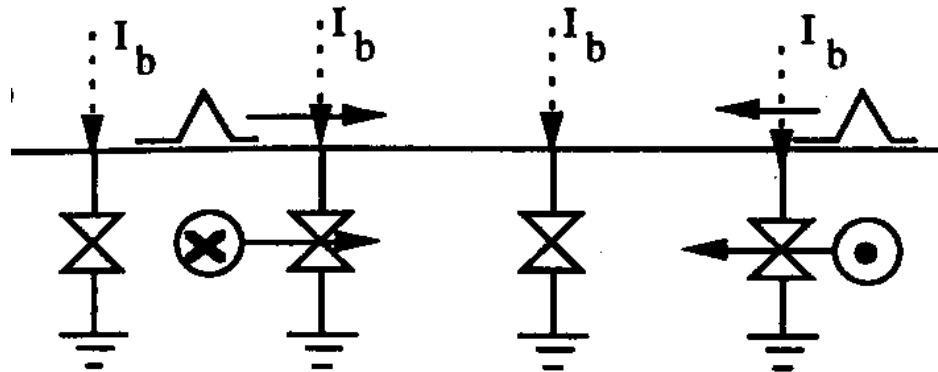


Vortex (fluxon) moving to the right

Anit-Vortex (anti-fluxon) moving to the left

From A. M. Kadin, Introduction to Superconducting Circuits




SFQ Splitter

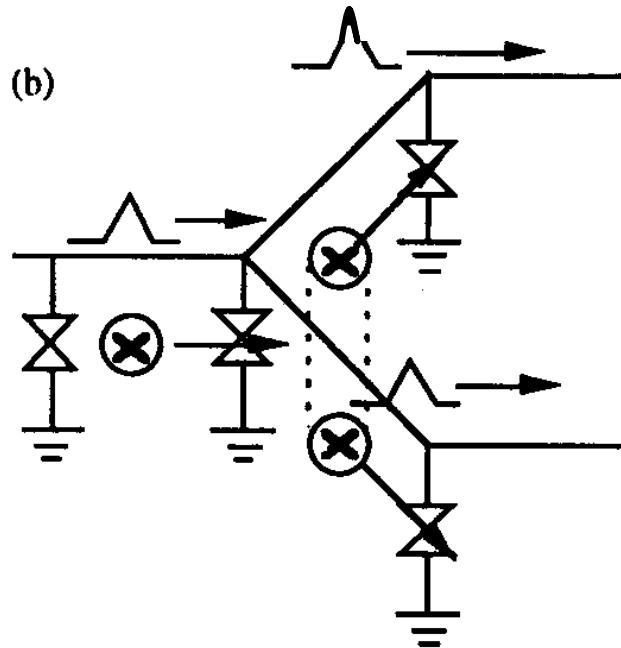

From A. M. Kadin, Introduction to Superconducting Circuits

SFQ Memory Cell

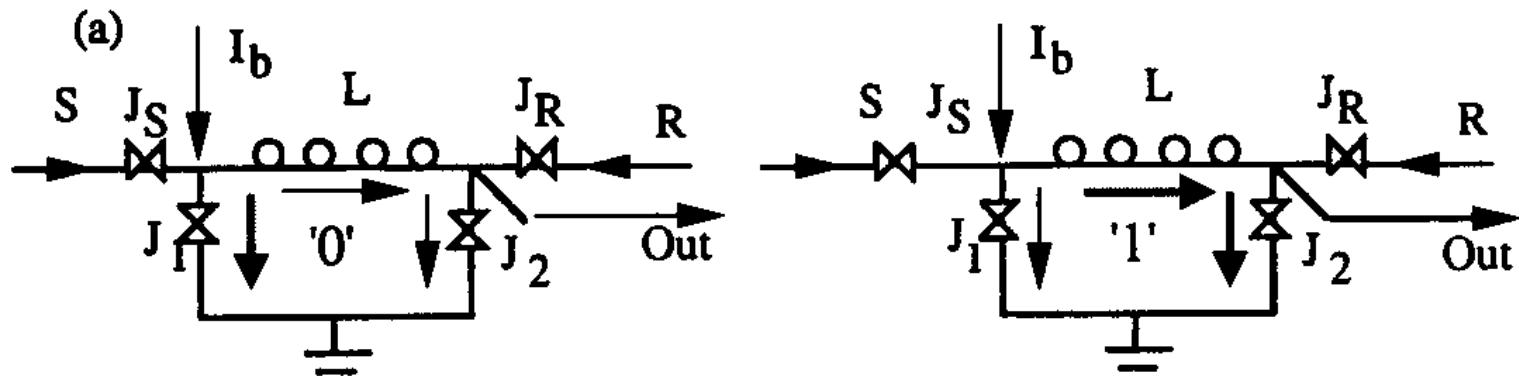


0 = No flux stored

1 = flux stored


From A. M. Kadin, Introduction to Superconducting Circuits

SFQ Logic Gates

OR

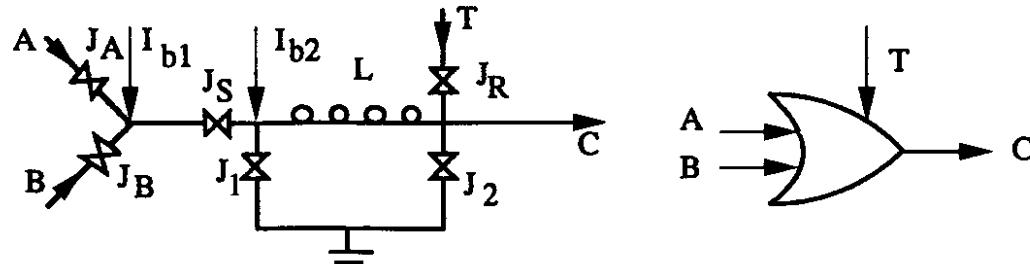

AND

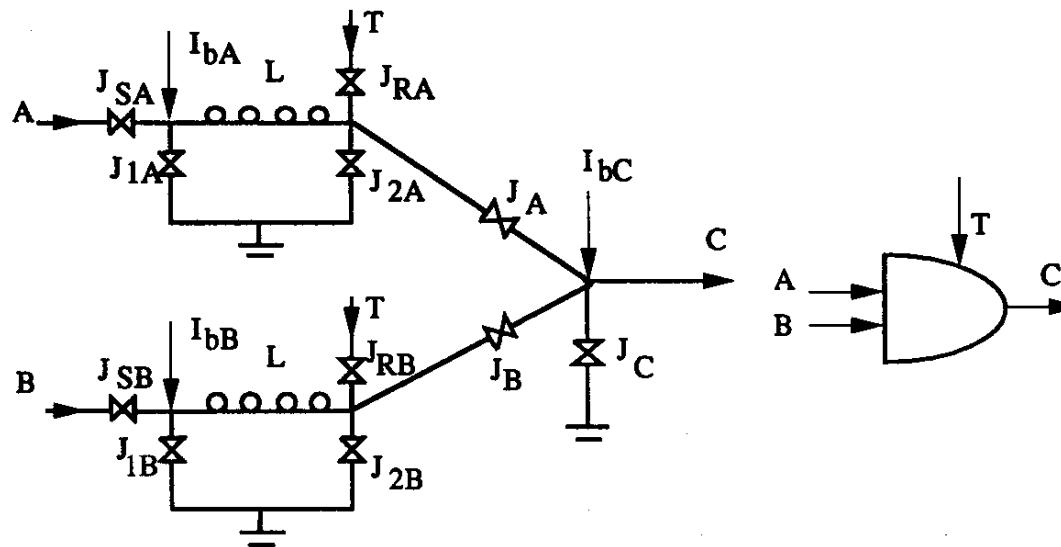

From A. M. Kadin, Introduction to Superconducting Circuits

Massachusetts Institute of Technology

6.763 2003 Lecture 16

