

EE101: ADC and DAC circuits



M. B. Patil

`mbpatil@ee.iitb.ac.in`

`www.ee.iitb.ac.in/~sequel`

Department of Electrical Engineering
Indian Institute of Technology Bombay

Introduction

- * Real signals (e.g., a voltage measured with a thermocouple or a speech signal recorded with a microphone) are analog quantities, varying continuously with time.

Introduction


- * Real signals (e.g., a voltage measured with a thermocouple or a speech signal recorded with a microphone) are analog quantities, varying continuously with time.
- * Digital format offers several advantages: digital signal processing, storage, use of computers, robust transmission, etc.


- * Real signals (e.g., a voltage measured with a thermocouple or a speech signal recorded with a microphone) are analog quantities, varying continuously with time.
- * Digital format offers several advantages: digital signal processing, storage, use of computers, robust transmission, etc.
- * An ADC (Analog-to-Digital Converter) is used to convert an analog signal to the digital format.

- * Real signals (e.g., a voltage measured with a thermocouple or a speech signal recorded with a microphone) are analog quantities, varying continuously with time.
- * Digital format offers several advantages: digital signal processing, storage, use of computers, robust transmission, etc.
- * An ADC (Analog-to-Digital Converter) is used to convert an analog signal to the digital format.
- * The reverse conversion (from digital to analog) is also required. For example, music stored in a DVD in digital format must be converted to an analog voltage for playing out on a speaker.


- * Real signals (e.g., a voltage measured with a thermocouple or a speech signal recorded with a microphone) are analog quantities, varying continuously with time.
- * Digital format offers several advantages: digital signal processing, storage, use of computers, robust transmission, etc.
- * An ADC (Analog-to-Digital Converter) is used to convert an analog signal to the digital format.
- * The reverse conversion (from digital to analog) is also required. For example, music stored in a DVD in digital format must be converted to an analog voltage for playing out on a speaker.
- * A DAC (Digital-to-Analog Converter) is used to convert a digital signal to the analog format.

DAC

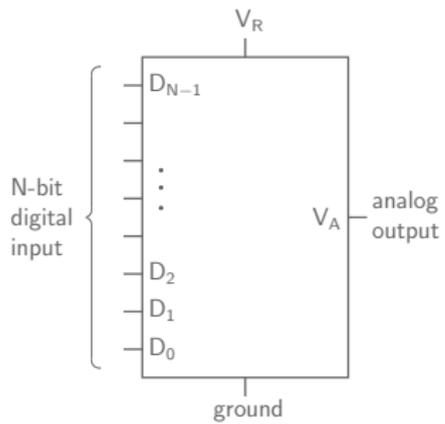


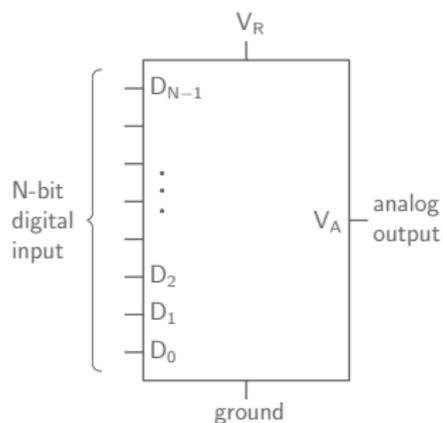

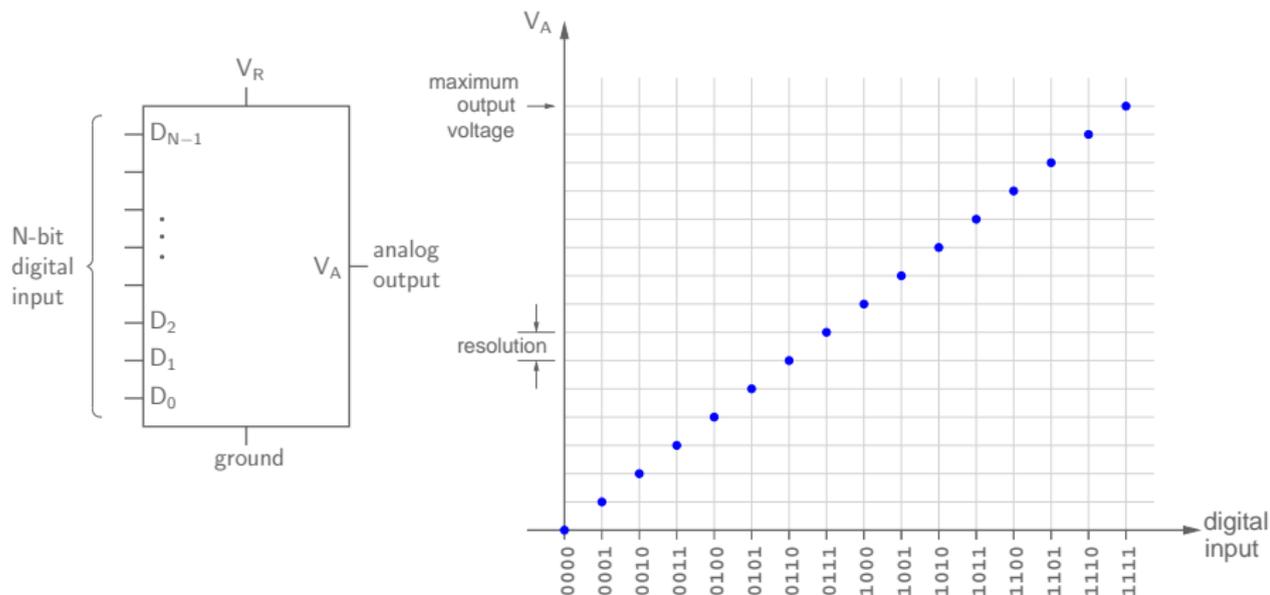- * For a 4-bit DAC, with input $S_3S_2S_1S_0$, the output voltage is $V_A = K [(S_3 \times 2^3) + (S_2 \times 2^2) + (S_1 \times 2^1) + (S_0 \times 2^0)]$.
In general, $V_A = K \sum_0^{N-1} S_k 2^k$.





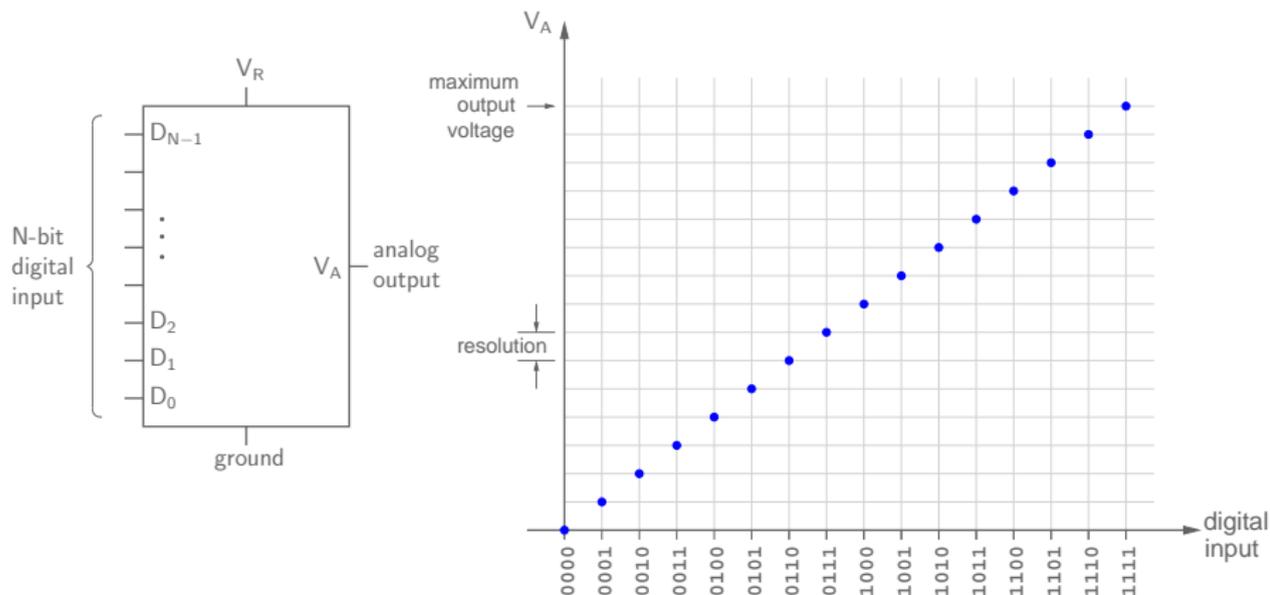- * For a 4-bit DAC, with input $S_3S_2S_1S_0$, the output voltage is $V_A = K [(S_3 \times 2^3) + (S_2 \times 2^2) + (S_1 \times 2^1) + (S_0 \times 2^0)]$.
In general, $V_A = K \sum_0^{N-1} S_k 2^k$.




- * For a 4-bit DAC, with input $S_3S_2S_1S_0$, the output voltage is $V_A = K [(S_3 \times 2^3) + (S_2 \times 2^2) + (S_1 \times 2^1) + (S_0 \times 2^0)]$.
In general, $V_A = K \sum_{k=0}^{N-1} S_k 2^k$.
- * K is proportional to the reference voltage V_R . Its value depends on how the DAC is implemented.

DAC using binary-weighted resistors

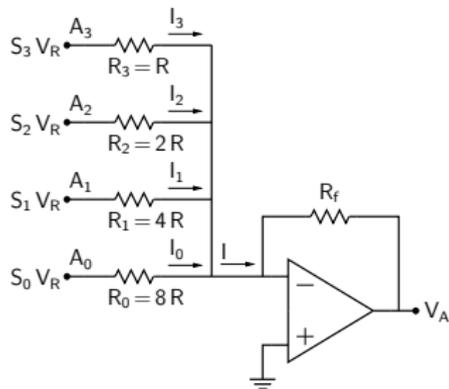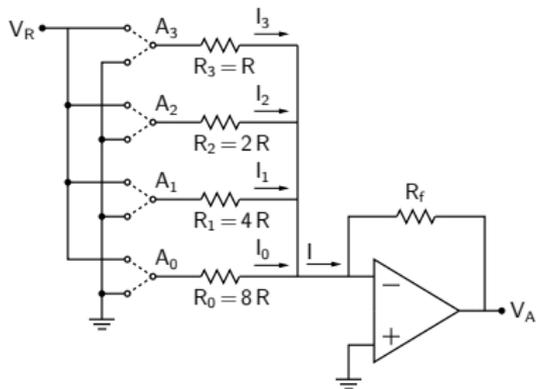


DAC using binary-weighted resistors

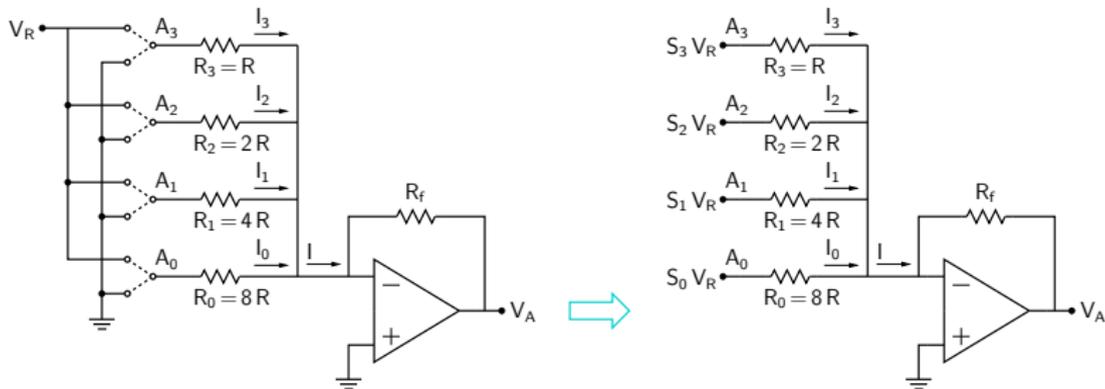


* If the input bit S_k is 1, A_k gets connected to V_R ; else, it gets connected to ground.

DAC using binary-weighted resistors

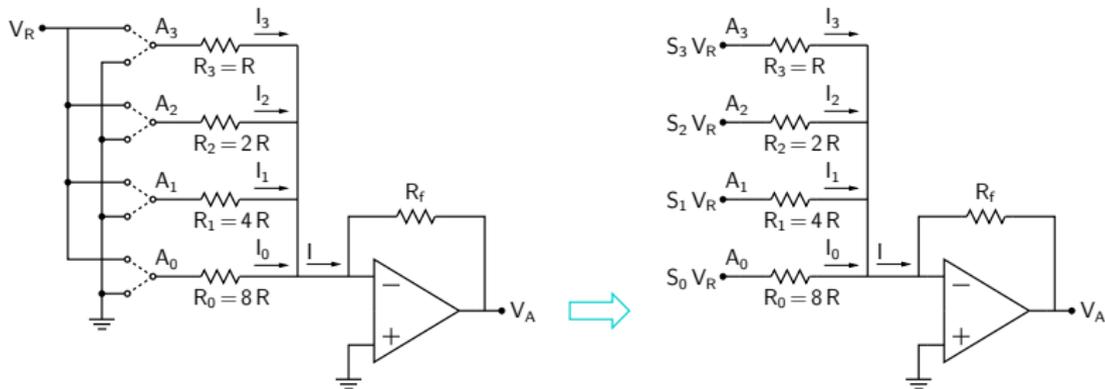

- * If the input bit S_k is 1, A_k gets connected to V_R ; else, it gets connected to ground.
→ $V(A_k) = S_k \times V_R$.

DAC using binary-weighted resistors

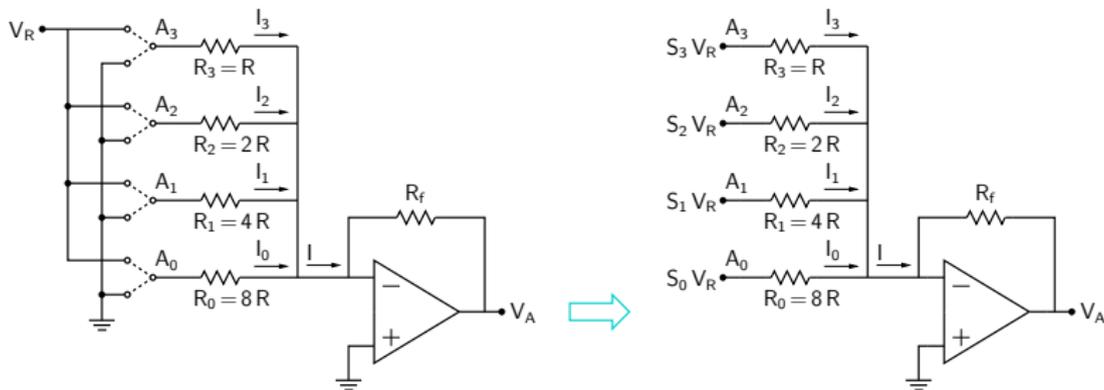


- * If the input bit S_k is 1, A_k gets connected to V_R ; else, it gets connected to ground.
 $\rightarrow V(A_k) = S_k \times V_R$.

- * Since the inverting terminal of the Op Amp is at virtual ground,

$$I_k = \frac{V(A_k) - 0}{R_k} = \frac{S_k V_R}{R_k}.$$

DAC using binary-weighted resistors

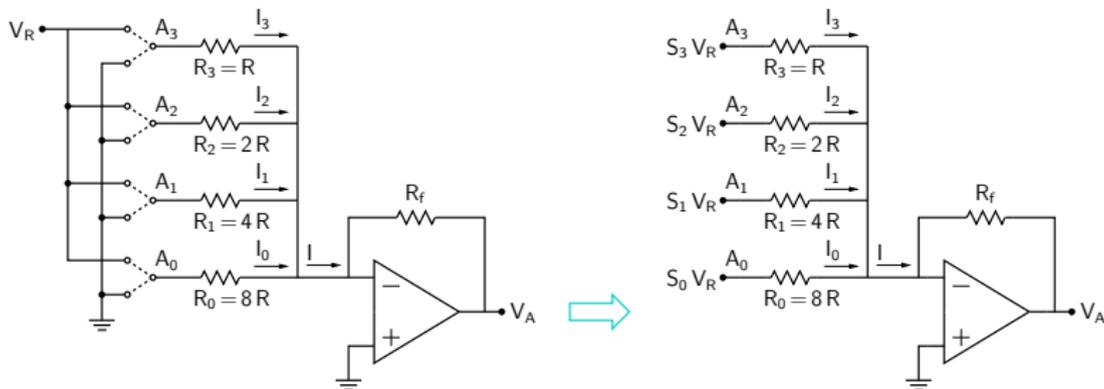


- * If the input bit S_k is 1, A_k gets connected to V_R ; else, it gets connected to ground.
 $\rightarrow V(A_k) = S_k \times V_R$.

- * Since the inverting terminal of the Op Amp is at virtual ground,

$$I_k = \frac{V(A_k) - 0}{R_k} = \frac{S_k V_R}{R_k}.$$

- * Using $R_k = 2^{N-1} R / 2^k$, we get $I = \frac{V_R}{2^{N-1} R} \sum_0^{N-1} S_k \times 2^k$ ($N = 4$ here).

DAC using binary-weighted resistors

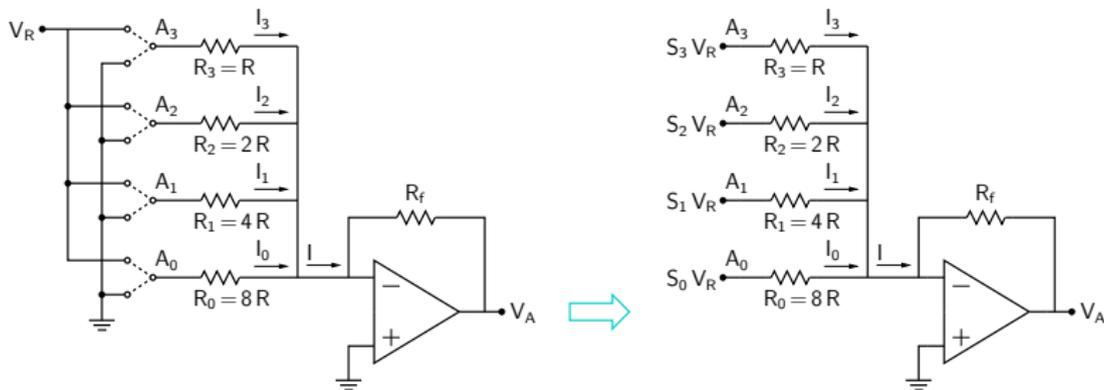

- * If the input bit S_k is 1, A_k gets connected to V_R ; else, it gets connected to ground.
 $\rightarrow V(A_k) = S_k \times V_R$.


- * Since the inverting terminal of the Op Amp is at virtual ground,

$$I_k = \frac{V(A_k) - 0}{R_k} = \frac{S_k V_R}{R_k}.$$


- * Using $R_k = 2^{N-1} R / 2^k$, we get $I = \frac{V_R}{2^{N-1} R} \sum_0^{N-1} S_k \times 2^k$ ($N = 4$ here).

- * The output voltage is $V_o = -R_f I = -V_R \frac{R_f}{2^{N-1} R} \sum_0^{N-1} S_k \times 2^k$.

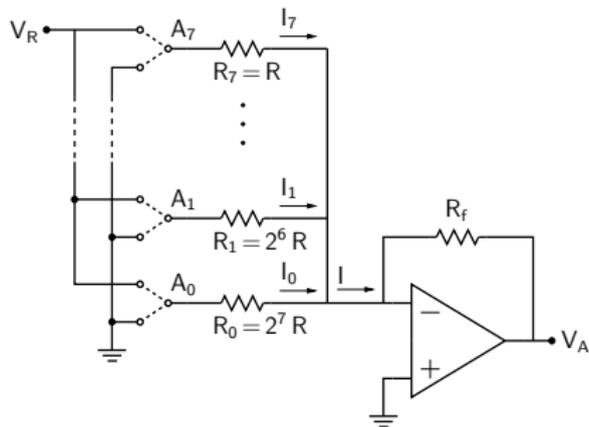DAC using binary-weighted resistors: Example (from Gopalan)




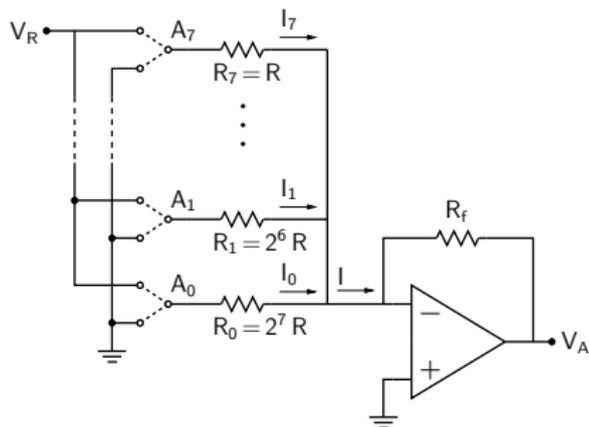DAC using binary-weighted resistors: Example (from Gopalan)



- * Consider an 8-bit DAC with $V_R = 5\text{ V}$. What is the smallest value of R which will limit the current drawn from the supply (V_R) to 10 mA?

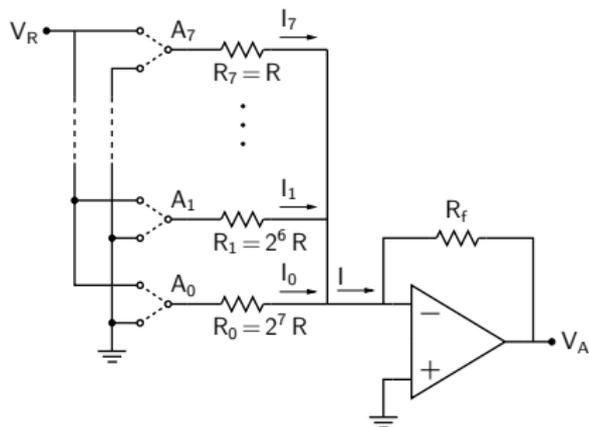
DAC using binary-weighted resistors: Example (from Gopalan)



- * Consider an 8-bit DAC with $V_R = 5\text{ V}$. What is the smallest value of R which will limit the current drawn from the supply (V_R) to 10 mA ?

Maximum current is drawn from V_R when the input is 1111 1111.

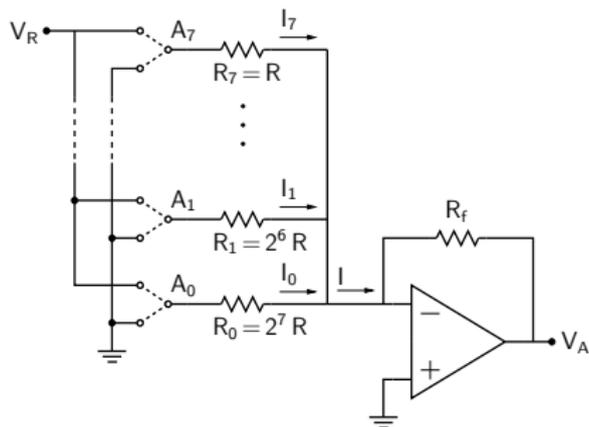DAC using binary-weighted resistors: Example (from Gopalan)




- * Consider an 8-bit DAC with $V_R = 5\text{ V}$. What is the smallest value of R which will limit the current drawn from the supply (V_R) to 10 mA?

Maximum current is drawn from V_R when the input is 1111 1111.

→ All nodes A_0 to A_7 get connected to V_R .

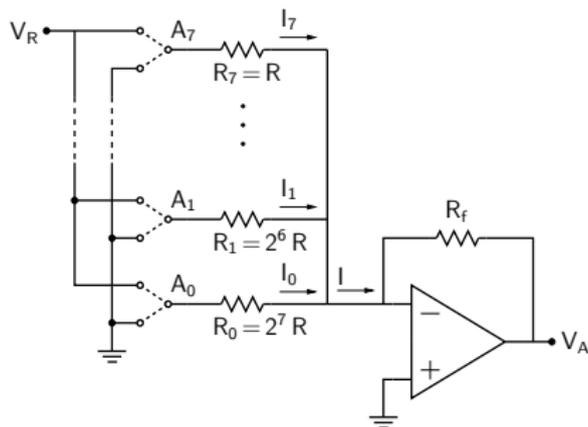DAC using binary-weighted resistors: Example (from Gopalan)




- * Consider an 8-bit DAC with $V_R = 5\text{ V}$. What is the smallest value of R which will limit the current drawn from the supply (V_R) to 10 mA?

Maximum current is drawn from V_R when the input is 1111 1111.

→ All nodes A_0 to A_7 get connected to V_R .

$$\begin{aligned} \rightarrow 10\text{ mA} &= \frac{V_R}{R} + \frac{V_R}{2R} + \dots + \frac{V_R}{2^7 R} = \frac{1}{2^7} \frac{V_R}{R} (2^0 + 2^1 + \dots + 2^7) \\ &= \frac{1}{2^7} \frac{V_R}{R} (2^8 - 1) = \frac{255}{128} \frac{V_R}{R} \end{aligned}$$

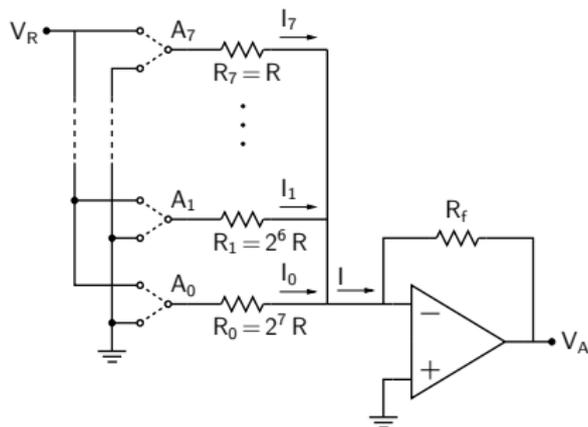DAC using binary-weighted resistors: Example (from Gopalan)



- * Consider an 8-bit DAC with $V_R = 5\text{ V}$. What is the smallest value of R which will limit the current drawn from the supply (V_R) to 10 mA?

Maximum current is drawn from V_R when the input is 1111 1111.


→ All nodes A_0 to A_7 get connected to V_R .

$$\rightarrow 10\text{ mA} = \frac{V_R}{R} + \frac{V_R}{2R} + \dots + \frac{V_R}{2^7 R} = \frac{1}{2^7} \frac{V_R}{R} (2^0 + 2^1 + \dots + 2^7)$$


$$= \frac{1}{2^7} \frac{V_R}{R} (2^8 - 1) = \frac{255}{128} \frac{V_R}{R}$$

$$\rightarrow R_{\min} = \frac{5\text{ V}}{10\text{ mA}} \times \frac{255}{128} = 996\ \Omega.$$

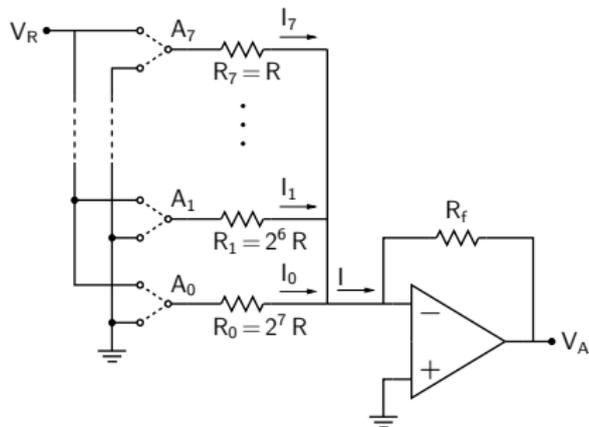DAC using binary-weighted resistors: Example (from Gopalan)




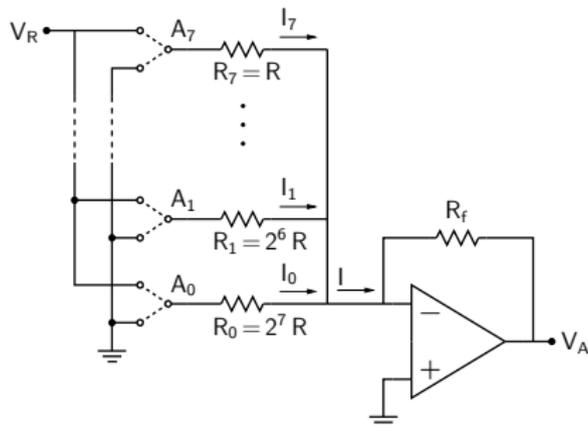DAC using binary-weighted resistors: Example (from Gopalan)



- * If $R_f = R$, what is the resolution (i.e., ΔV_A corresponding to the input LSB changing from 0 to 1 with other input bits constant)?

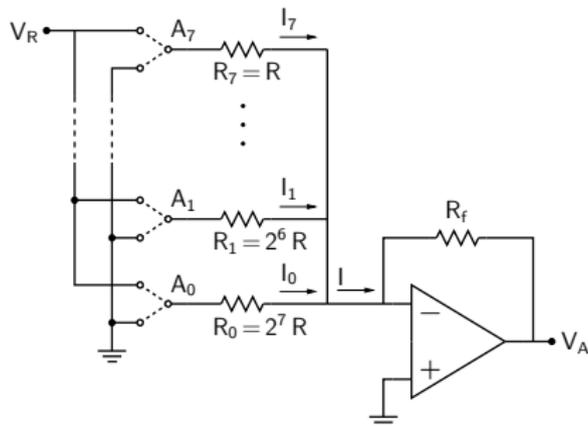
DAC using binary-weighted resistors: Example (from Gopalan)



- * If $R_f = R$, what is the resolution (i.e., ΔV_A corresponding to the input LSB changing from 0 to 1 with other input bits constant)?

$$V_A = -V_R \frac{R_f}{2^{N-1}R} \left[S_7 2^7 + \dots + S_1 2^1 + S_0 2^0 \right]$$

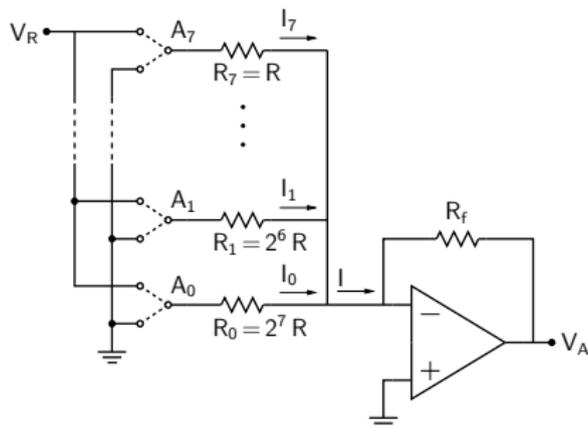DAC using binary-weighted resistors: Example (from Gopalan)




- * If $R_f = R$, what is the resolution (i.e., ΔV_A corresponding to the input LSB changing from 0 to 1 with other input bits constant)?


$$V_A = -V_R \frac{R_f}{2^{N-1}R} \left[S_7 2^7 + \dots + S_1 2^1 + S_0 2^0 \right]$$

$$\rightarrow \Delta V_A = \frac{V_R}{2^{N-1}} \frac{R_f}{R} = \frac{5\text{ V}}{2^{8-1}} \times 1 = \frac{5}{128} = 0.0391\text{ V.}$$

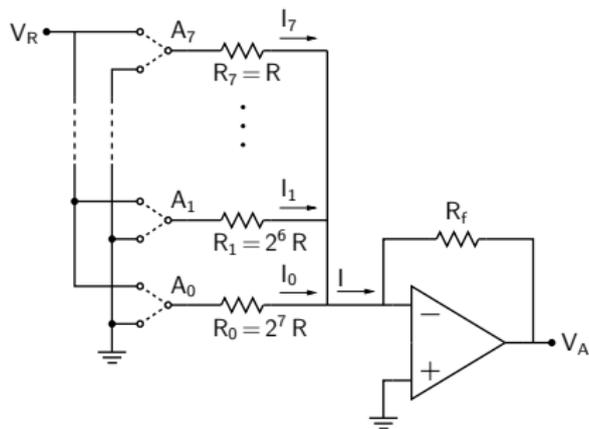DAC using binary-weighted resistors: Example (from Gopalan)




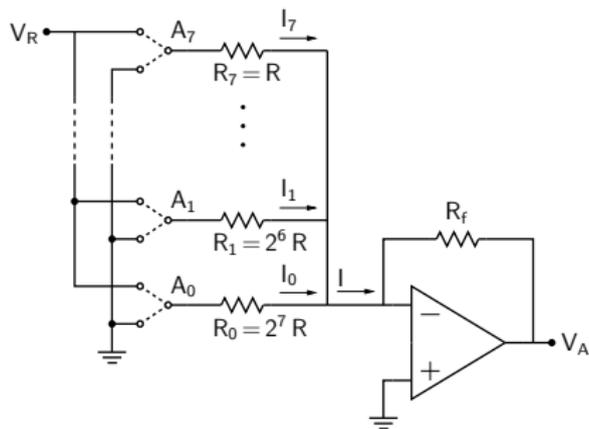DAC using binary-weighted resistors: Example (from Gopalan)



- * What is the maximum output voltage (in magnitude)?

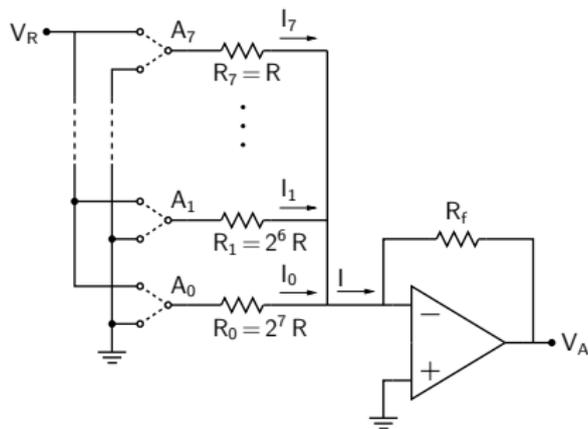
DAC using binary-weighted resistors: Example (from Gopalan)



- * What is the maximum output voltage (in magnitude)?

$$V_A = -\frac{V_R}{2^{N-1}} \frac{R_f}{R} [S_7 2^7 + \dots + S_1 2^1 + S_0 2^0].$$

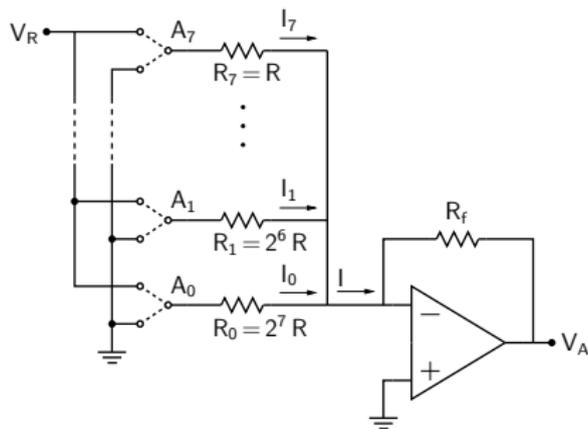DAC using binary-weighted resistors: Example (from Gopalan)




- * What is the maximum output voltage (in magnitude)?

$$V_A = -\frac{V_R}{2^{N-1}} \frac{R_f}{R} [S_7 2^7 + \dots + S_1 2^1 + S_0 2^0].$$

Maximum V_A (in magnitude) is obtained when the input is 1111 1111.

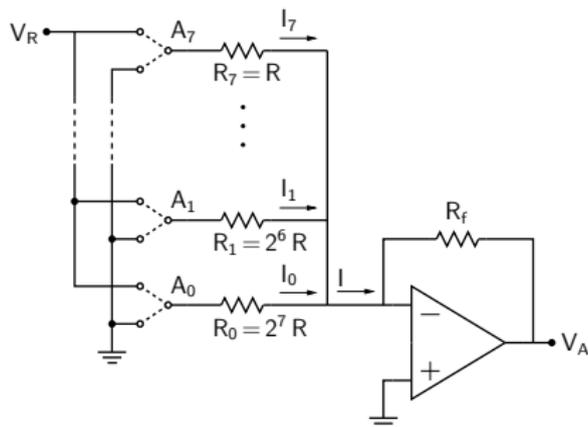DAC using binary-weighted resistors: Example (from Gopalan)




- * What is the maximum output voltage (in magnitude)?

$$V_A = -\frac{V_R}{2^{N-1}} \frac{R_f}{R} [S_7 2^7 + \dots + S_1 2^1 + S_0 2^0].$$


Maximum V_A (in magnitude) is obtained when the input is 1111 1111.

$$|V_A|^{\max} = \frac{5}{128} \times 1 \times [2^0 + 2^1 + \dots + 2^7] = \frac{5}{128} \times (2^8 - 1) = 5 \times \frac{255}{128} = 9.961 \text{ V}.$$

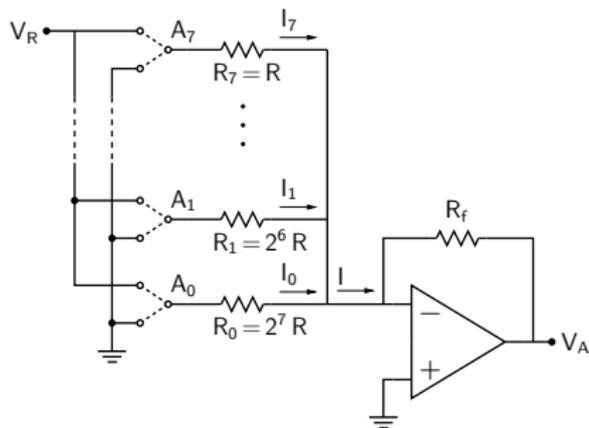DAC using binary-weighted resistors: Example (from Gopalan)




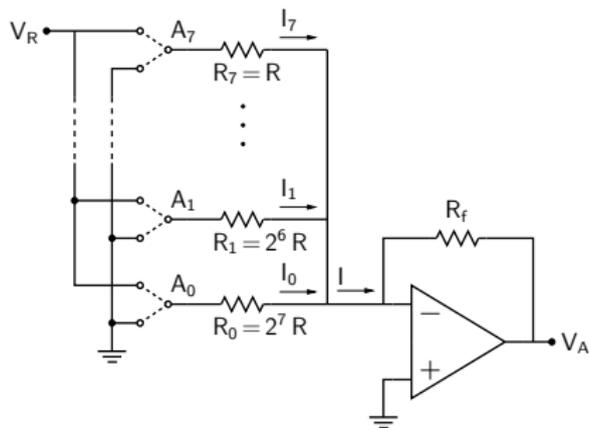DAC using binary-weighted resistors: Example (from Gopalan)



* Find the output voltage corresponding to the input 1010 1101.

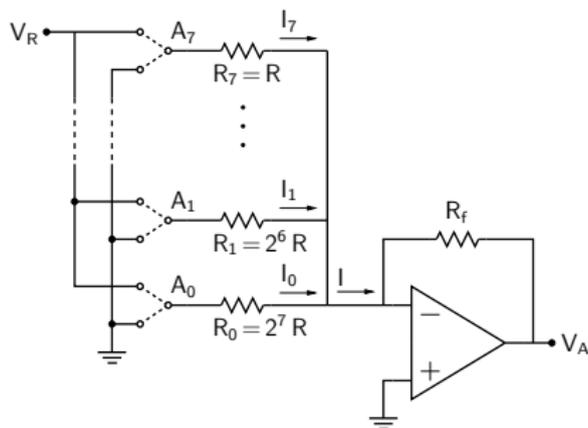
DAC using binary-weighted resistors: Example (from Gopalan)



- * Find the output voltage corresponding to the input 1010 1101.

$$V_A = -\frac{V_R}{2^{N-1}} \frac{R_f}{R} [S_7 2^7 + \dots + S_1 2^1 + S_0 2^0].$$

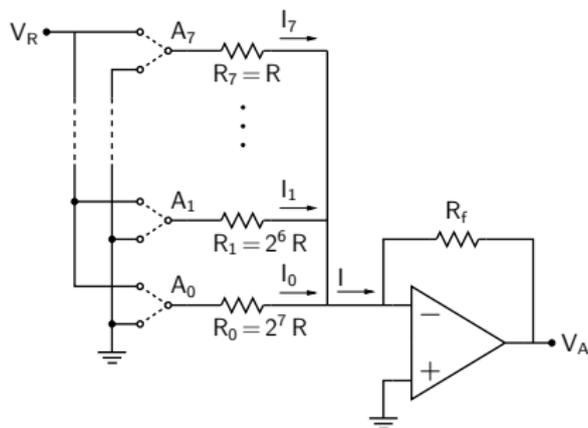
DAC using binary-weighted resistors: Example (from Gopalan)




- * Find the output voltage corresponding to the input 1010 1101.

$$\begin{aligned} V_A &= -\frac{V_R}{2^{N-1}} \frac{R_f}{R} \left[S_7 2^7 + \cdots + S_1 2^1 + S_0 2^0 \right]. \\ &= -\frac{5}{128} \times 1 \times \left[2^7 + 2^5 + 2^3 + 2^2 + 2^0 \right] = -5 \times \frac{173}{128} = -6.758 \text{ V}. \end{aligned}$$

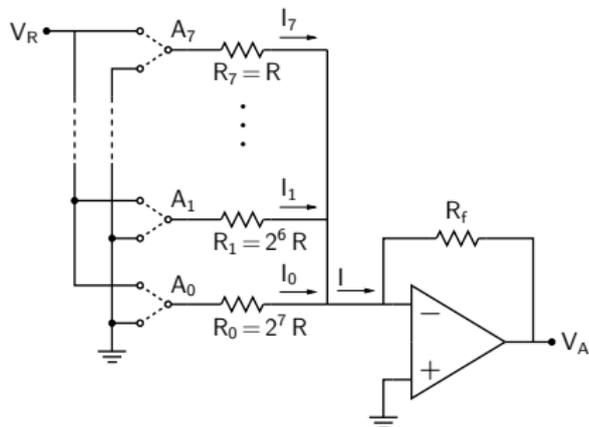DAC using binary-weighted resistors: Example (from Gopalan)




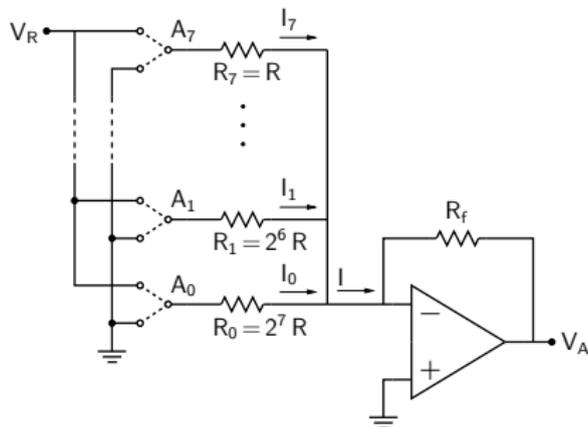DAC using binary-weighted resistors: Example (from Gopalan)



- * If the resistors are specified to have a tolerance of 1%, what is the range of $|V_A|$ corresponding to input 1111 1111?

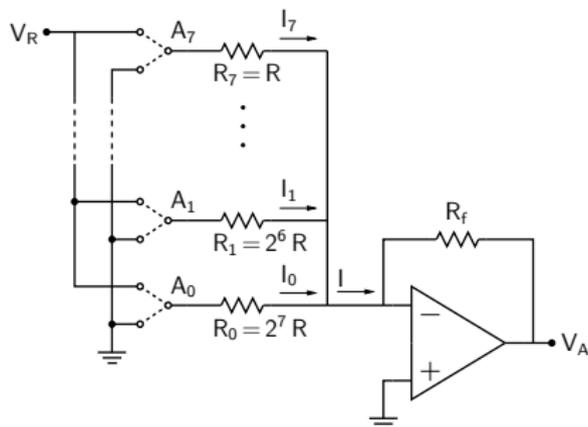
DAC using binary-weighted resistors: Example (from Gopalan)



- * If the resistors are specified to have a tolerance of 1%, what is the range of $|V_A|$ corresponding to input 1111 1111?

$|V_A|$ is maximum when (a) currents I_0, I_1 , etc. assume their maximum values, with $R_k = R_k^0 \times (1 - 0.01)$ and (b) R_f is maximum, $R_f = R_f^0 \times (1 + 0.01)$.
(The superscript '0' denotes nominal value.)

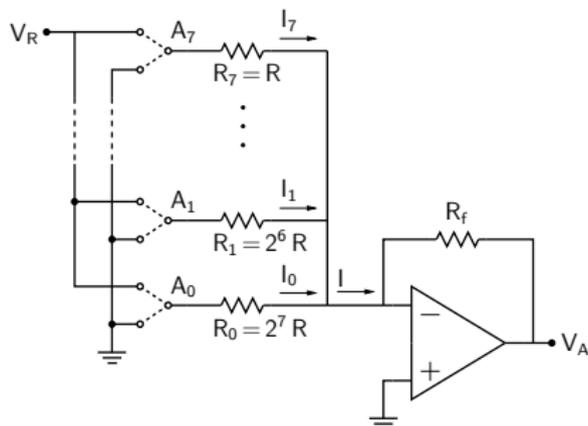DAC using binary-weighted resistors: Example (from Gopalan)




- * If the resistors are specified to have a tolerance of 1%, what is the range of $|V_A|$ corresponding to input 1111 1111?

$|V_A|$ is maximum when (a) currents I_0, I_1 , etc. assume their maximum values, with $R_k = R_k^0 \times (1 - 0.01)$ and (b) R_f is maximum, $R_f = R_f^0 \times (1 + 0.01)$.
(The superscript '0' denotes nominal value.)

$$\rightarrow |V_A|_{11111111}^{\max} = V_R \times \frac{255}{128} \times \frac{R_f}{R} \Big|_{\max} = 5 \times \frac{255}{128} \times \frac{1.01}{0.99} = 10.162 \text{ V.}$$

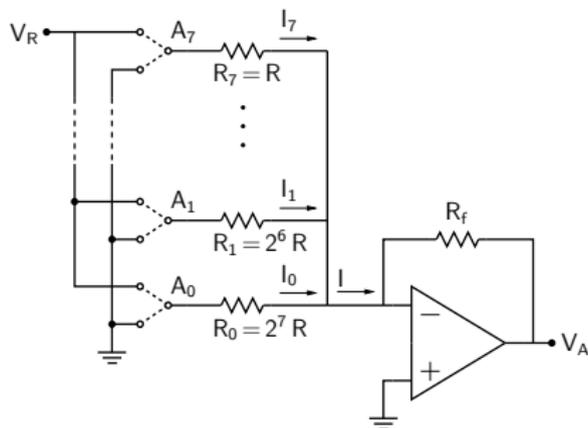DAC using binary-weighted resistors: Example (from Gopalan)




- * If the resistors are specified to have a tolerance of 1%, what is the range of $|V_A|$ corresponding to input 1111 1111?

$|V_A|$ is maximum when (a) currents I_0, I_1 , etc. assume their maximum values, with $R_k = R_k^0 \times (1 - 0.01)$ and (b) R_f is maximum, $R_f = R_f^0 \times (1 + 0.01)$.
(The superscript '0' denotes nominal value.)


$$\rightarrow |V_A|_{11111111}^{\max} = V_R \times \frac{255}{128} \times \frac{R_f}{R} \Big|_{\max} = 5 \times \frac{255}{128} \times \frac{1.01}{0.99} = 10.162 \text{ V.}$$

$$\text{Similarly, } |V_A|_{11111111}^{\min} = 5 \times \frac{255}{128} \times \frac{0.99}{1.01} = 9.764 \text{ V.}$$

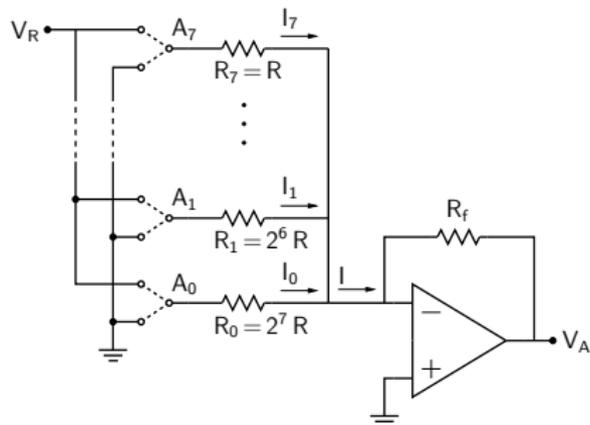DAC using binary-weighted resistors: Example (from Gopalan)




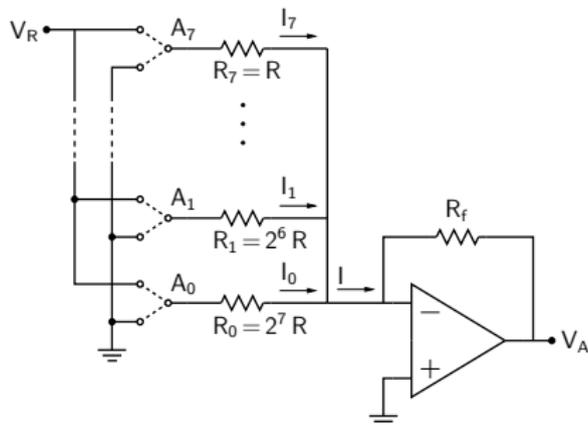DAC using binary-weighted resistors: Example (from Gopalan)




- * ΔV_A for input 1111 1111 = $10.162 - 9.764 \approx 0.4 \text{ V}$ which is larger than the resolution (0.039 V) of the DAC. This situation is not acceptable.

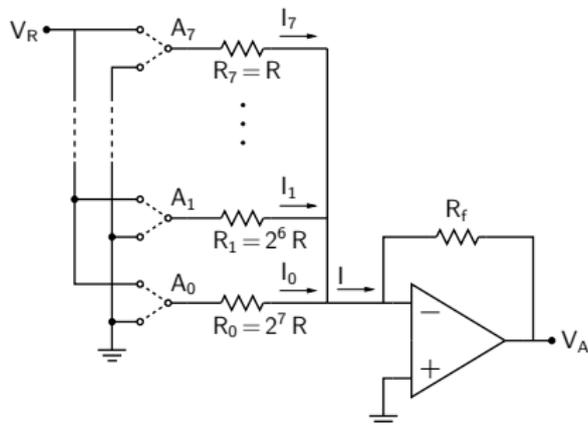DAC using binary-weighted resistors: Example (from Gopalan)




- * ΔV_A for input 1111 1111 = $10.162 - 9.764 \approx 0.4 \text{ V}$ which is larger than the resolution (0.039 V) of the DAC. This situation is not acceptable.
- * The output voltage variation can be reduced by using resistors with a smaller tolerance. However, it is difficult to fabricate an IC with widely varying resistance values (from R to $2^{N-1}R$) and each with a small enough tolerance.

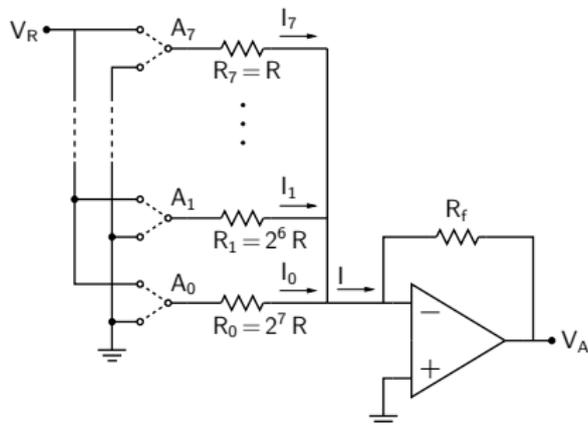DAC using binary-weighted resistors: Example (from Gopalan)




- * ΔV_A for input 1111 1111 = $10.162 - 9.764 \approx 0.4 \text{ V}$ which is larger than the resolution (0.039 V) of the DAC. This situation is not acceptable.
- * The output voltage variation can be reduced by using resistors with a smaller tolerance. However, it is difficult to fabricate an IC with widely varying resistance values (from R to $2^{N-1}R$) and each with a small enough tolerance.
→ use $R - 2R$ ladder network instead.

R-2R ladder network

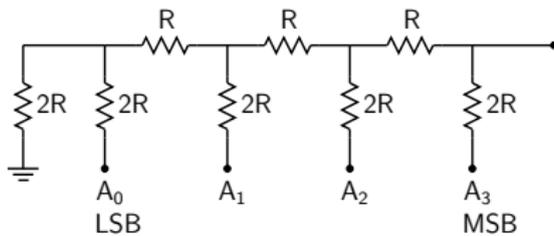


Node A_k is connected to V_R if input bit S_k is 1; else, it is connected to ground.

R-2R ladder network

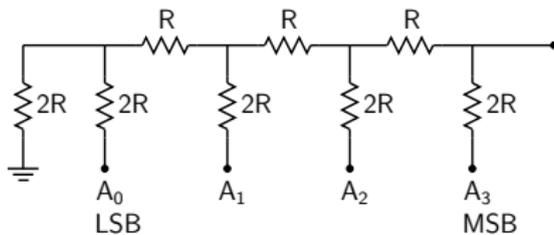


Node A_k is connected to V_R if input bit S_k is 1; else, it is connected to ground.


The original network is equivalent to

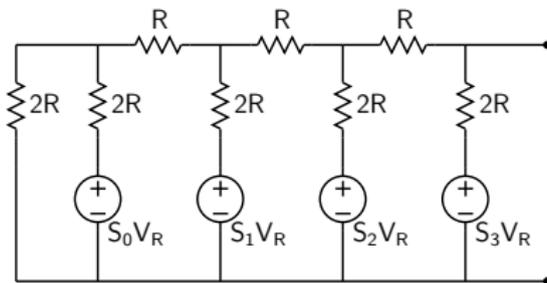


R-2R ladder network: Thevenin resistance

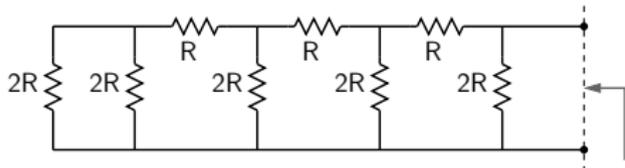


R-2R ladder network: Thevenin resistance

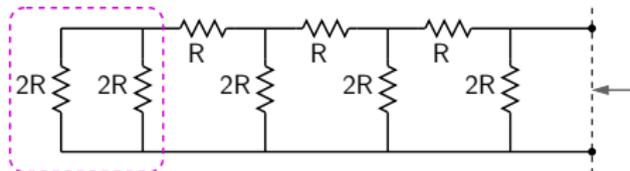


R-2R ladder network: Thevenin resistance

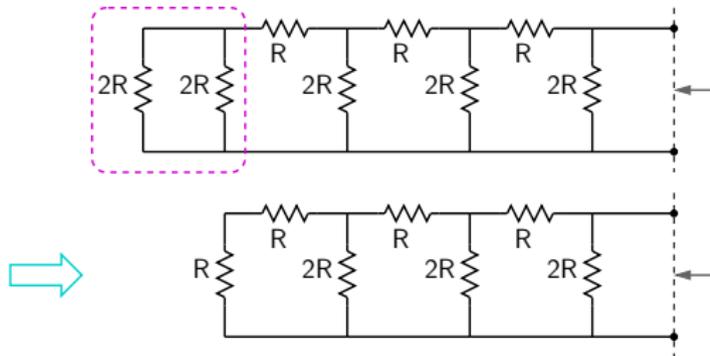


R-2R ladder network: Thevenin resistance

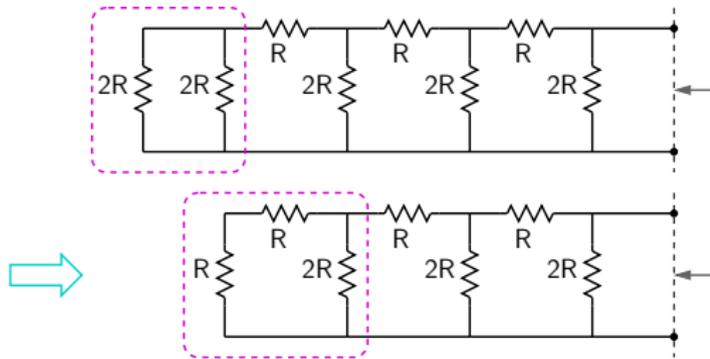


R-2R ladder network: Thevenin resistance

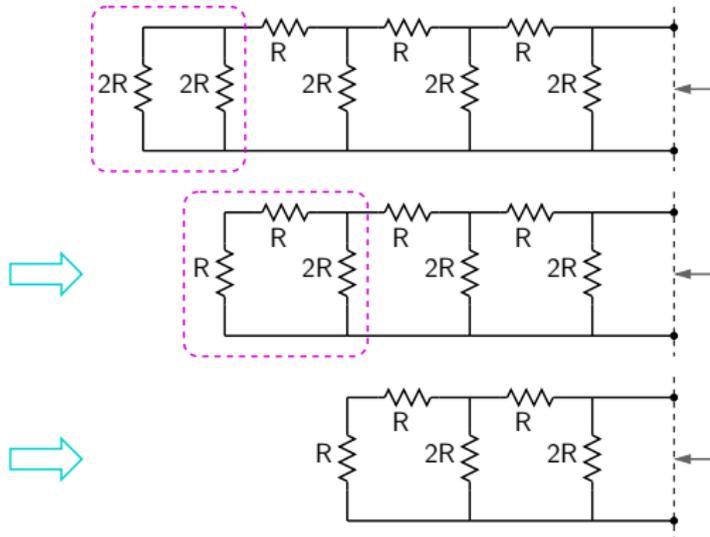


R-2R ladder network: Thevenin resistance

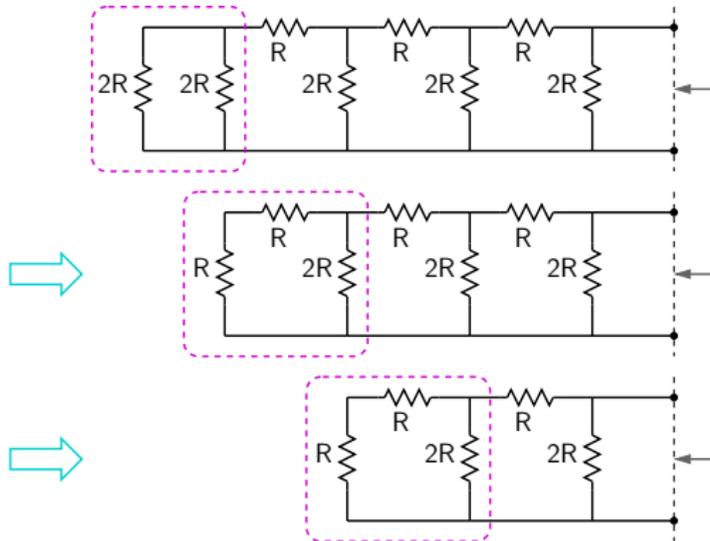


R-2R ladder network: Thevenin resistance

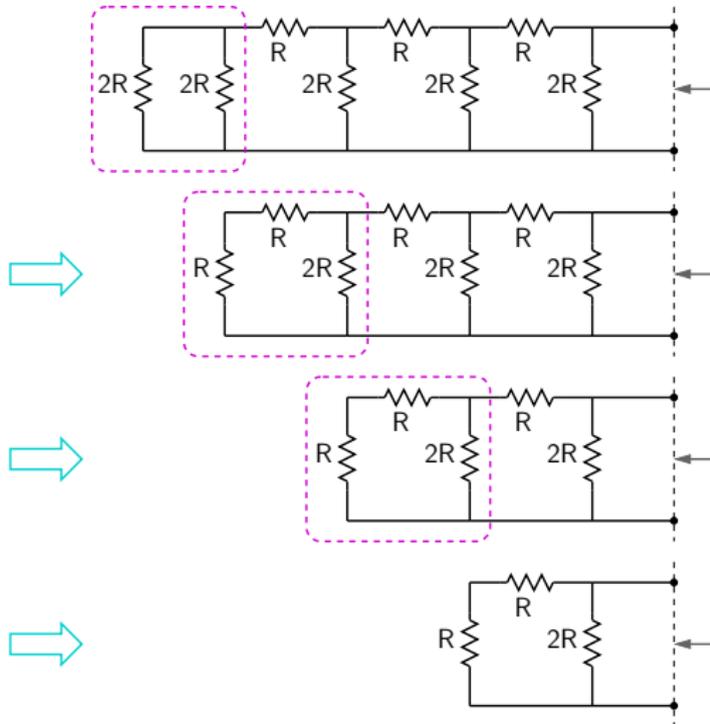


R-2R ladder network: Thevenin resistance

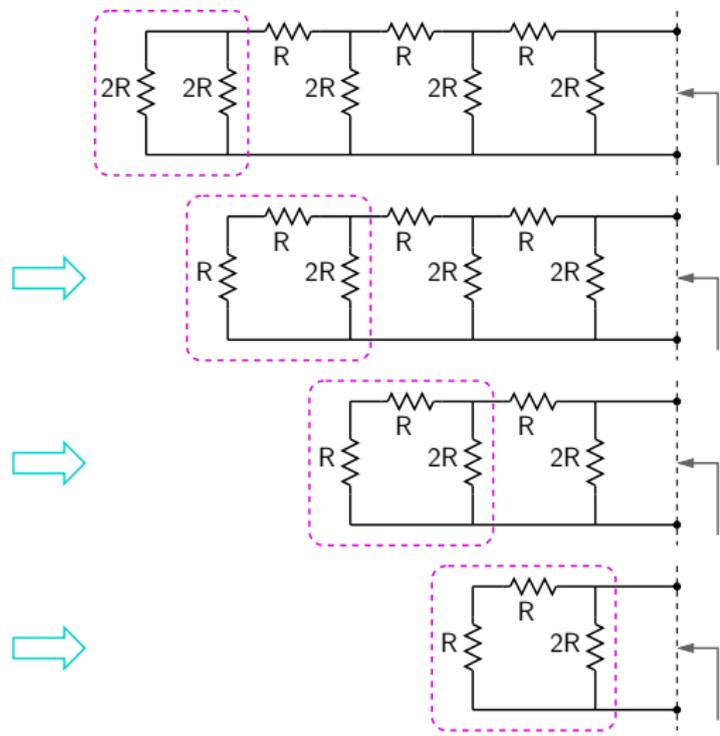


R-2R ladder network: Thevenin resistance

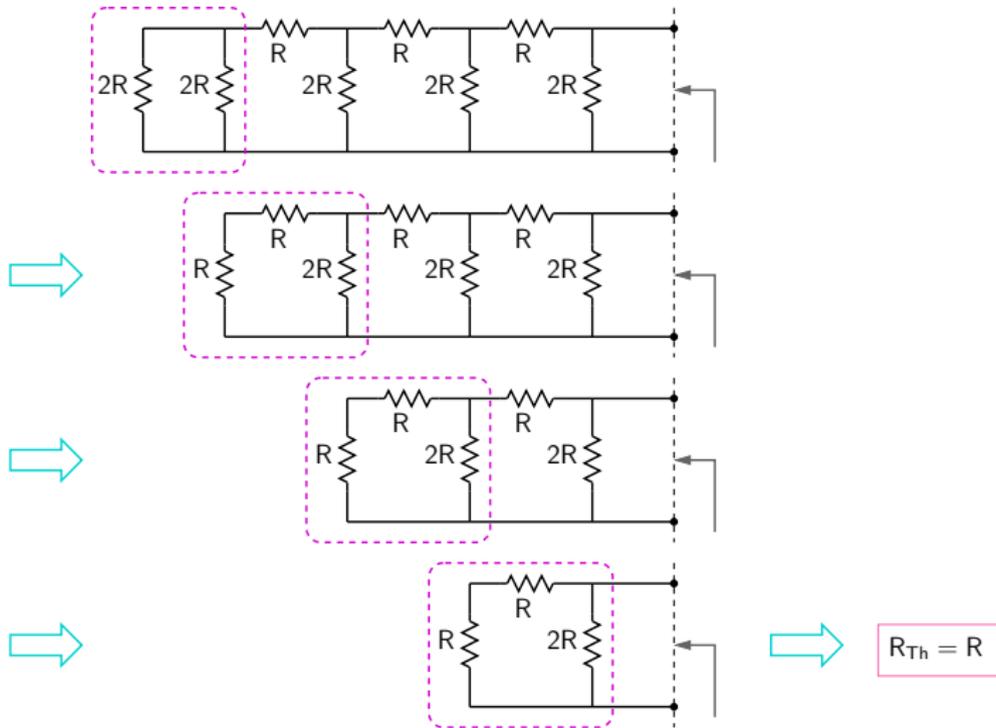

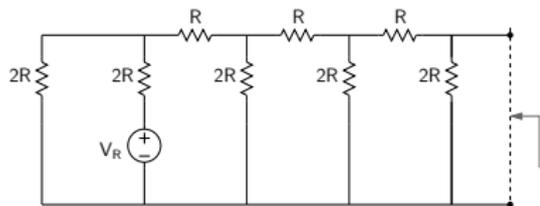
R-2R ladder network: V_{Th} for $S_0 = 1$



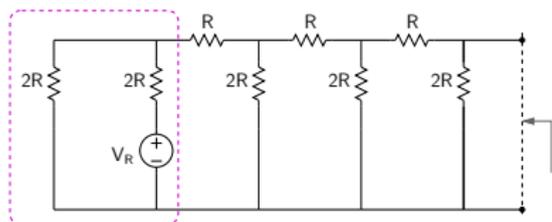
R-2R ladder network: V_{Th} for $S_0 = 1$



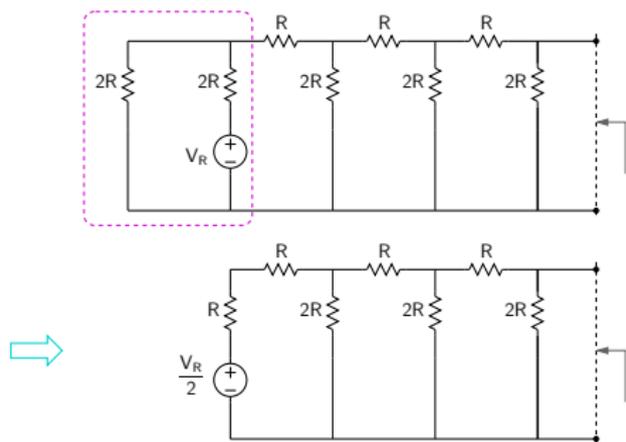
R-2R ladder network: V_{Th} for $S_0 = 1$



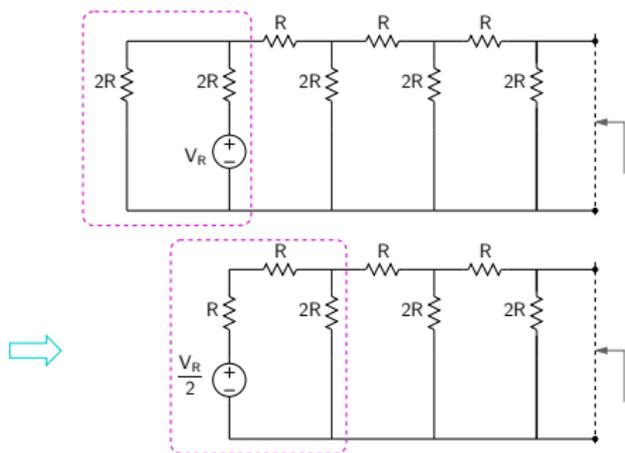
R-2R ladder network: V_{Th} for $S_0 = 1$



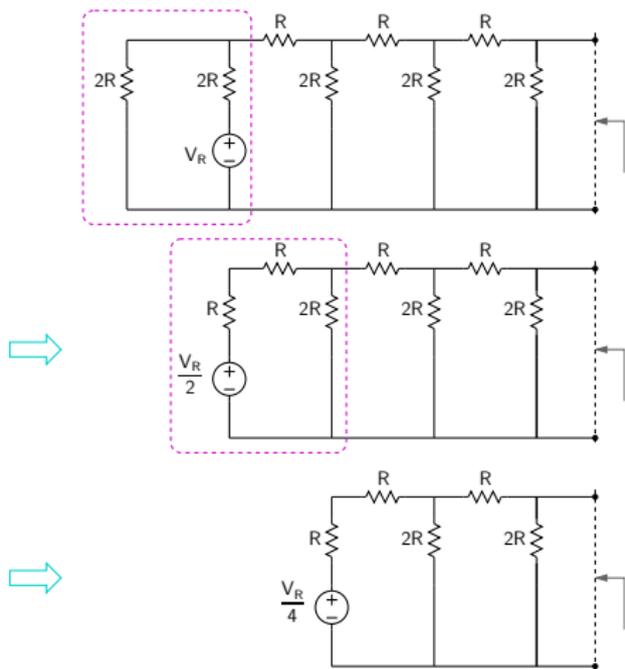
R-2R ladder network: V_{Th} for $S_0 = 1$



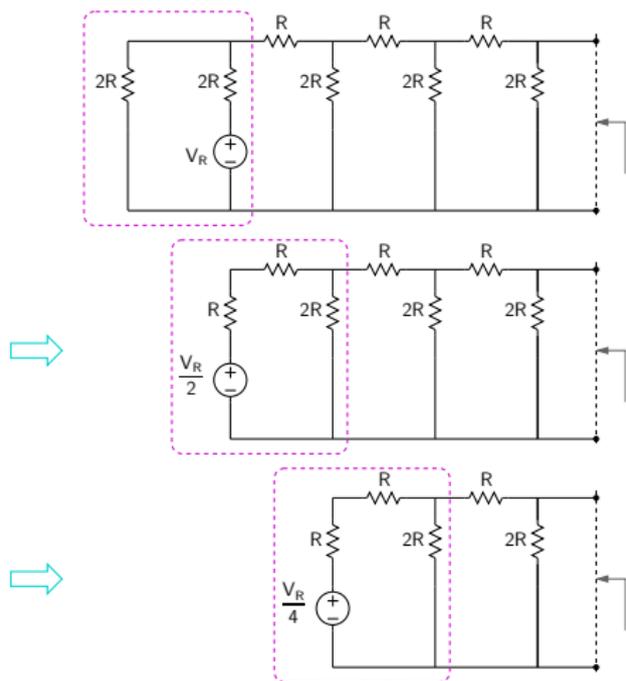
R-2R ladder network: V_{Th} for $S_0 = 1$



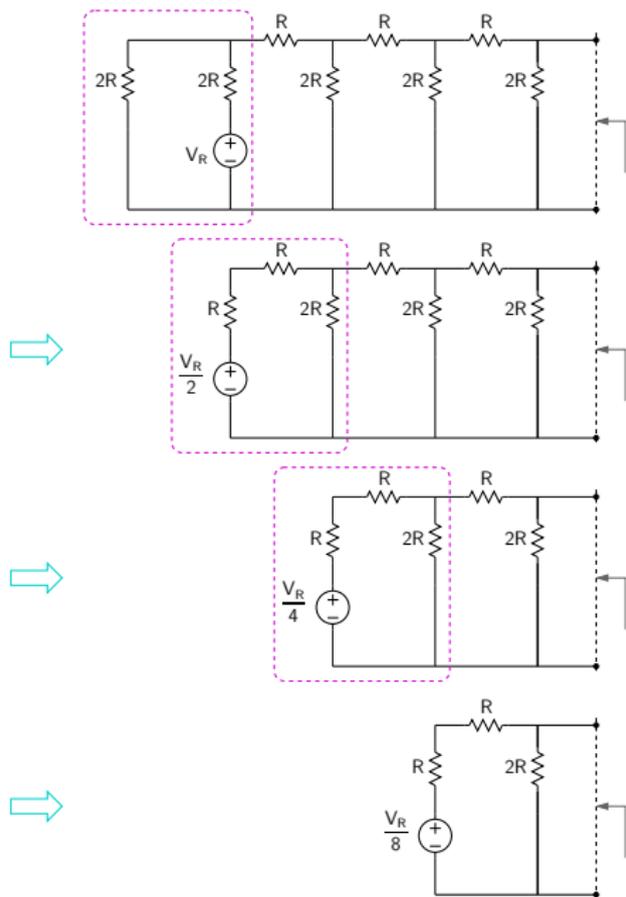
R-2R ladder network: V_{Th} for $S_0 = 1$



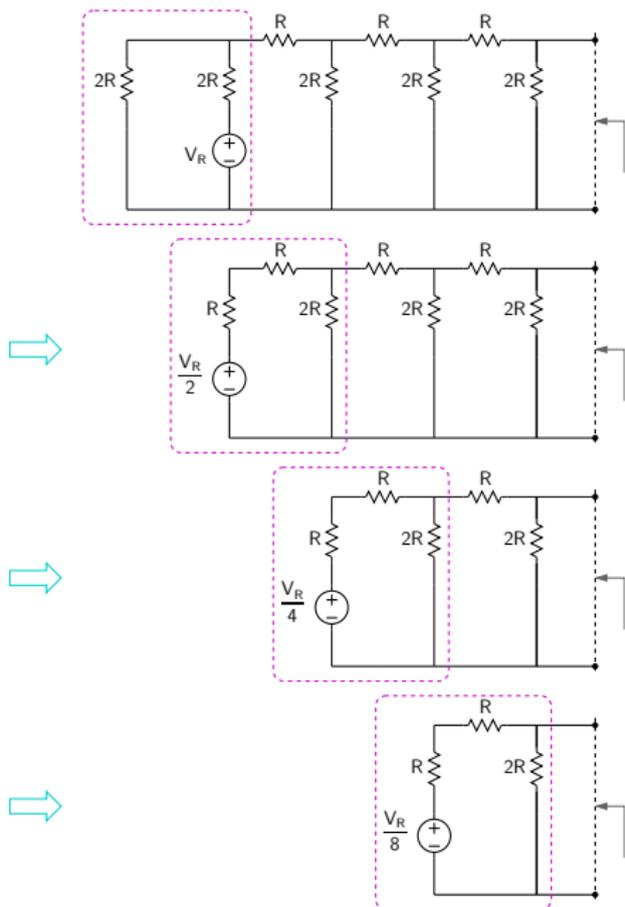
R-2R ladder network: V_{Th} for $S_0 = 1$



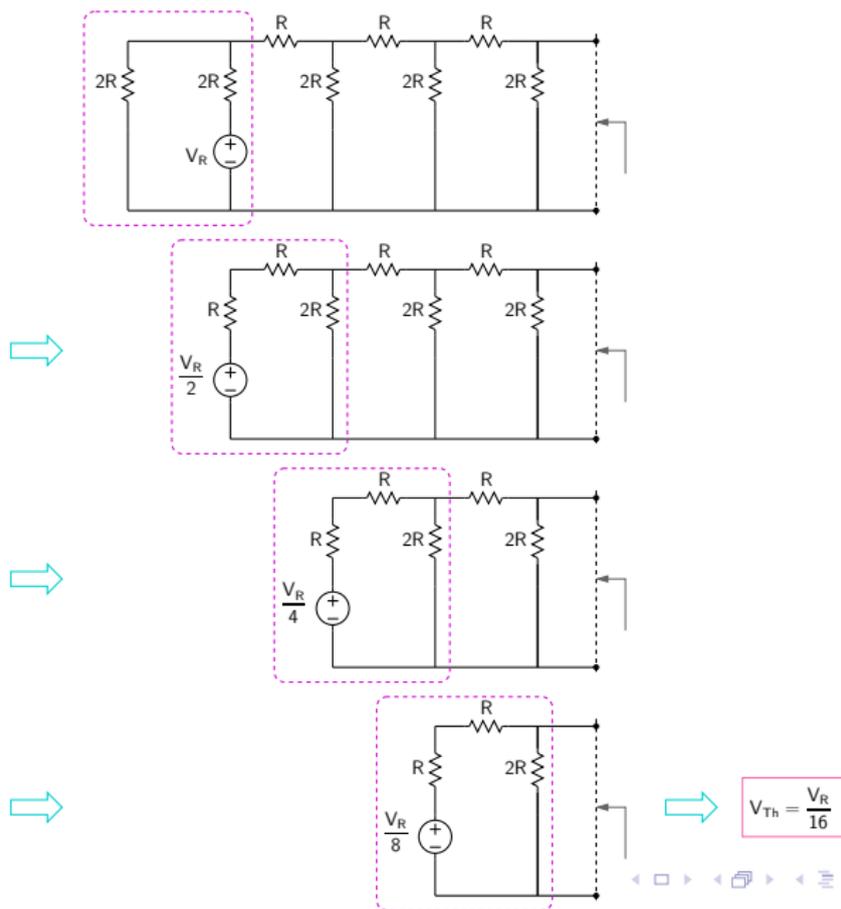
R-2R ladder network: V_{Th} for $S_0 = 1$



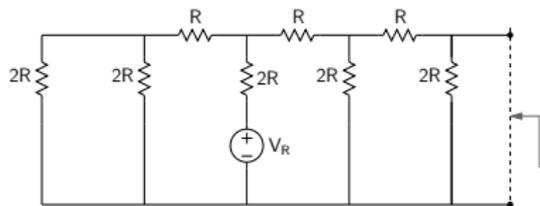
R-2R ladder network: V_{Th} for $S_1 = 1$



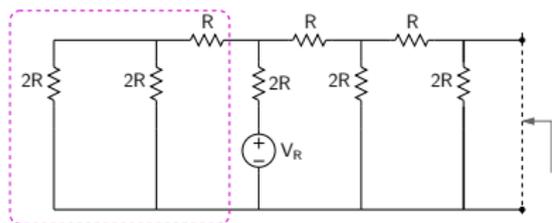
R-2R ladder network: V_{Th} for $S_1 = 1$



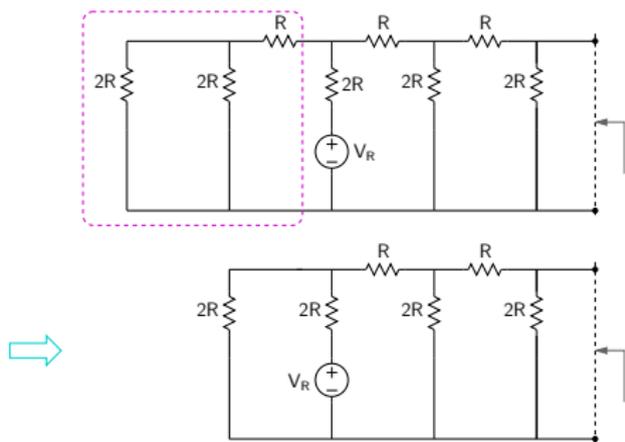
R-2R ladder network: V_{Th} for $S_1 = 1$



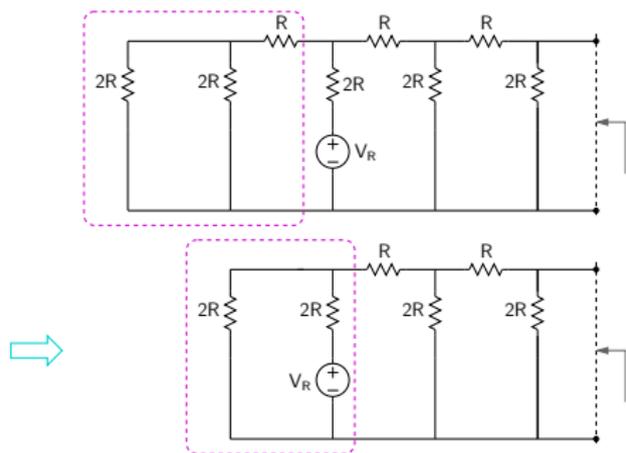
R-2R ladder network: V_{Th} for $S_1 = 1$






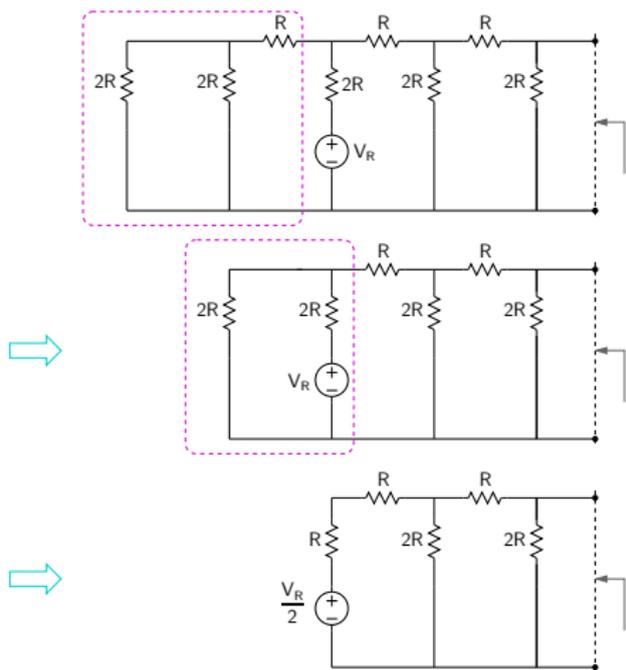
R-2R ladder network: V_{Th} for $S_1 = 1$



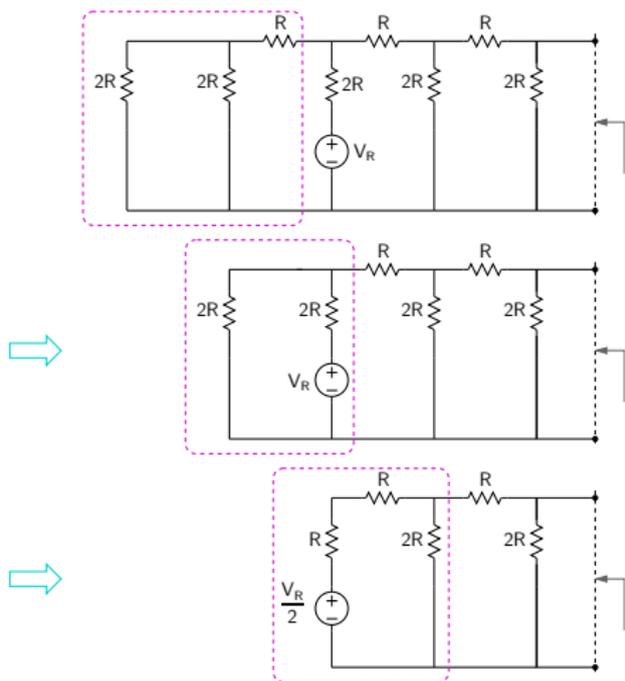
R-2R ladder network: V_{Th} for $S_1 = 1$



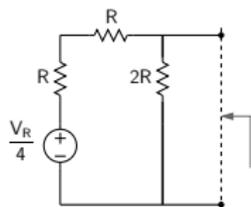
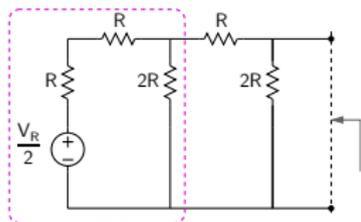
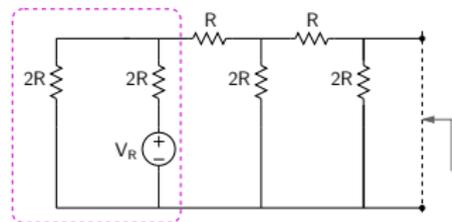
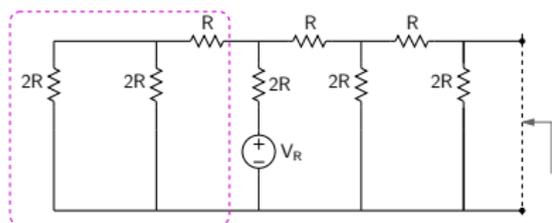
R-2R ladder network: V_{Th} for $S_1 = 1$



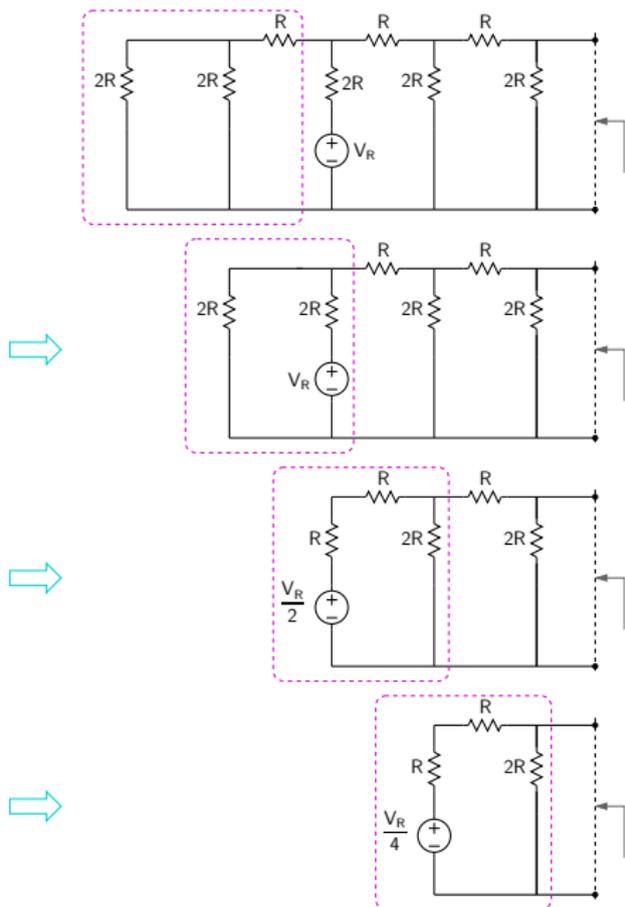R-2R ladder network: V_{Th} for $S_1 = 1$




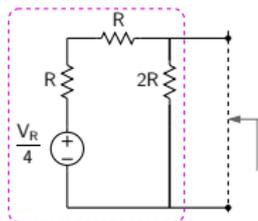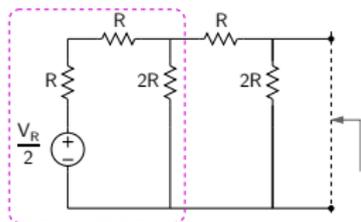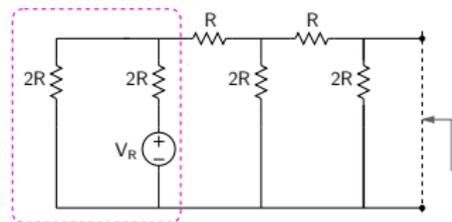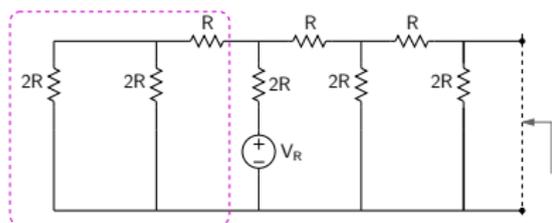R-2R ladder network: V_{Th} for $S_1 = 1$




$$V_{Th} = \frac{V_R}{8}$$


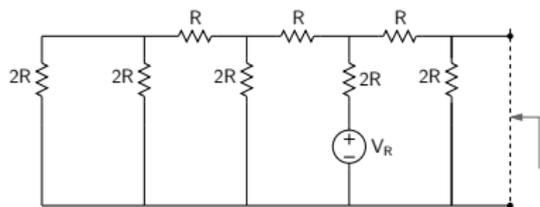
R-2R ladder network: V_{Th} for $S_2 = 1$



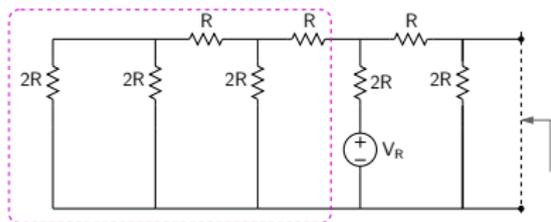
R-2R ladder network: V_{Th} for $S_2 = 1$




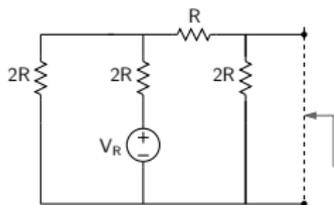
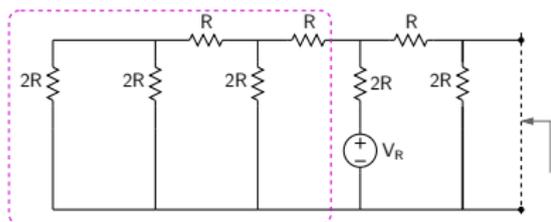
R-2R ladder network: V_{Th} for $S_2 = 1$



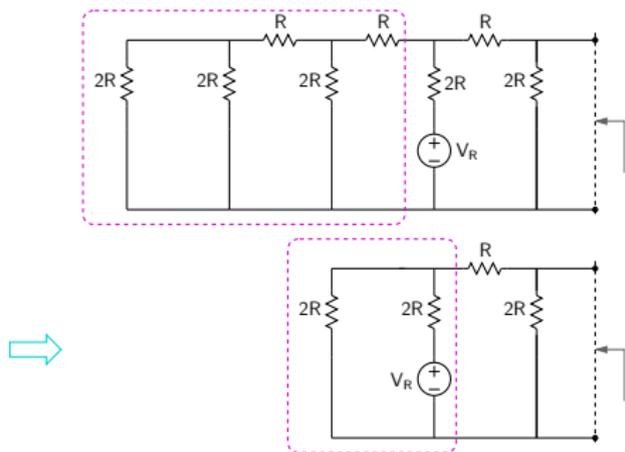
R-2R ladder network: V_{Th} for $S_2 = 1$



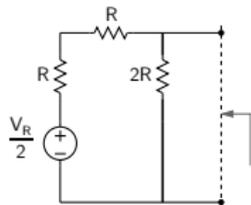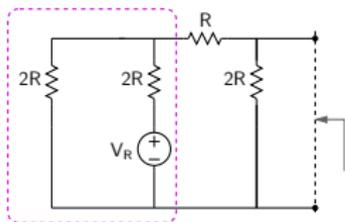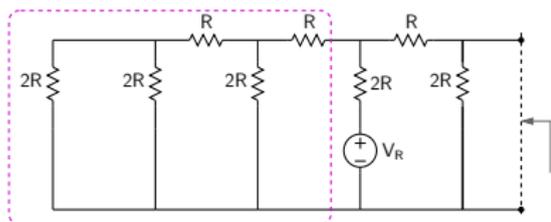
R-2R ladder network: V_{Th} for $S_2 = 1$



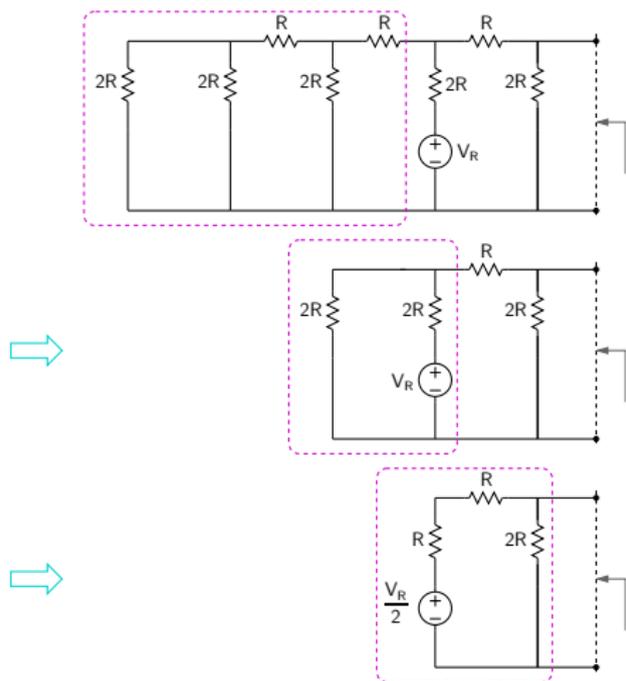
R-2R ladder network: V_{Th} for $S_2 = 1$



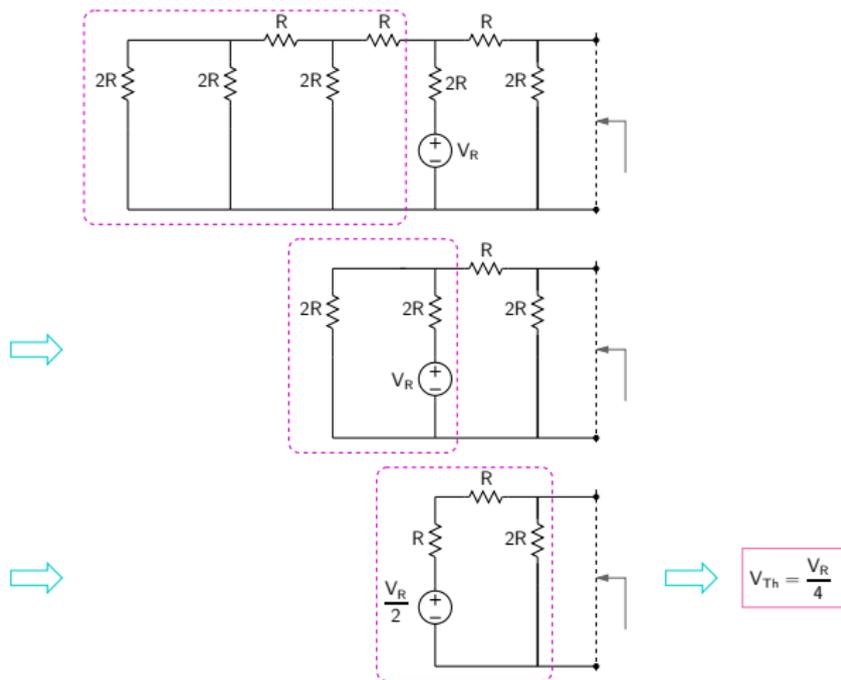
R-2R ladder network: V_{Th} for $S_2 = 1$




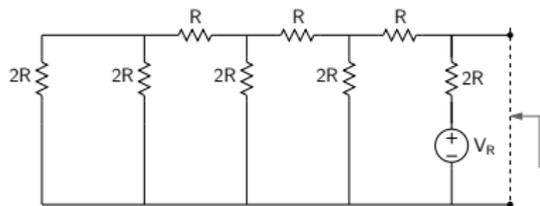
R-2R ladder network: V_{Th} for $S_3 = 1$




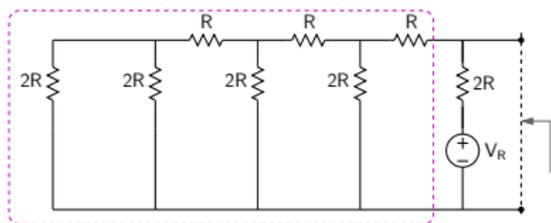
R-2R ladder network: V_{Th} for $S_3 = 1$



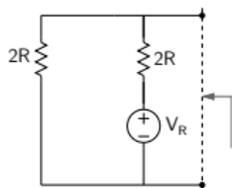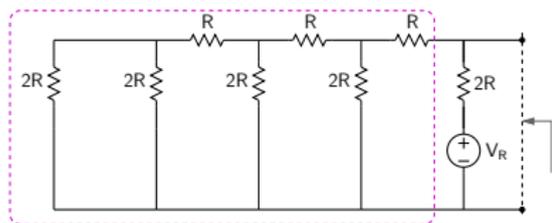R-2R ladder network: V_{Th} for $S_3 = 1$




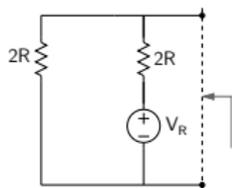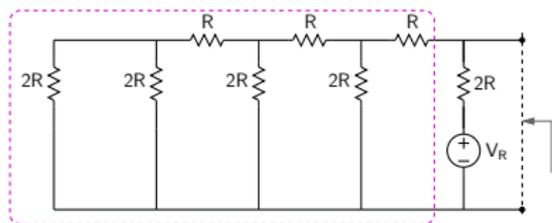R-2R ladder network: V_{Th} for $S_3 = 1$




$$V_{Th} = \frac{V_R}{2}$$

R-2R ladder network: R_{Th} and V_{Th}

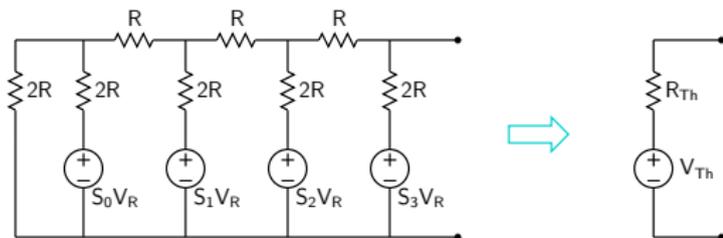


R-2R ladder network: R_{Th} and V_{Th}

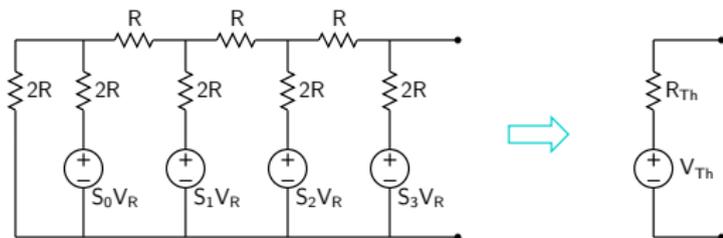

* $R_{Th} = R$.


R-2R ladder network: R_{Th} and V_{Th}

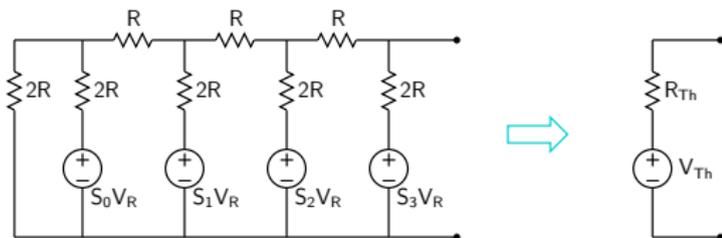

* $R_{Th} = R$.


*
$$V_{Th} = V_{Th}^{(S_0)} + V_{Th}^{(S_1)} + V_{Th}^{(S_2)} + V_{Th}^{(S_3)}$$
$$= \frac{V_R}{16} [S_0 2^0 + S_1 2^1 + S_2 2^2 + S_3 2^3].$$

R-2R ladder network: R_{Th} and V_{Th}

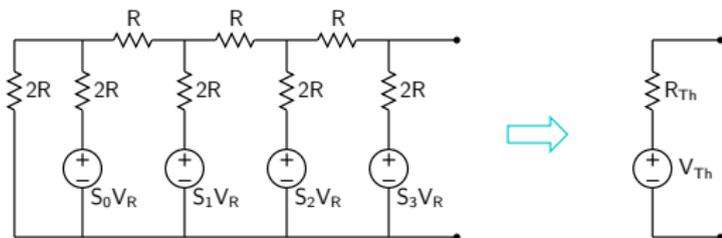


- * $R_{Th} = R$.
- * $V_{Th} = V_{Th}^{(S_0)} + V_{Th}^{(S_1)} + V_{Th}^{(S_2)} + V_{Th}^{(S_3)}$
 $= \frac{V_R}{16} [S_0 2^0 + S_1 2^1 + S_2 2^2 + S_3 2^3]$.
- * We can use the R - $2R$ ladder network and an Op Amp to make up a DAC \rightarrow next slide.

DAC with R-2R ladder

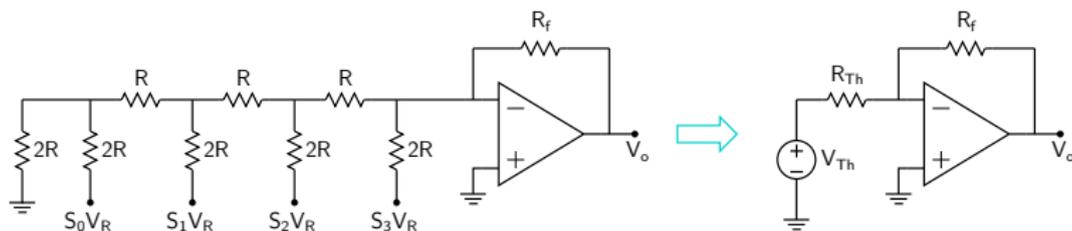


DAC with R-2R ladder

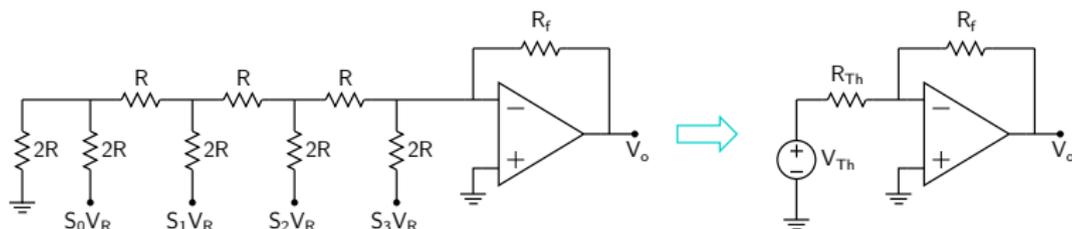

$$* V_o = -\frac{R_f}{R_{Th}} V_{Th} = -\frac{R_f}{R_{Th}} \frac{V_R}{16} [S_0 2^0 + S_1 2^1 + S_2 2^2 + S_3 2^3] .$$


DAC with R-2R ladder

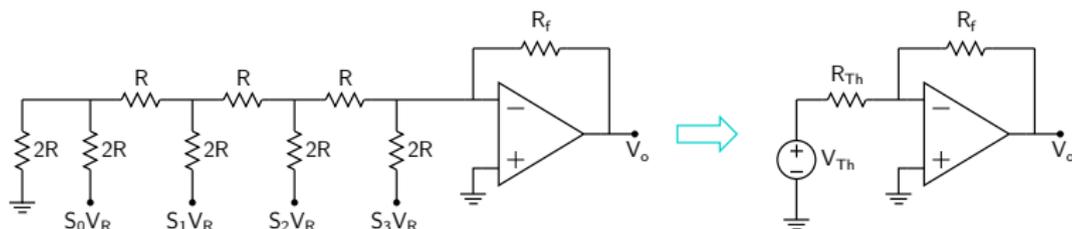

$$* V_o = -\frac{R_f}{R_{Th}} V_{Th} = -\frac{R_f}{R_{Th}} \frac{V_R}{16} [S_0 2^0 + S_1 2^1 + S_2 2^2 + S_3 2^3] .$$

$$* \text{ For an N-bit DAC, } V_o = -\frac{R_f}{R_{Th}} V_{Th} = -\frac{R_f}{R_{Th}} \frac{V_R}{2^N} \sum_0^{N-1} S_k 2^k .$$

DAC with R-2R ladder

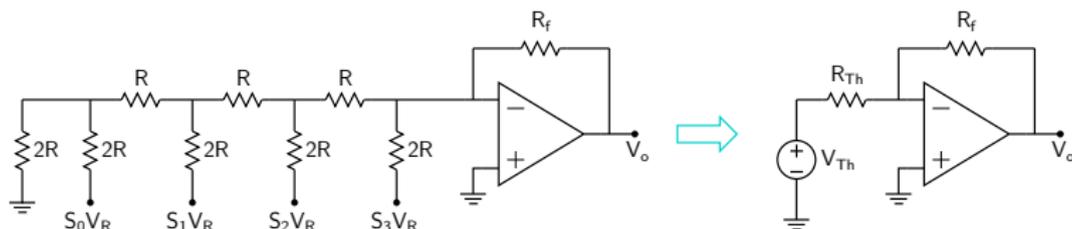


$$* V_o = -\frac{R_f}{R_{Th}} V_{Th} = -\frac{R_f}{R_{Th}} \frac{V_R}{16} [S_0 2^0 + S_1 2^1 + S_2 2^2 + S_3 2^3] .$$

$$* \text{ For an } N\text{-bit DAC, } V_o = -\frac{R_f}{R_{Th}} V_{Th} = -\frac{R_f}{R_{Th}} \frac{V_R}{2^N} \sum_0^{N-1} S_k 2^k .$$

- * 6- to 20-bit DACs based on the R-2R ladder network are commercially available in monolithic form (single chip).

DAC with R-2R ladder

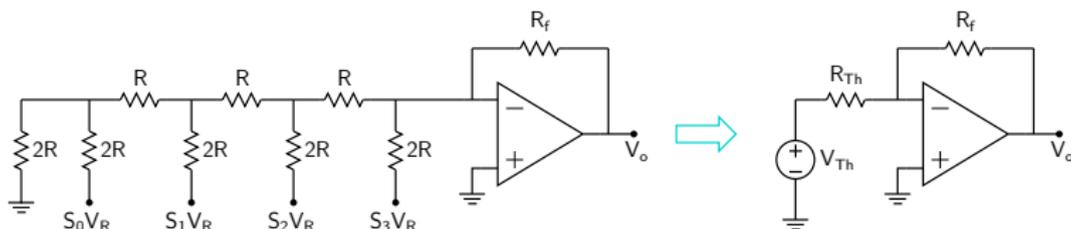


$$* V_o = -\frac{R_f}{R_{Th}} V_{Th} = -\frac{R_f}{R_{Th}} \frac{V_R}{16} [S_0 2^0 + S_1 2^1 + S_2 2^2 + S_3 2^3] .$$


$$* \text{ For an N-bit DAC, } V_o = -\frac{R_f}{R_{Th}} V_{Th} = -\frac{R_f}{R_{Th}} \frac{V_R}{2^N} \sum_0^{N-1} S_k 2^k .$$

- * 6- to 20-bit DACs based on the R-2R ladder network are commercially available in monolithic form (single chip).
- * Bipolar, CMOS, or BiCMOS technology is used for these DACs.

DAC: home work

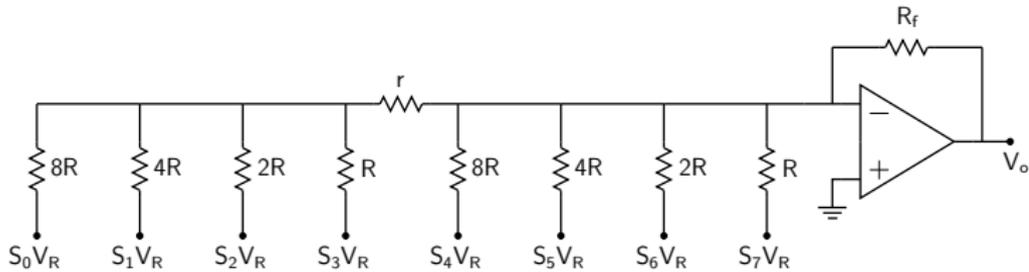


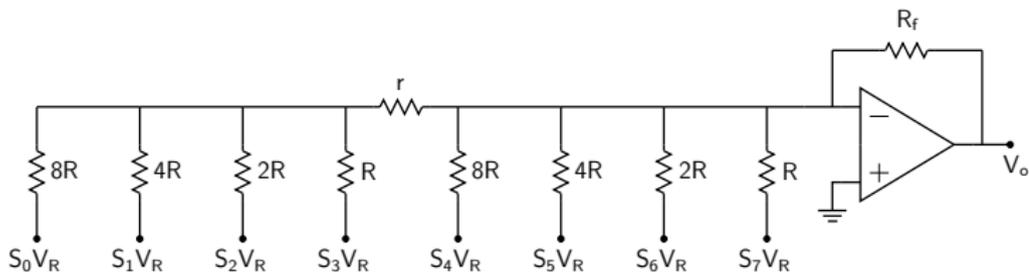Combination of weighted-resistor and R-2R ladder networks



Combination of weighted-resistor and R-2R ladder networks


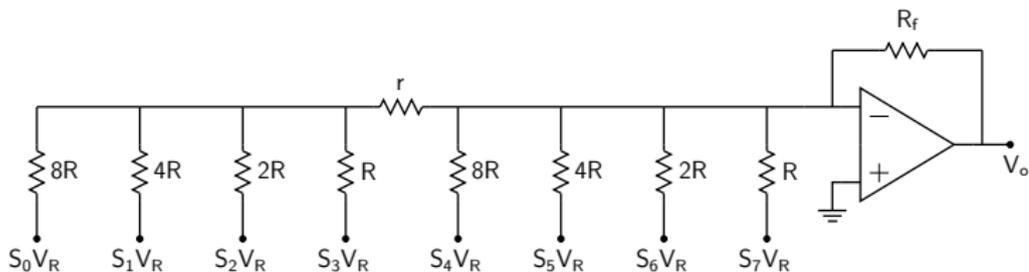
- * Find the value of r for the circuit to work as a regular (i.e., binary to analog) DAC.





Combination of weighted-resistor and R-2R ladder networks

- * Find the value of r for the circuit to work as a regular (i.e., binary to analog) DAC.
- * Find the value of r for the circuit to work as a BCD to analog DAC.

DAC: settling time

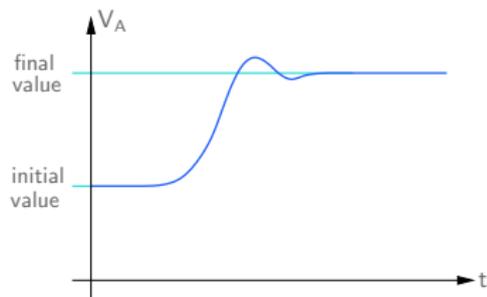
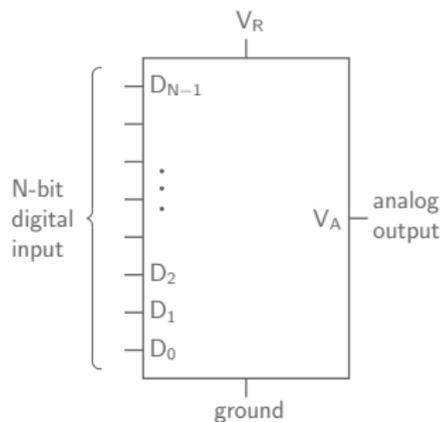


DAC: settling time

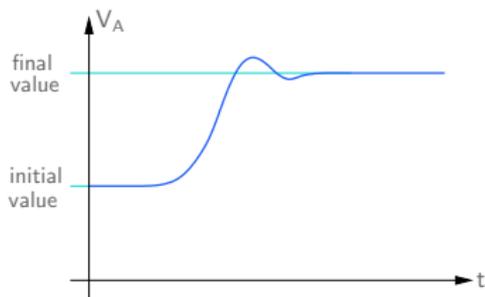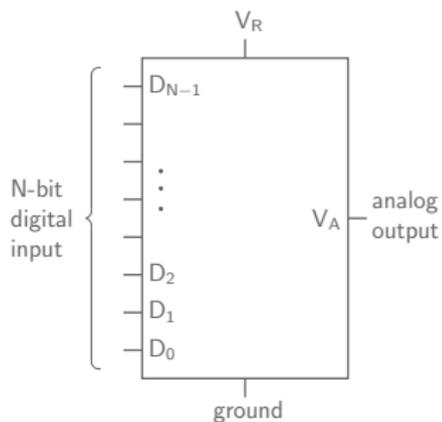



- * When there is a change in the input binary number, the output V_A takes a finite time to settle to the new value.

DAC: settling time

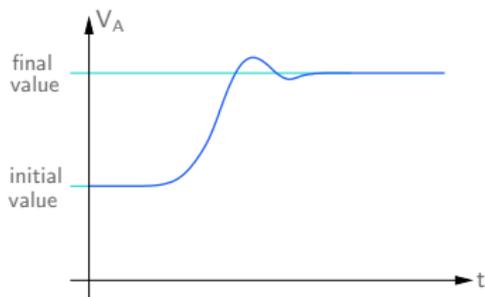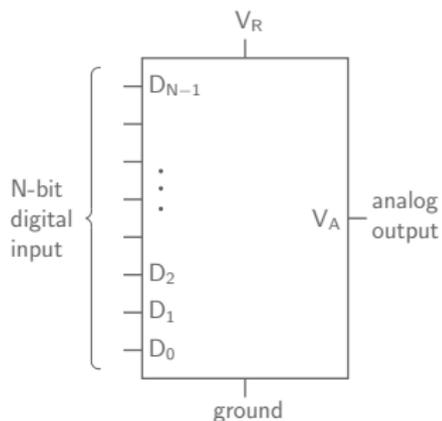



- * When there is a change in the input binary number, the output V_A takes a finite time to settle to the new value.
- * The finite settling time arises because of stray capacitances and switching delays of the semiconductor devices used within the DAC chip.

DAC: settling time

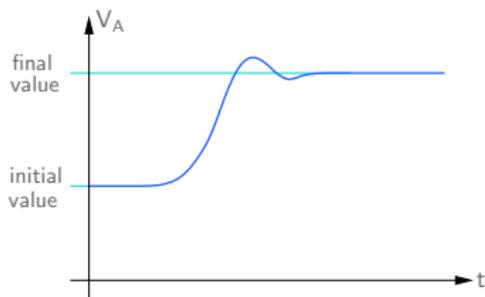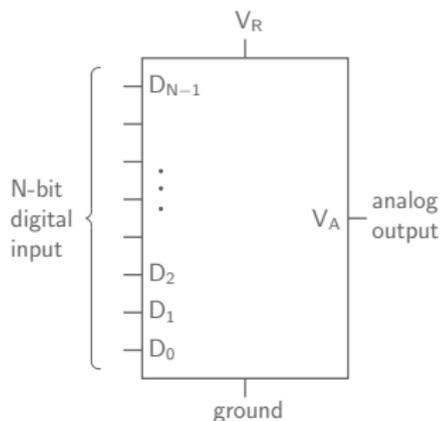


- * When there is a change in the input binary number, the output V_A takes a finite time to settle to the new value.
- * The finite settling time arises because of stray capacitances and switching delays of the semiconductor devices used within the DAC chip.
- * Example: 500 ns to 0.2% of full scale.



ADC: introduction

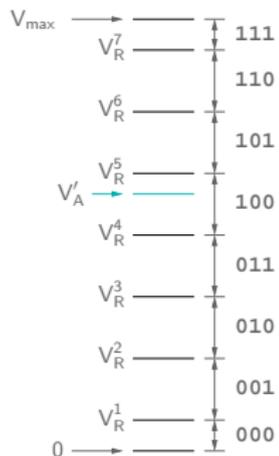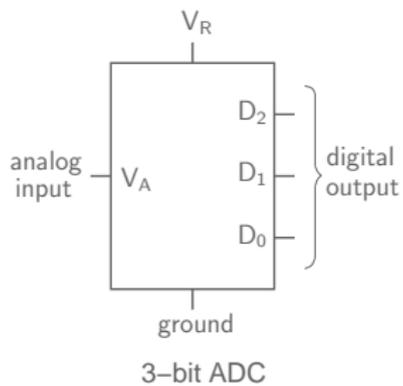

ADC: introduction

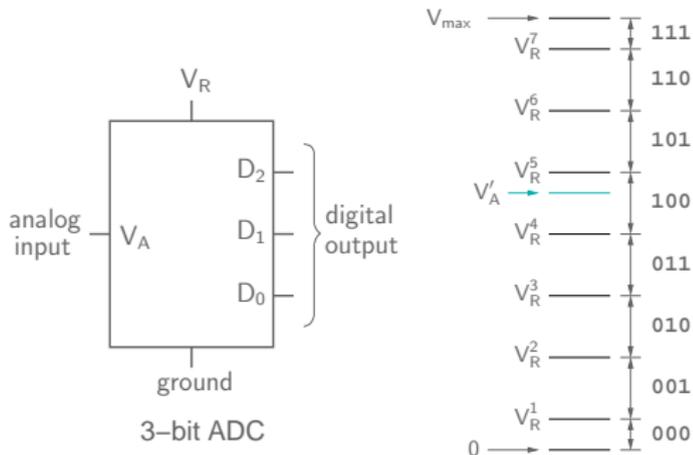


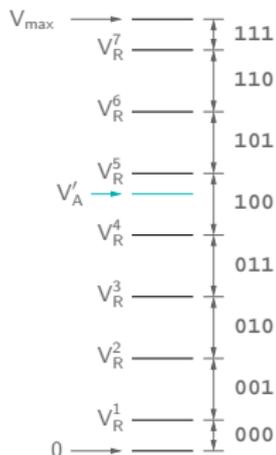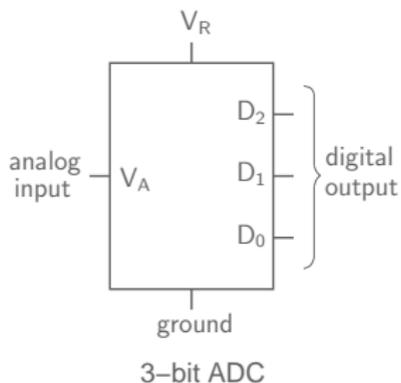- * If the input V_A is in the range $V_R^k < V_A < V_R^{k+1}$, the output is the binary number corresponding to the integer k . For example, for $V_A = V_A'$, the output is 100.





- * If the input V_A is in the range $V_R^k < V_A < V_R^{k+1}$, the output is the binary number corresponding to the integer k . For example, for $V_A = V_A'$, the output is 100.
- * We may think of each voltage interval (corresponding to 000, 001, etc.) as a “bin.” In the above example, the input voltage V_A' falls in the 100 bin; therefore, the output of the ADC would be 100.

ADC: introduction

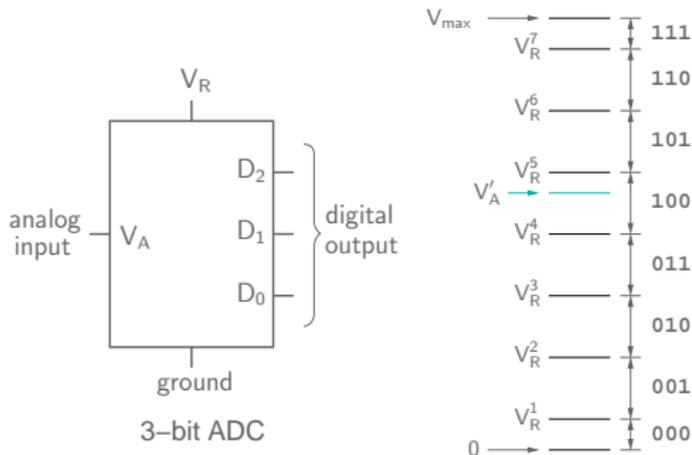


- * If the input V_A is in the range $V_R^k < V_A < V_R^{k+1}$, the output is the binary number corresponding to the integer k . For example, for $V_A = V_A'$, the output is 100.
- * We may think of each voltage interval (corresponding to 000, 001, etc.) as a "bin." In the above example, the input voltage V_A' falls in the 100 bin; therefore, the output of the ADC would be 100.
- * Note that, for an N-bit ADC, there would be 2^N bins.


ADC: introduction

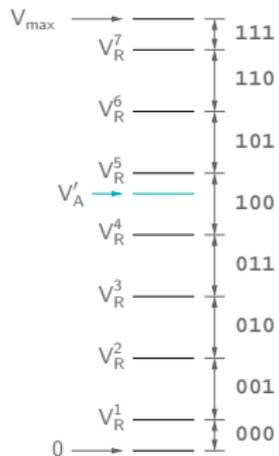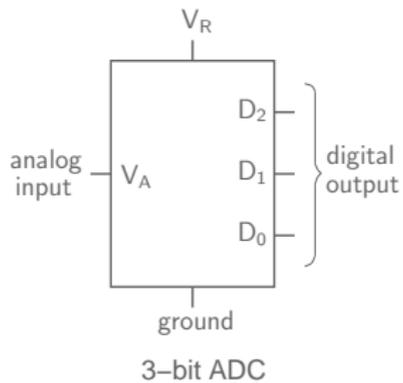


ADC: introduction

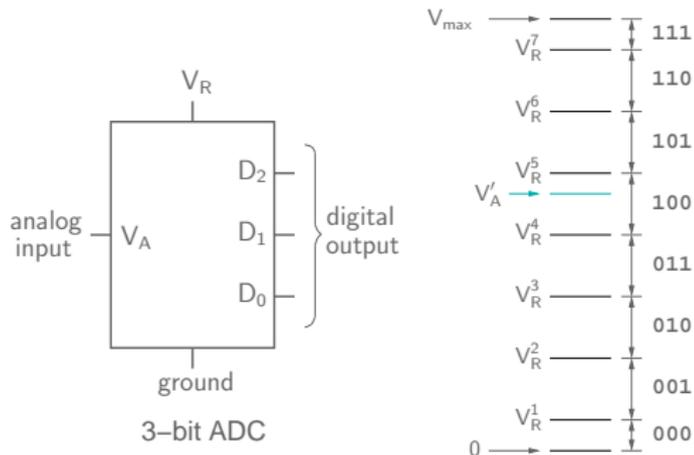

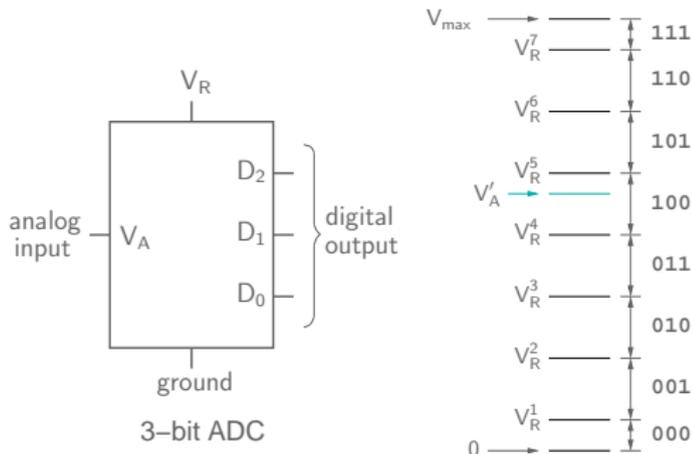
- * The basic idea behind an ADC is simple:



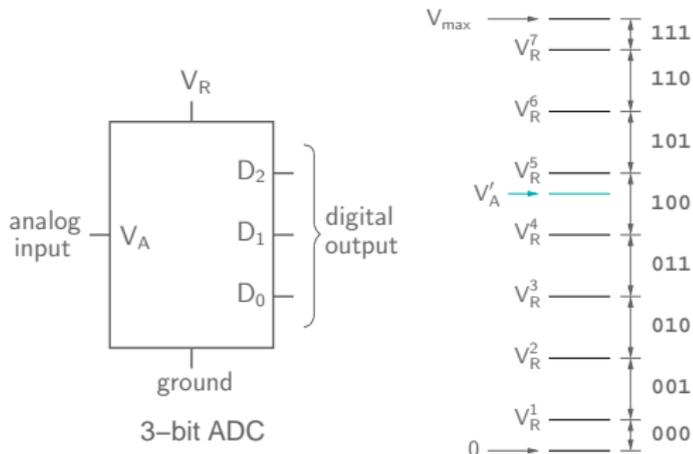- * The basic idea behind an ADC is simple:
 - Generate reference voltages V_R^1 , V_R^2 , etc.




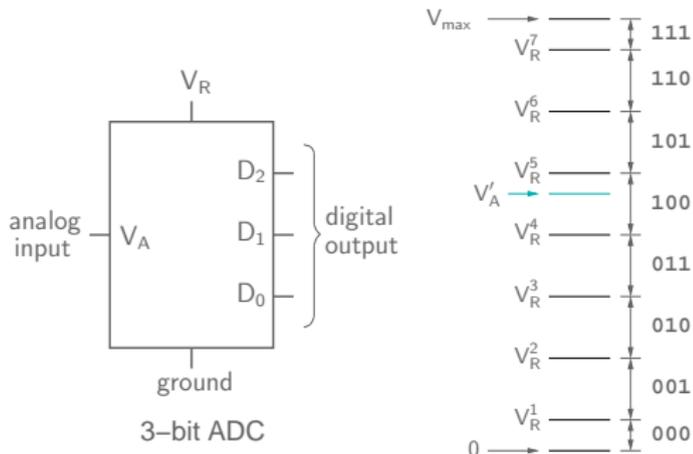- * The basic idea behind an ADC is simple:
 - Generate reference voltages V_R^1, V_R^2 , etc.
 - Compare the input V_A with each of V_R^i to figure out which bin it belongs to.






* The basic idea behind an ADC is simple:

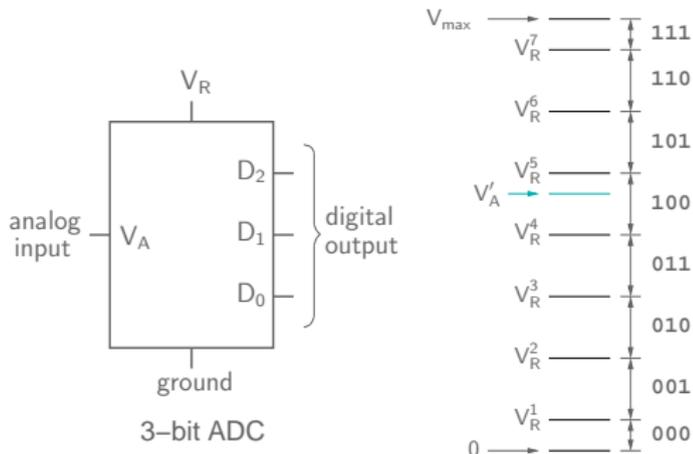- Generate reference voltages V_R^1 , V_R^2 , etc.
- Compare the input V_A with each of V_R^i to figure out which bin it belongs to.
- If V_A belongs to bin k (i.e., $V_R^k < V_A < V_R^{k+1}$), convert k to the binary format.




- * The basic idea behind an ADC is simple:
 - Generate reference voltages V_R^1 , V_R^2 , etc.
 - Compare the input V_A with each of V_R^i to figure out which bin it belongs to.
 - If V_A belongs to bin k (i.e., $V_R^k < V_A < V_R^{k+1}$), convert k to the binary format.
- * A "parallel" ADC does exactly that → next slide.


3-bit parallel (flash) ADC

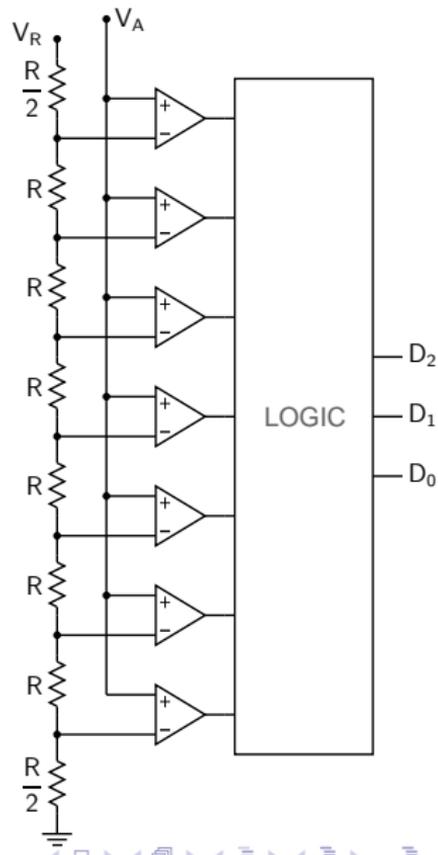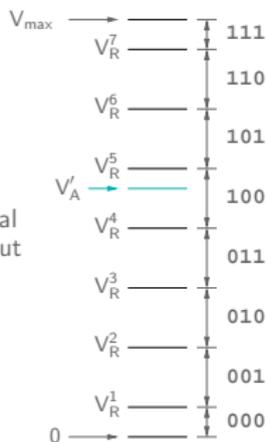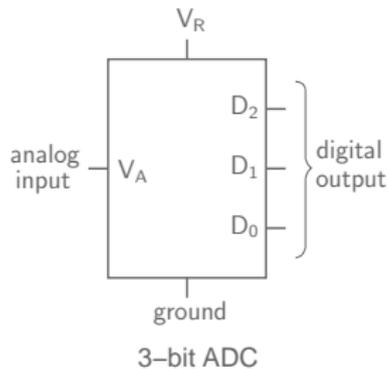

3-bit parallel (flash) ADC

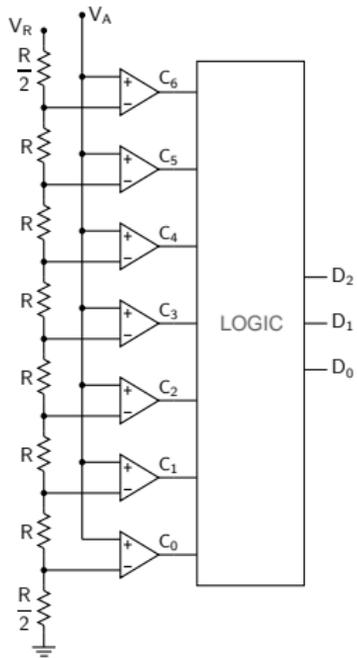


3-bit parallel (flash) ADC

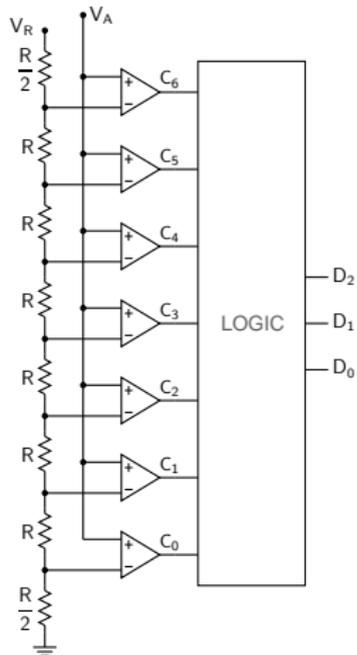


- * Practical difficulty: As the input changes, the comparator outputs (C_0 , C_1 , etc.) may not settle to their new values at the same time.
→ ADC output will depend on when we sample it.

3-bit parallel (flash) ADC

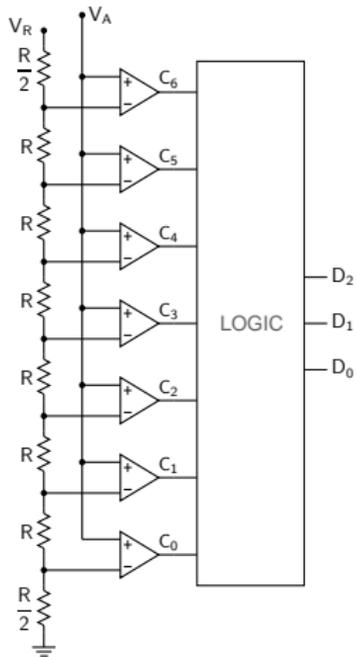

- * Practical difficulty: As the input changes, the comparator outputs (C_0 , C_1 , etc.) may not settle to their new values at the same time.
→ ADC output will depend on when we sample it.
- * Add D flip-flops. Allow sufficient time (between the change in V_A and the active clock edge) so that the comparator outputs have already settled to their new values before they get latched in.

3-bit parallel (flash) ADC

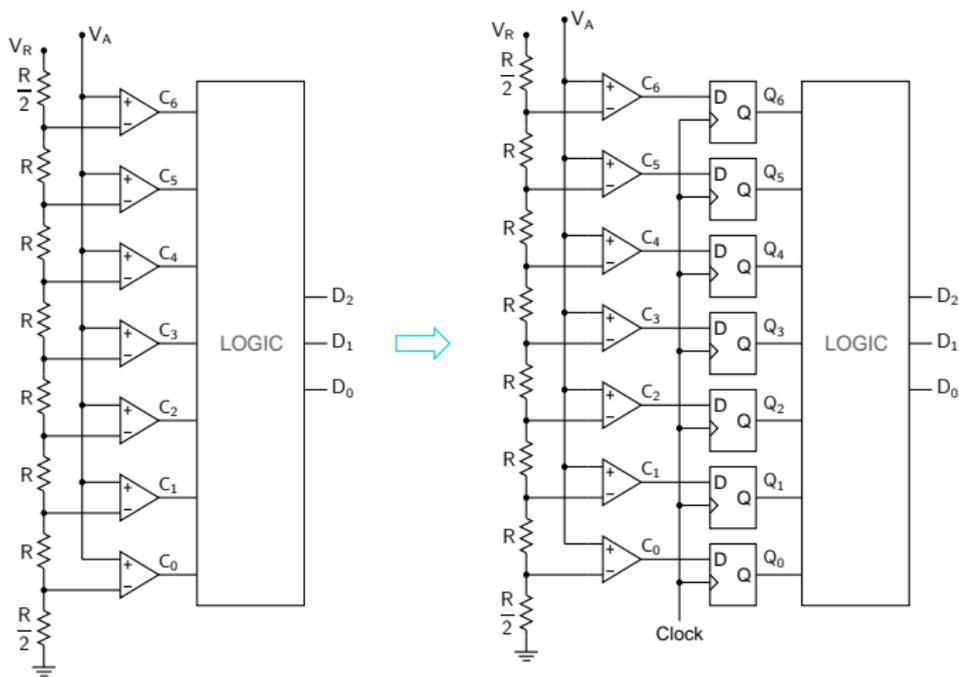

- * Practical difficulty: As the input changes, the comparator outputs (C_0 , C_1 , etc.) may not settle to their new values at the same time.
→ ADC output will depend on when we sample it.
- * Add D flip-flops. Allow sufficient time (between the change in V_A and the active clock edge) so that the comparator outputs have already settled to their new values before they get latched in.

Parallel (flash) ADC

- * In the parallel (flash) ADC, the conversion gets done “in parallel,” since all comparators operate on the same input voltage.

Parallel (flash) ADC

- * In the parallel (flash) ADC, the conversion gets done “in parallel,” since all comparators operate on the same input voltage.
- * Conversion time is governed only by the comparator response time → fast conversion (hence the name “flash” converter).




Parallel (flash) ADC

- * In the parallel (flash) ADC, the conversion gets done “in parallel,” since all comparators operate on the same input voltage.
- * Conversion time is governed only by the comparator response time → fast conversion (hence the name “flash” converter).
- * Flash ADCs to handle 500 million analog samples per second are commercially available.




Parallel (flash) ADC

- * In the parallel (flash) ADC, the conversion gets done “in parallel,” since all comparators operate on the same input voltage.
- * Conversion time is governed only by the comparator response time → fast conversion (hence the name “flash” converter).
- * Flash ADCs to handle 500 million analog samples per second are commercially available.
- * 2^N comparators are required for N-bit ADC → generally limited to 8 bits.

ADC: sampling of input signal

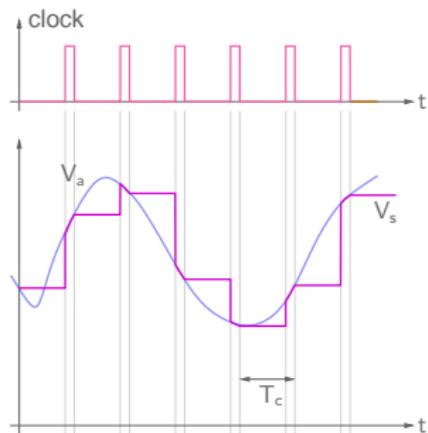
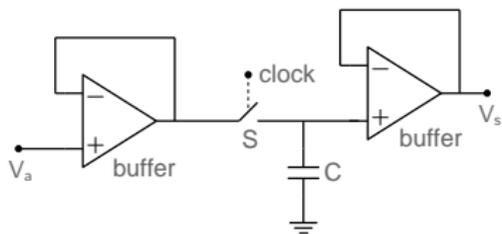
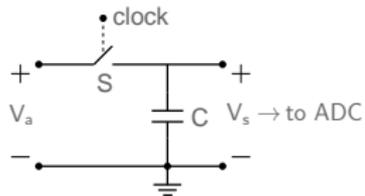


ADC: sampling of input signal

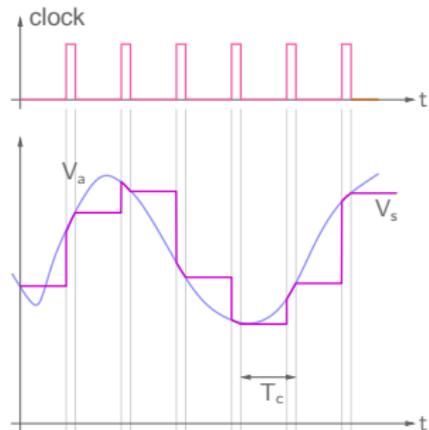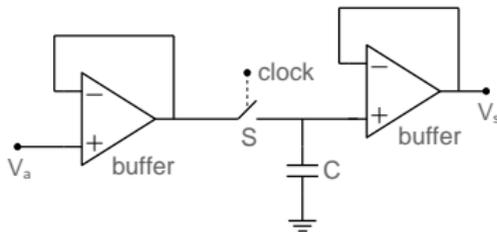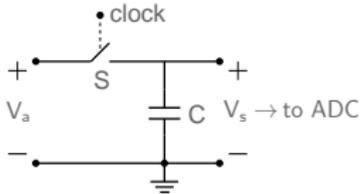




- * An ADC typically operates on a “sampled” input signal ($V_s(t)$ in the figure) which is derived from the continuously varying input signal ($V_a(t)$ in the figure) with a “sample-and-hold” (S/H) circuit.

ADC: sampling of input signal

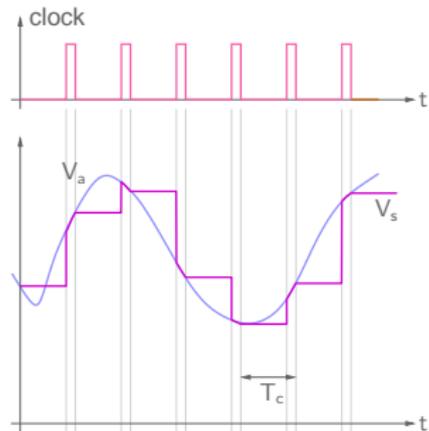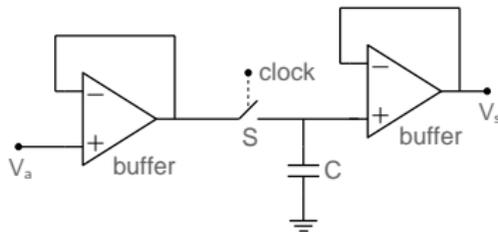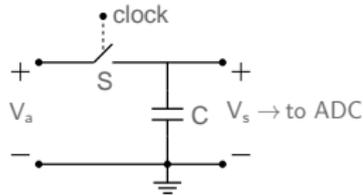




- * An ADC typically operates on a “sampled” input signal ($V_s(t)$ in the figure) which is derived from the continuously varying input signal ($V_a(t)$ in the figure) with a “sample-and-hold” (S/H) circuit.
- * The S/H circuit samples the input signal $V_a(t)$ at uniform intervals of duration T_c , the clock period.

ADC: sampling of input signal

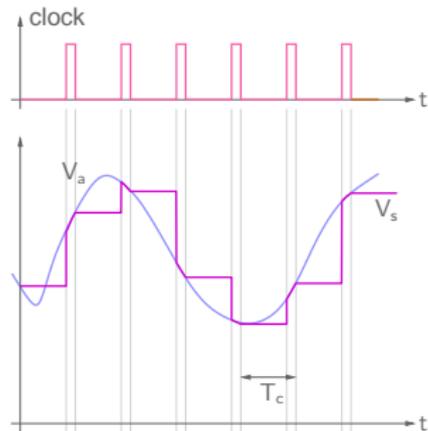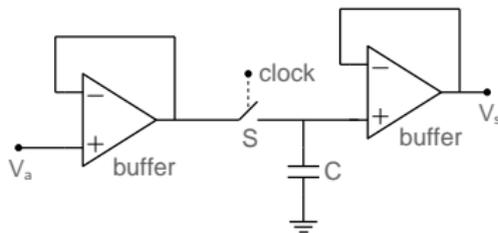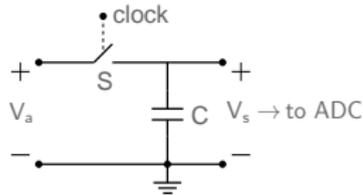


- * An ADC typically operates on a “sampled” input signal ($V_s(t)$ in the figure) which is derived from the continuously varying input signal ($V_a(t)$ in the figure) with a “sample-and-hold” (S/H) circuit.
- * The S/H circuit samples the input signal $V_a(t)$ at uniform intervals of duration T_c , the clock period.
- * When the clock goes high, switch S (e.g., a FET or a CMOS pass gate) is closed, and the capacitor C gets charged to the signal voltage at that time. When the clock goes low, switch S is turned off, and C holds the voltage constant, as desired.

ADC: sampling of input signal

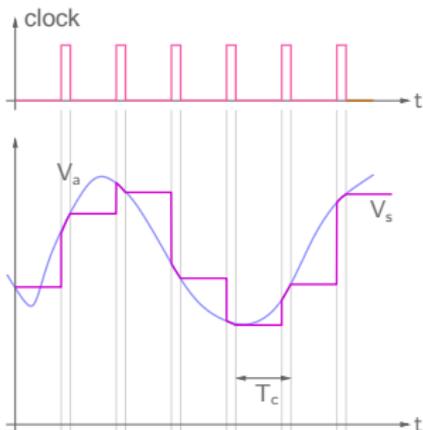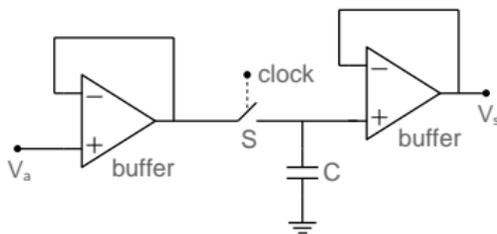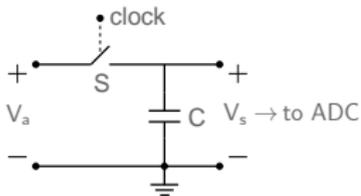


- * An ADC typically operates on a “sampled” input signal ($V_s(t)$ in the figure) which is derived from the continuously varying input signal ($V_a(t)$ in the figure) with a “sample-and-hold” (S/H) circuit.
- * The S/H circuit samples the input signal $V_a(t)$ at uniform intervals of duration T_c , the clock period.
- * When the clock goes high, switch S (e.g., a FET or a CMOS pass gate) is closed, and the capacitor C gets charged to the signal voltage at that time. When the clock goes low, switch S is turned off, and C holds the voltage constant, as desired.
- * Op Amp buffers can be used to minimise loading effects.

Successive Approximation ADC

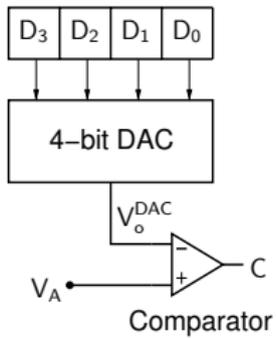


Successive Approximation ADC

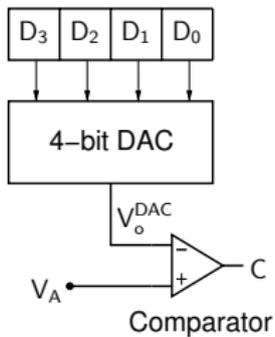


- * Suppose we have a 4-bit DAC. We can use it to perform A-to-D conversion by successively setting the four bits as follows.

Successive Approximation ADC

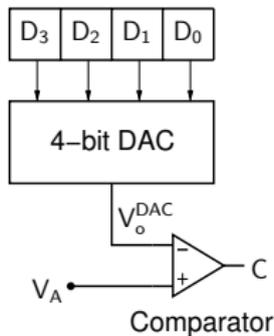


- * Suppose we have a 4-bit DAC. We can use it to perform A-to-D conversion by successively setting the four bits as follows.
 - Start with $D_3D_2D_1D_0 = 0000$, $I = 3$.

Successive Approximation ADC

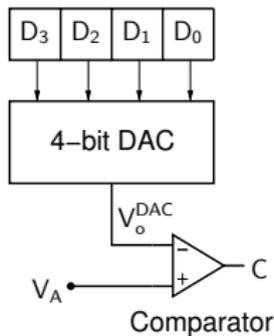


- * Suppose we have a 4-bit DAC. We can use it to perform A-to-D conversion by successively setting the four bits as follows.
 - Start with $D_3D_2D_1D_0 = 0000$, $I = 3$.
 - Set $D[I] = 1$ (keep other bits unchanged).

Successive Approximation ADC

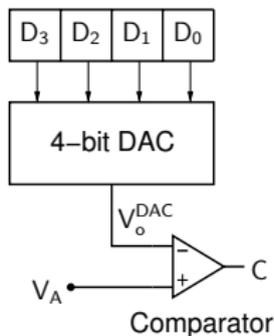


- * Suppose we have a 4-bit DAC. We can use it to perform A-to-D conversion by successively setting the four bits as follows.
 - Start with $D_3D_2D_1D_0 = 0000$, $I = 3$.
 - Set $D[I] = 1$ (keep other bits unchanged).
 - If $V_o^{DAC} > V_A$ (i.e., $C = 0$), set $D[I] = 0$; else, keep $D[I] = 1$.

Successive Approximation ADC

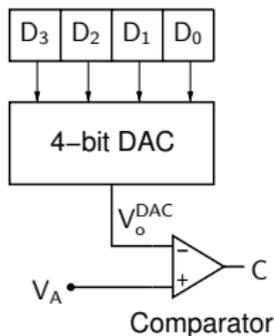



- * Suppose we have a 4-bit DAC. We can use it to perform A-to-D conversion by successively setting the four bits as follows.
 - Start with $D_3D_2D_1D_0 = 0000$, $I = 3$.
 - Set $D[I] = 1$ (keep other bits unchanged).
 - If $V_o^{DAC} > V_A$ (i.e., $C = 0$), set $D[I] = 0$; else, keep $D[I] = 1$.
 - $I \leftarrow I - 1$; go to step 1.

Successive Approximation ADC


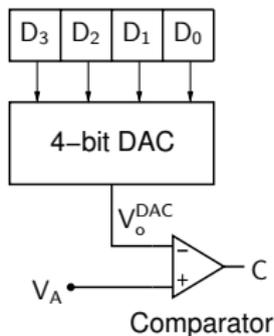


- * Suppose we have a 4-bit DAC. We can use it to perform A-to-D conversion by successively setting the four bits as follows.
 - Start with $D_3D_2D_1D_0 = 0000$, $I = 3$.
 - Set $D[I] = 1$ (keep other bits unchanged).
 - If $V_o^{DAC} > V_A$ (i.e., $C = 0$), set $D[I] = 0$; else, keep $D[I] = 1$.
 - $I \leftarrow I - 1$; go to step 1.
- * At the end of four steps, the digital output is given by $D_3D_2D_1D_0$.
Example \rightarrow next slide.

Successive Approximation ADC

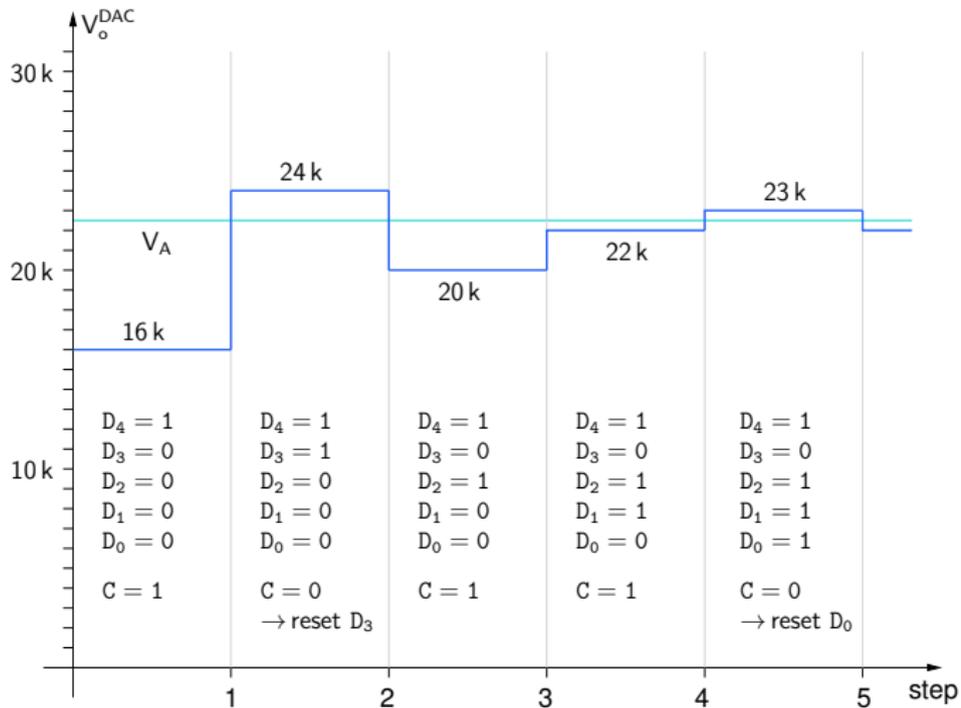
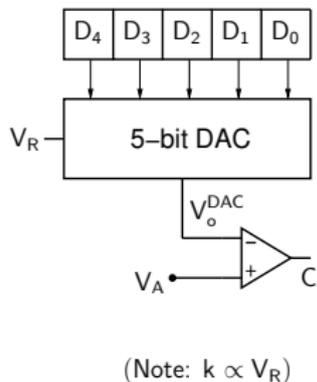


Successive Approximation ADC

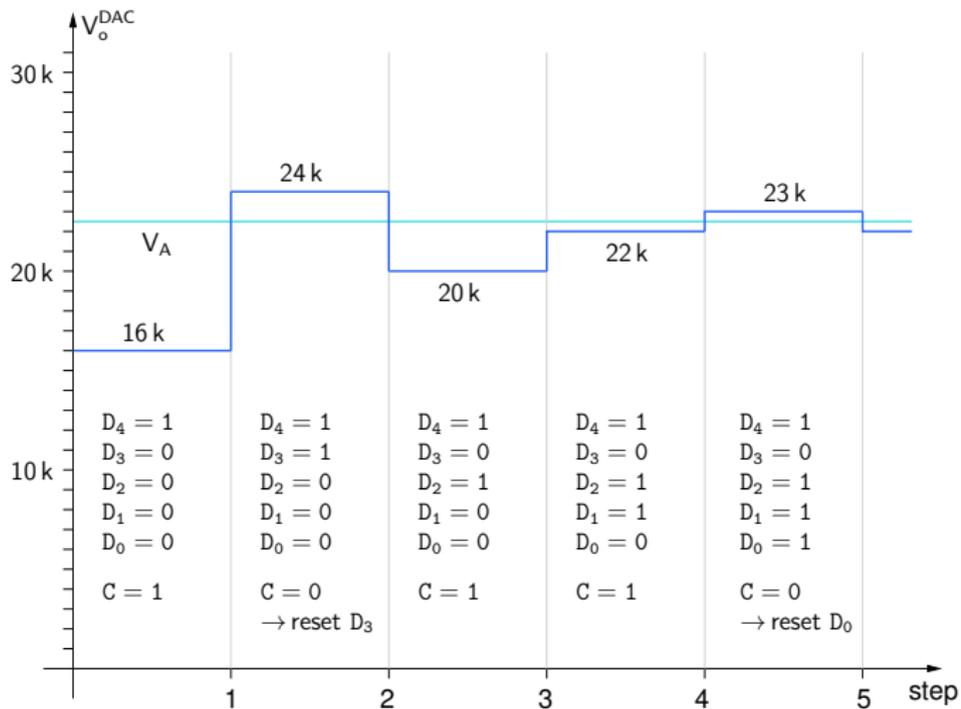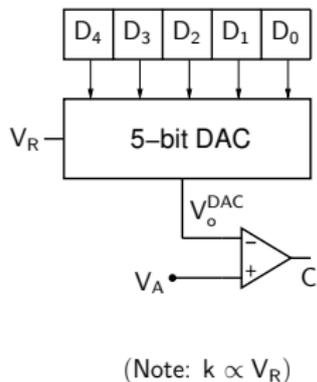


* At the end of the 5th step, we know that the input voltage corresponds to 10110.

Successive Approximation ADC

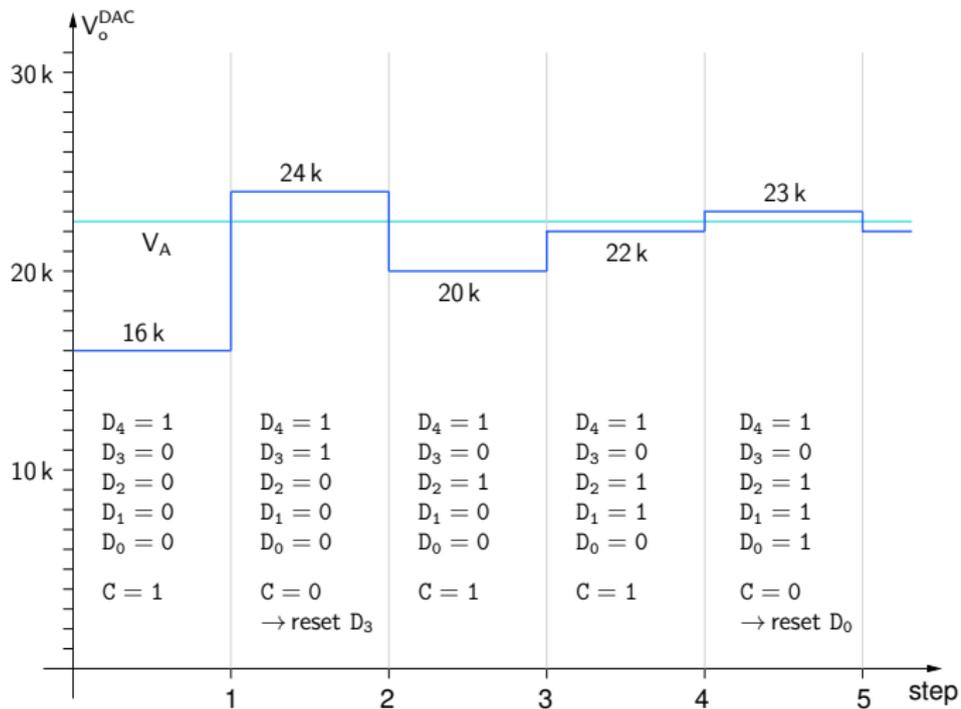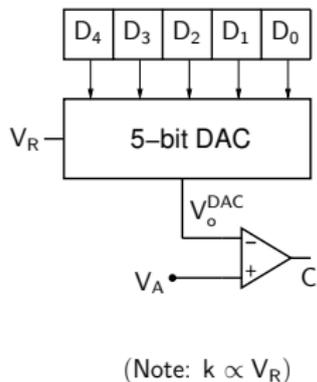


- * At the end of the 5th step, we know that the input voltage corresponds to 10110.
- * For the digital representation to be accurate up to $\pm \frac{1}{2}$ LSB, ΔV corresponding to $\frac{1}{2}$ LSB is added to V_A (see [Taub]).

Successive Approximation ADC

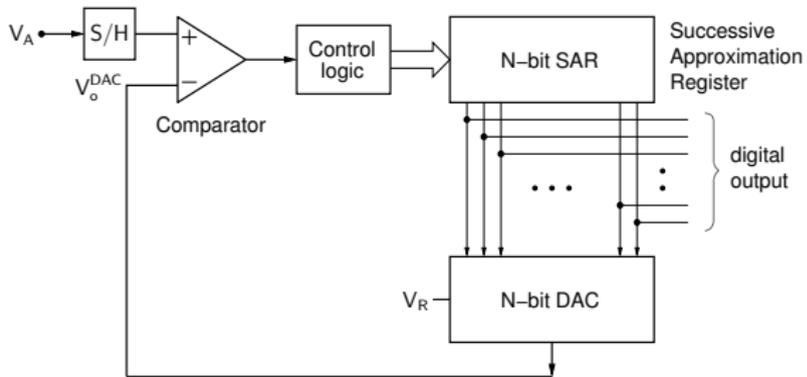


Successive Approximation ADC

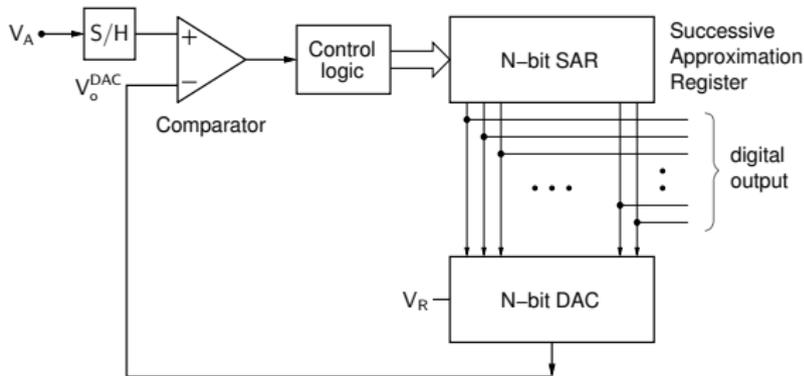


- * Each step (setting SAR bits, comparison of V_A and V_o^{DAC}) is performed in one clock cycle
→ conversion time is N cycles, irrespective of the input voltage value V_A .

Successive Approximation ADC

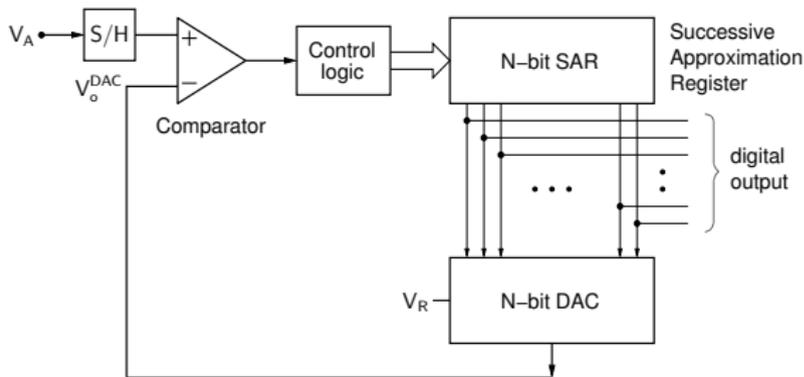



- * Each step (setting SAR bits, comparison of V_A and V_o^{DAC}) is performed in one clock cycle → conversion time is N cycles, irrespective of the input voltage value V_A .
- * S. A. ADCs with built-in or external S/H (sample-and-hold) are available for 8- to 16-bit resolution and conversion times of a few μsec to tens of μsec .

Successive Approximation ADC


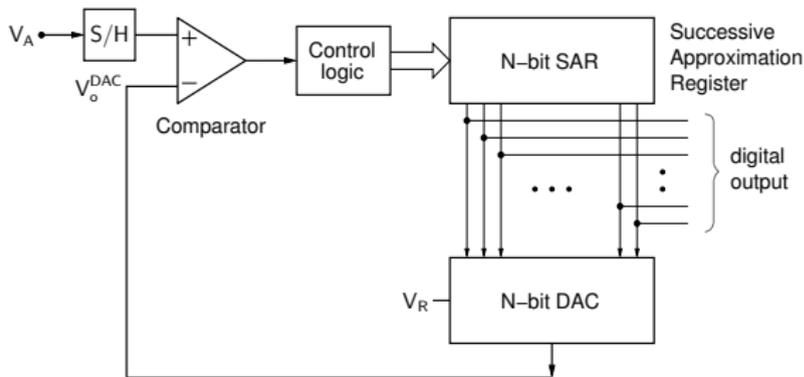


- * Each step (setting SAR bits, comparison of V_A and V_o^{DAC}) is performed in one clock cycle → conversion time is N cycles, irrespective of the input voltage value V_A .
- * S. A. ADCs with built-in or external S/H (sample-and-hold) are available for 8- to 16-bit resolution and conversion times of a few μsec to tens of μsec .
- * Useful for medium-speed applications such as speech transmission with PCM.

Counting ADC

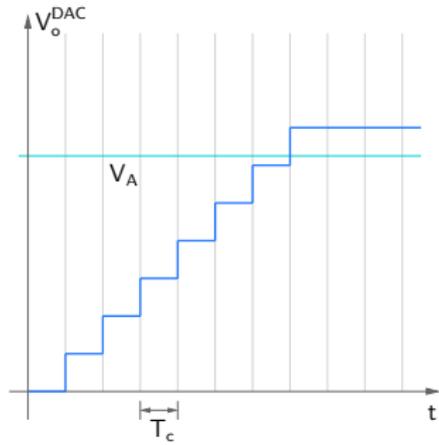
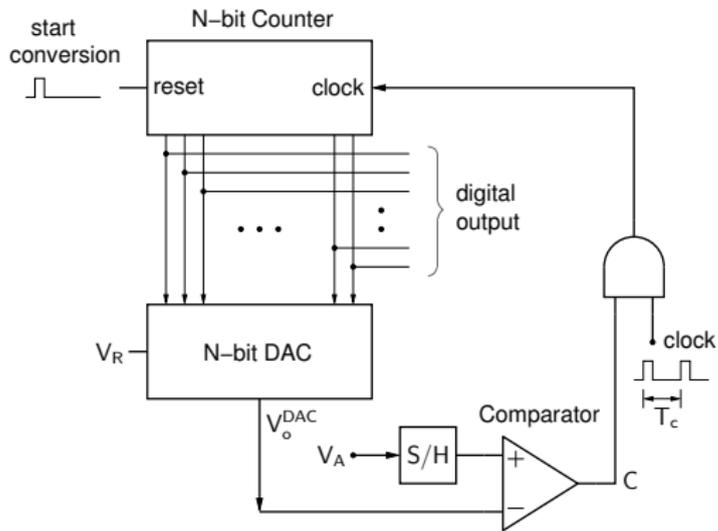


Counting ADC

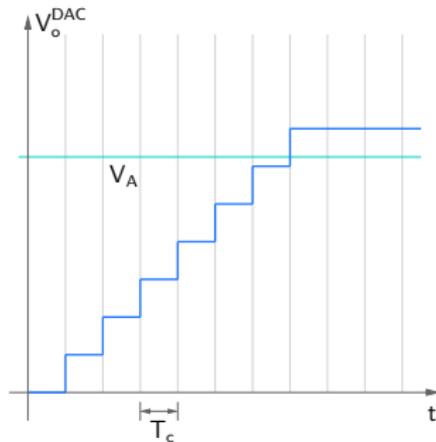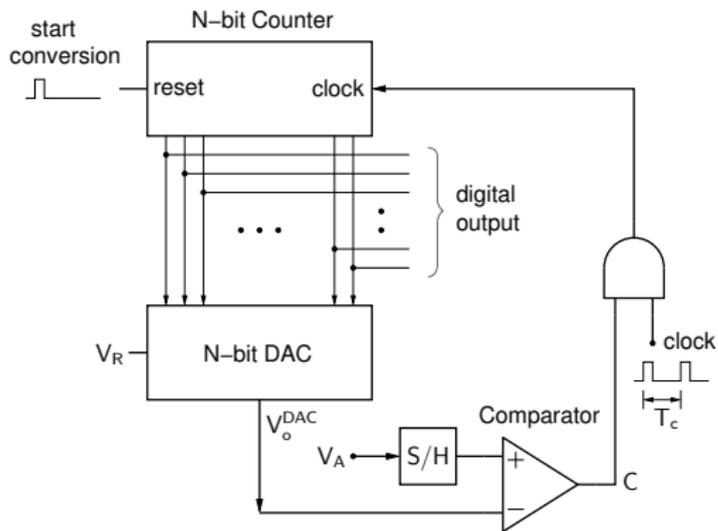


- * The “start conversion” signal clears the counter; counting begins, and V_o^{DAC} increases with each clock cycle.

Counting ADC

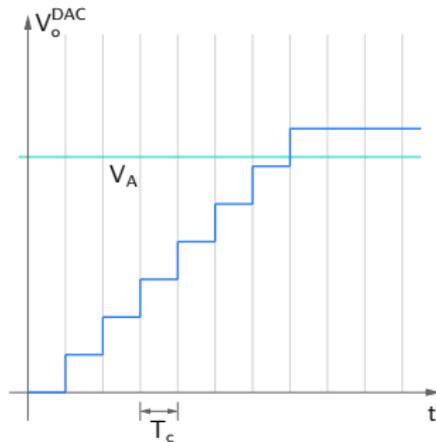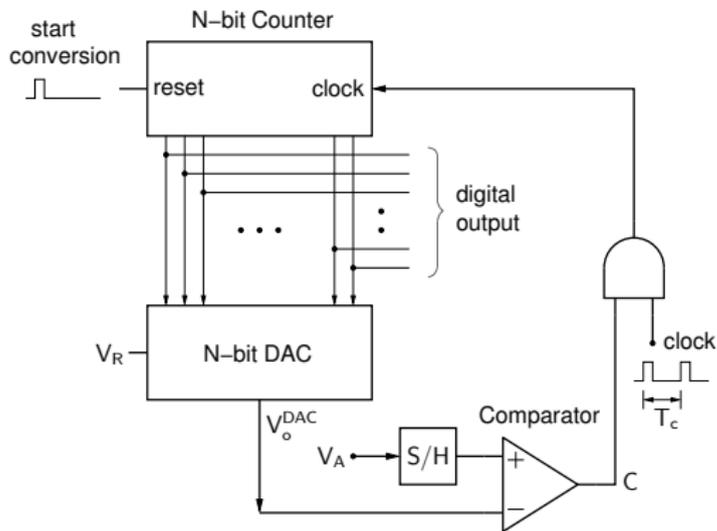



- * The “start conversion” signal clears the counter; counting begins, and V_o^{DAC} increases with each clock cycle.
- * When V_o^{DAC} exceeds V_A , C becomes 0, and counting stops.

Counting ADC


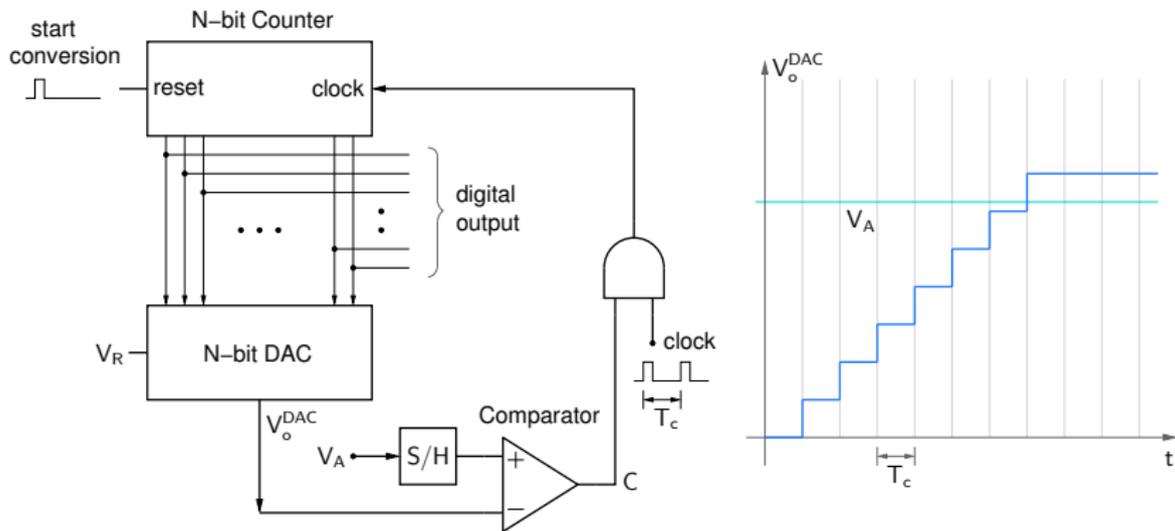


- * The “start conversion” signal clears the counter; counting begins, and V_o^{DAC} increases with each clock cycle.
- * When V_o^{DAC} exceeds V_A , C becomes 0, and counting stops.
- * Simple scheme, but (a) conversion time depends on V_A , (b) slow (takes 2^N clock cycles in the worst case) → tracking ADC (next slide)

Tracking ADC

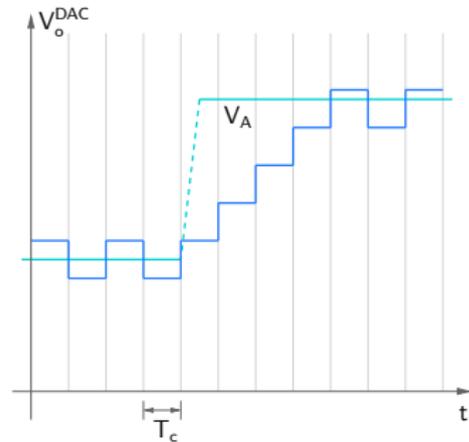
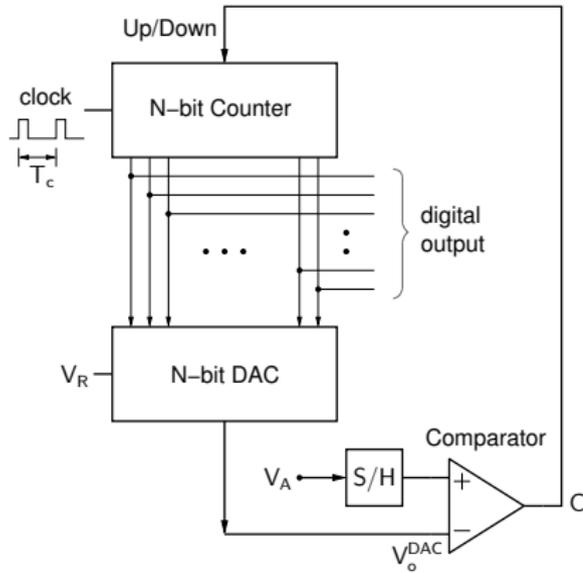


Tracking ADC

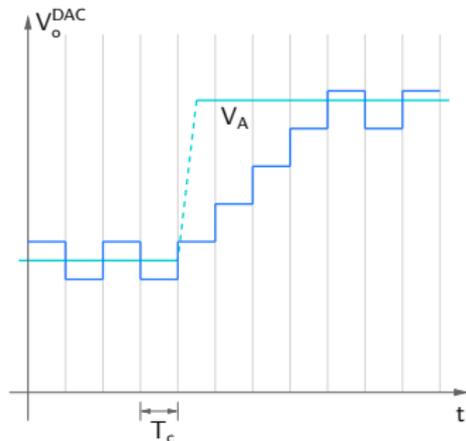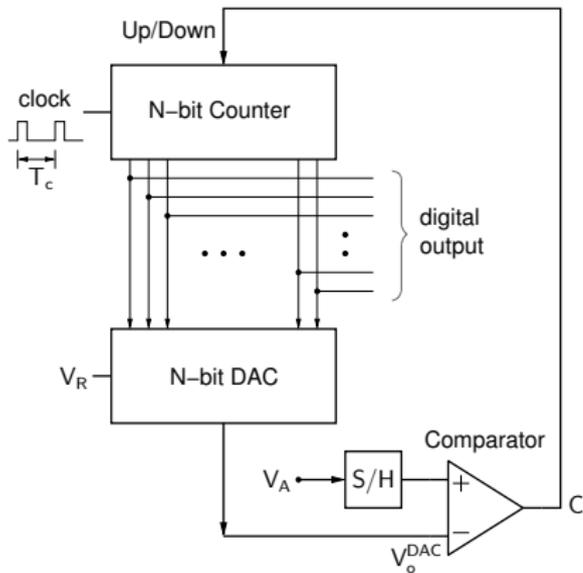



- * The counter counts up if $V_o^{DAC} < V_A$; else, it counts down.

Tracking ADC

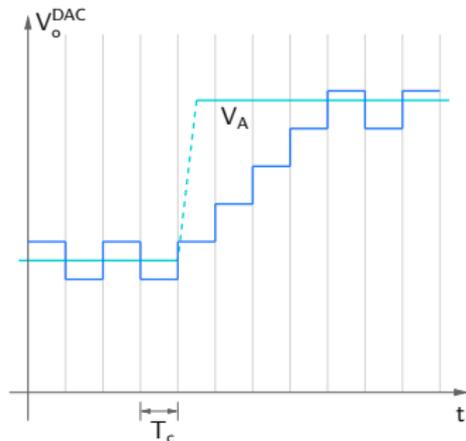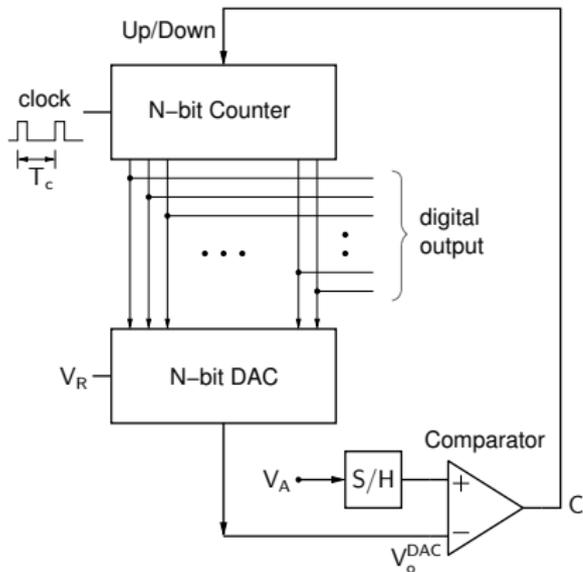



- * The counter counts up if $V_o^{DAC} < V_A$; else, it counts down.
- * If V_A changes, the counter does not need to start from 000...0, so the conversion time is less than that required by a counting ADC.

Tracking ADC

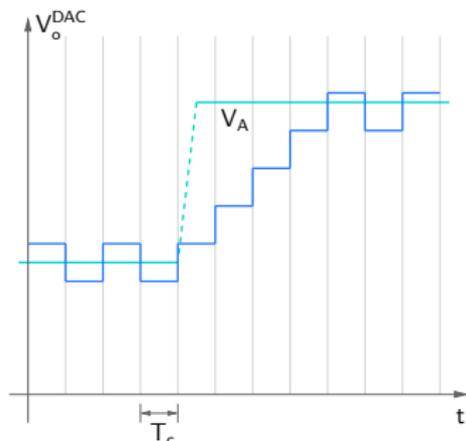
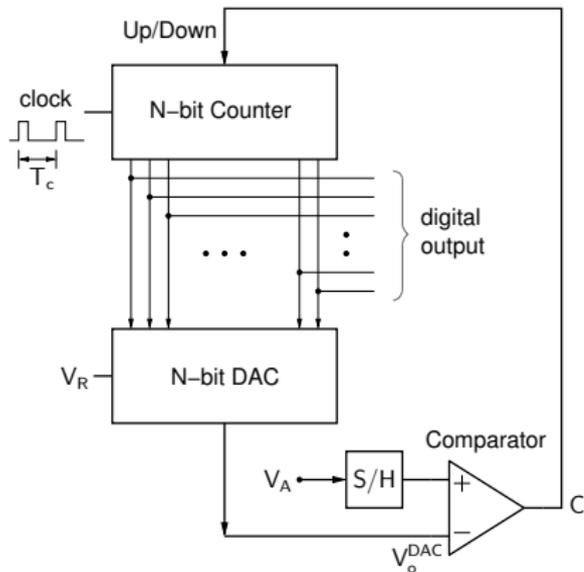


- * The counter counts up if $V_o^{DAC} < V_A$; else, it counts down.
- * If V_A changes, the counter does not need to start from 000...0, so the conversion time is less than that required by a counting ADC.
- * used in low-cost, low-speed applications, e.g., measuring output from a temperature sensor or a strain gauge

Dual-slope ADC

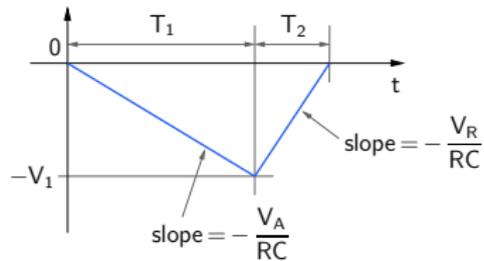
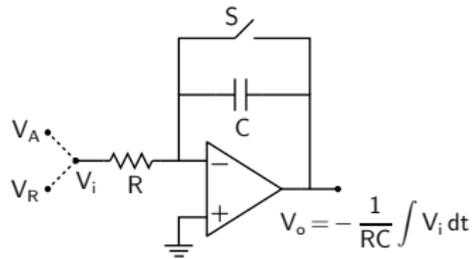


Dual-slope ADC

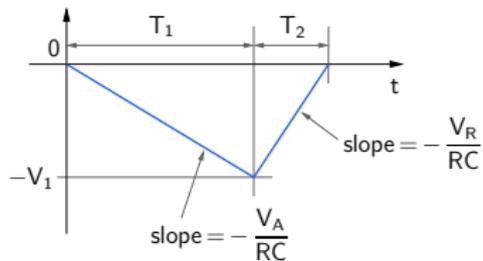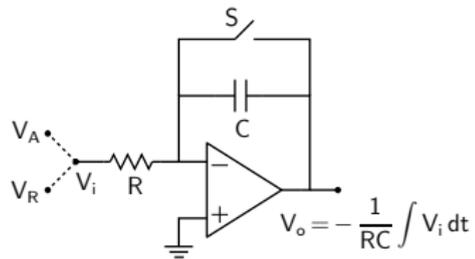



- * $t=0$: reset integrator output V_o to 0V by closing S momentarily.

Dual-slope ADC

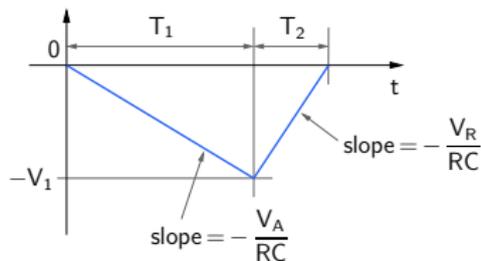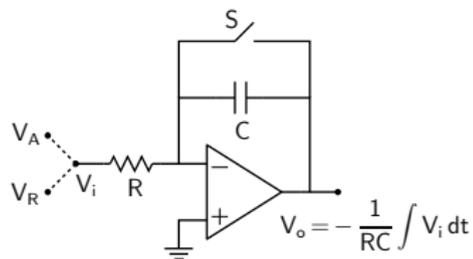



- * $t=0$: reset integrator output V_o to 0V by closing S momentarily.
- * Integrate V_A (voltage to be converted to digital format, assumed to be positive) for a fixed interval T_1 .

Dual-slope ADC

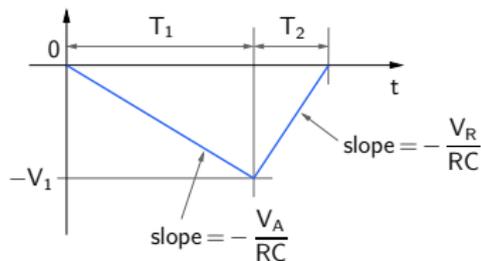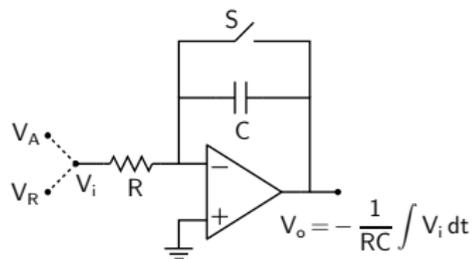



- * $t=0$: reset integrator output V_o to $0V$ by closing S momentarily.
- * Integrate V_A (voltage to be converted to digital format, assumed to be positive) for a fixed interval T_1 .
- * At $t = T_1$, integrator output reaches $-V_1 = -V_A \frac{T_1}{RC}$.

Dual-slope ADC

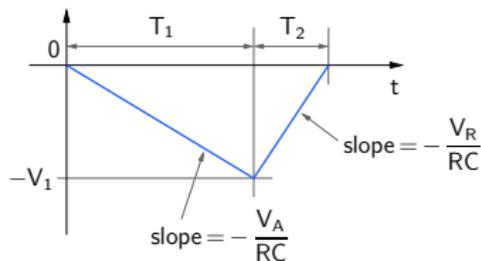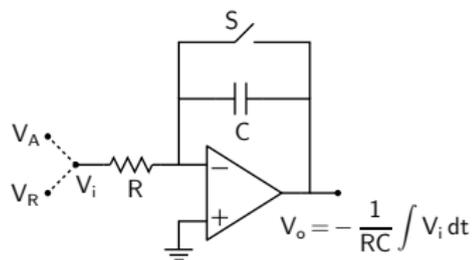



- * $t=0$: reset integrator output V_o to 0V by closing S momentarily.
- * Integrate V_A (voltage to be converted to digital format, assumed to be positive) for a fixed interval T_1 .
- * At $t = T_1$, integrator output reaches $-V_1 = -V_A \frac{T_1}{RC}$.
- * Now apply a reference voltage V_R (assumed to be negative, with $|V_R| > V_A$), and integrate until V_o reaches 0V.

Dual-slope ADC

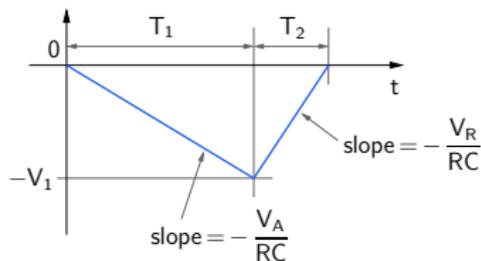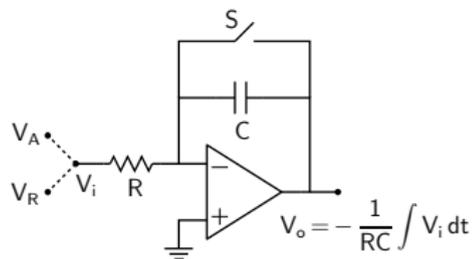



- * $t=0$: reset integrator output V_o to 0V by closing S momentarily.
- * Integrate V_A (voltage to be converted to digital format, assumed to be positive) for a fixed interval T_1 .
- * At $t = T_1$, integrator output reaches $-V_1 = -V_A \frac{T_1}{RC}$.
- * Now apply a reference voltage V_R (assumed to be negative, with $|V_R| > V_A$), and integrate until V_o reaches 0V.
- * Since $V_1 = V_A \frac{T_1}{RC} = |V_R| \frac{T_2}{RC}$, we have $T_2 = T_1 \frac{V_A}{|V_R|} \rightarrow T_2$ gives a measure of V_A .

Dual-slope ADC

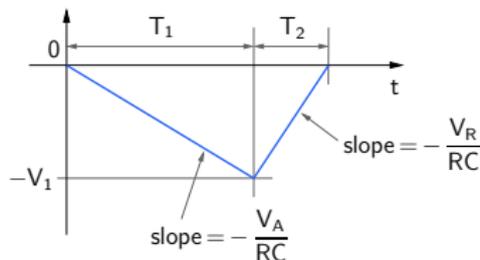
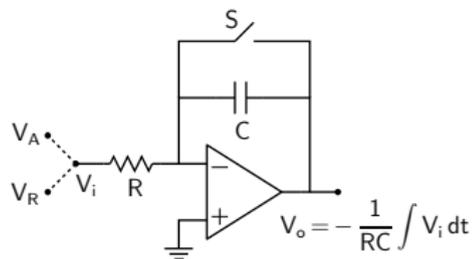


- * $t=0$: reset integrator output V_o to 0V by closing S momentarily.
- * Integrate V_A (voltage to be converted to digital format, assumed to be positive) for a fixed interval T_1 .
- * At $t = T_1$, integrator output reaches $-V_1 = -V_A \frac{T_1}{RC}$.
- * Now apply a reference voltage V_R (assumed to be negative, with $|V_R| > V_A$), and integrate until V_o reaches 0V.
- * Since $V_1 = V_A \frac{T_1}{RC} = |V_R| \frac{T_2}{RC}$, we have $T_2 = T_1 \frac{V_A}{|V_R|} \rightarrow T_2$ gives a measure of V_A .
- * In the dual-slope ADC, a counter output – which is proportional to T_2 – provides the desired digital output.

Dual-slope ADC

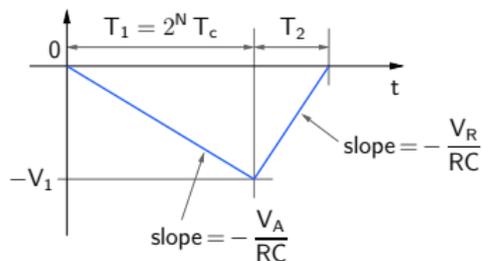
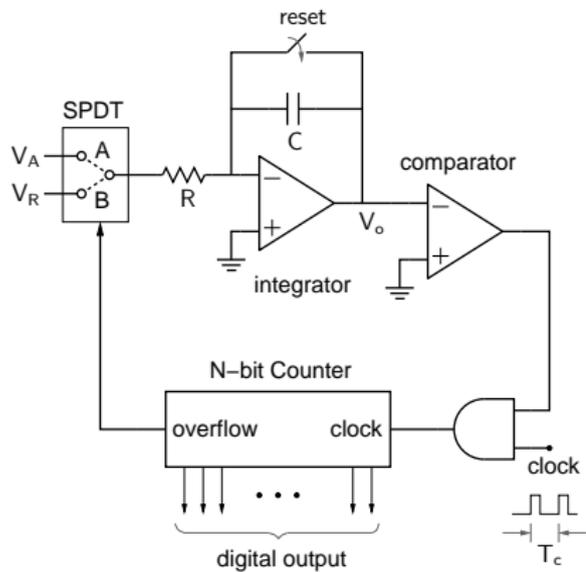


Dual-slope ADC

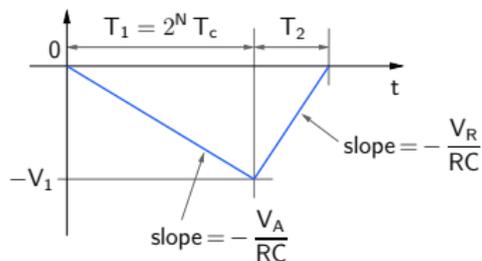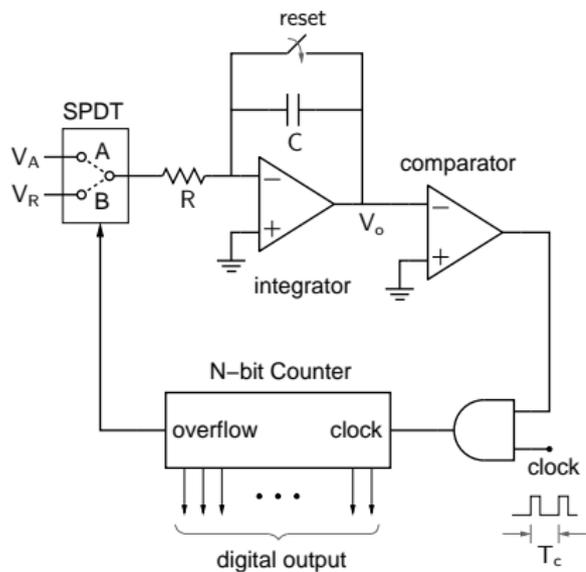



* Start: counter reset to 000...0, SPDT in position A.

Dual-slope ADC

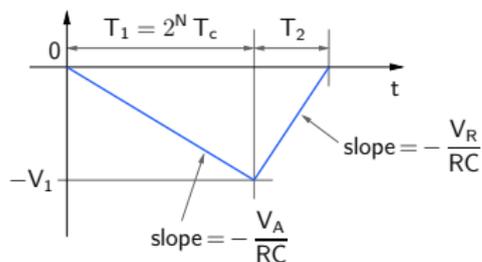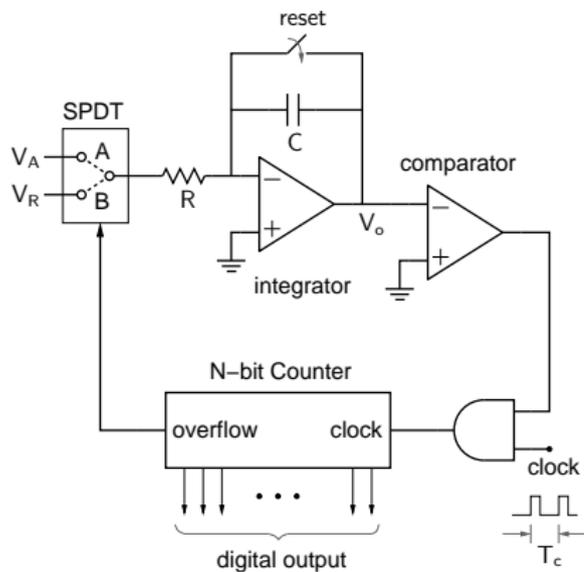

- * Start: counter reset to $000 \dots 0$, SPDT in position A.
- * Counter counts up to 2^N at which point the overflow flag becomes 1, and SPDT switches to position B $\rightarrow T_1 = 2^N T_c$ where T_c is the clock period.

Dual-slope ADC

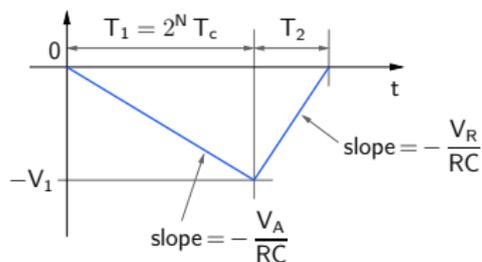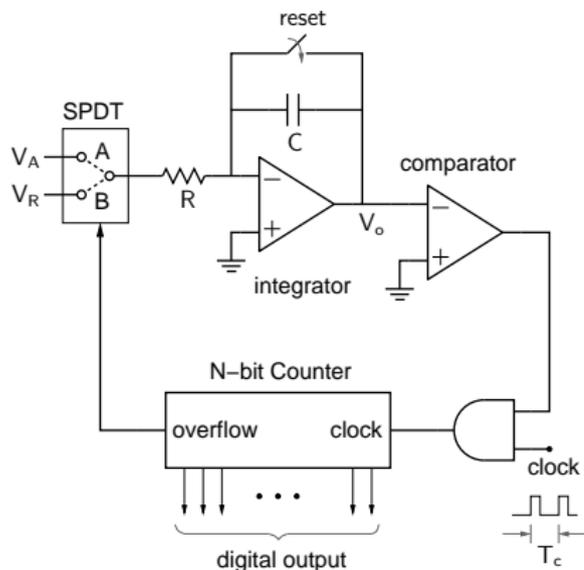

- * Start: counter reset to $000 \dots 0$, SPDT in position A.
- * Counter counts up to 2^N at which point the overflow flag becomes 1, and SPDT switches to position B $\rightarrow T_1 = 2^N T_c$ where T_c is the clock period.
- * The counter starts counting again from $000 \dots 0$, and stops counting when V_o crosses 0V. The counter output gives T_2 in binary format.

- * K. Gopalan, *Introduction to Digital Microelectronic Circuits*, Tata McGraw-Hill, New Delhi, 1978.
- * H. Taub and D. Schilling, *Digital Integrated Electronics*, McGraw-Hill, 1977.